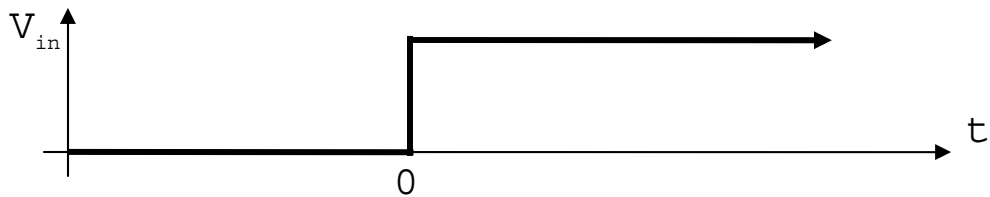



Problem 3-11

Sketch the approximate output from a differentiating circuit with $R=10\text{ k}\Omega$, $C=0.01\mu\text{F}$ for the following inputs:


(a)




(b)

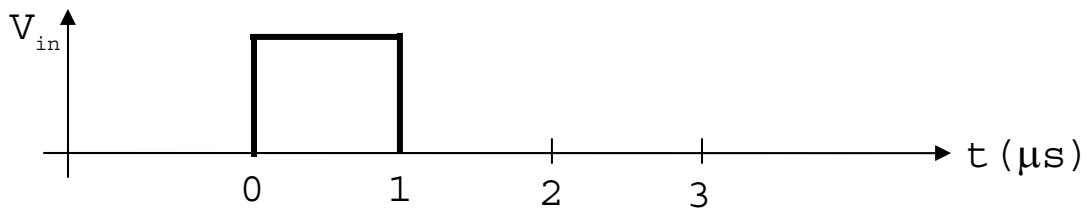

(c)

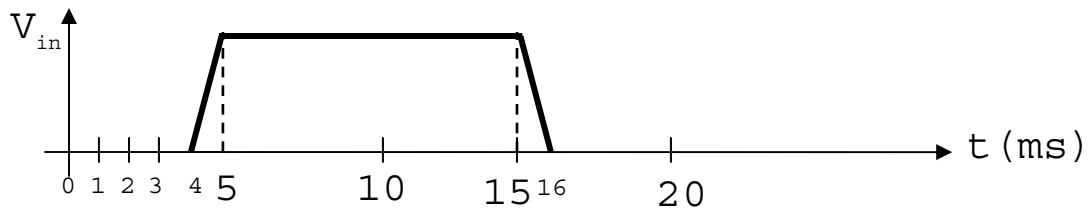


(d)

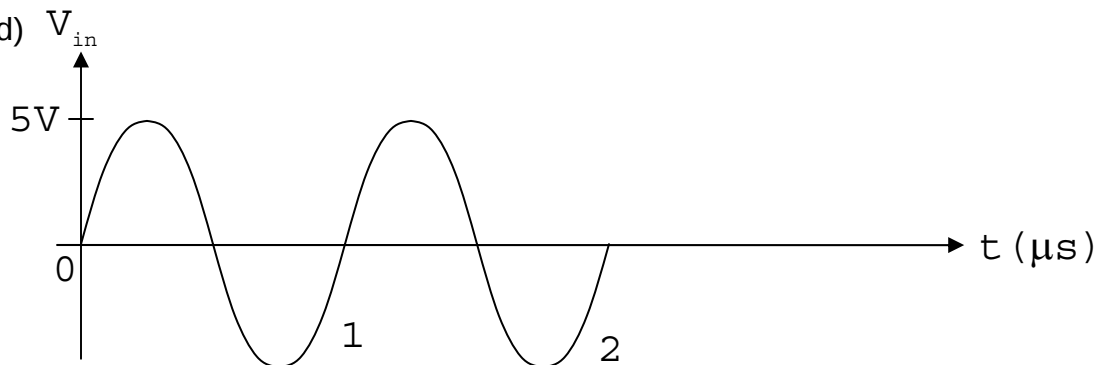


Solution:

RC time constant :
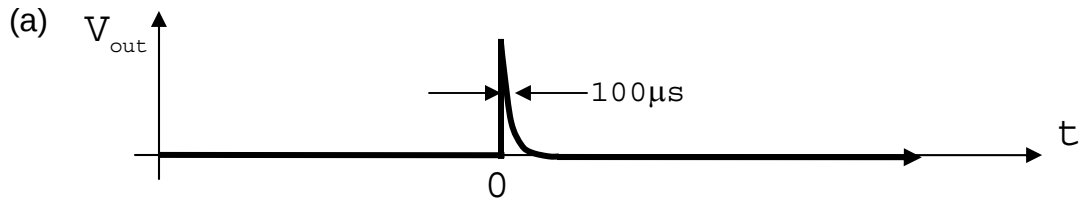
$$RC = (10 \times 10^3)(0.01 \times 10^{-6}) = 1 \times 10^{-4} \text{ s or } 100 \mu\text{s or } 0.1 \text{ ms}$$



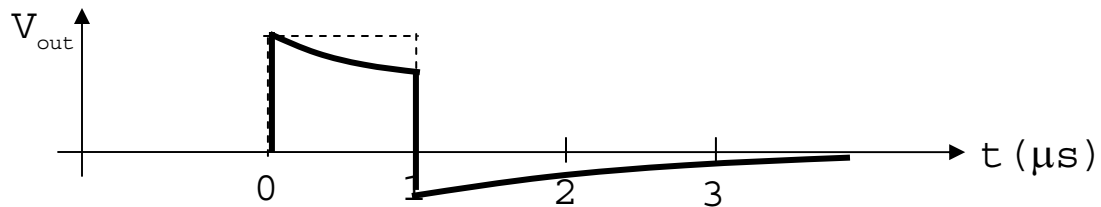(b) Note that the width of the pulse is much shorter than the time constant (!1%).



(c)

At the leading edge,

$$V_{in} = \frac{Q}{C} + IR \Rightarrow \frac{dV_{in}}{dt} = \frac{1}{C} \frac{dQ}{dt} + R \frac{dI}{dt}$$

$$\Rightarrow K = \frac{I}{C} + R \frac{dI}{dt} \quad \left(\frac{dV_{in}}{dt} = K \right)$$


Integrating,

$$I = KC(1 - e^{-t/RC})$$

$$\therefore V_{out} = V_R = IR$$

$$= KCR(1 - e^{-t/RC})$$

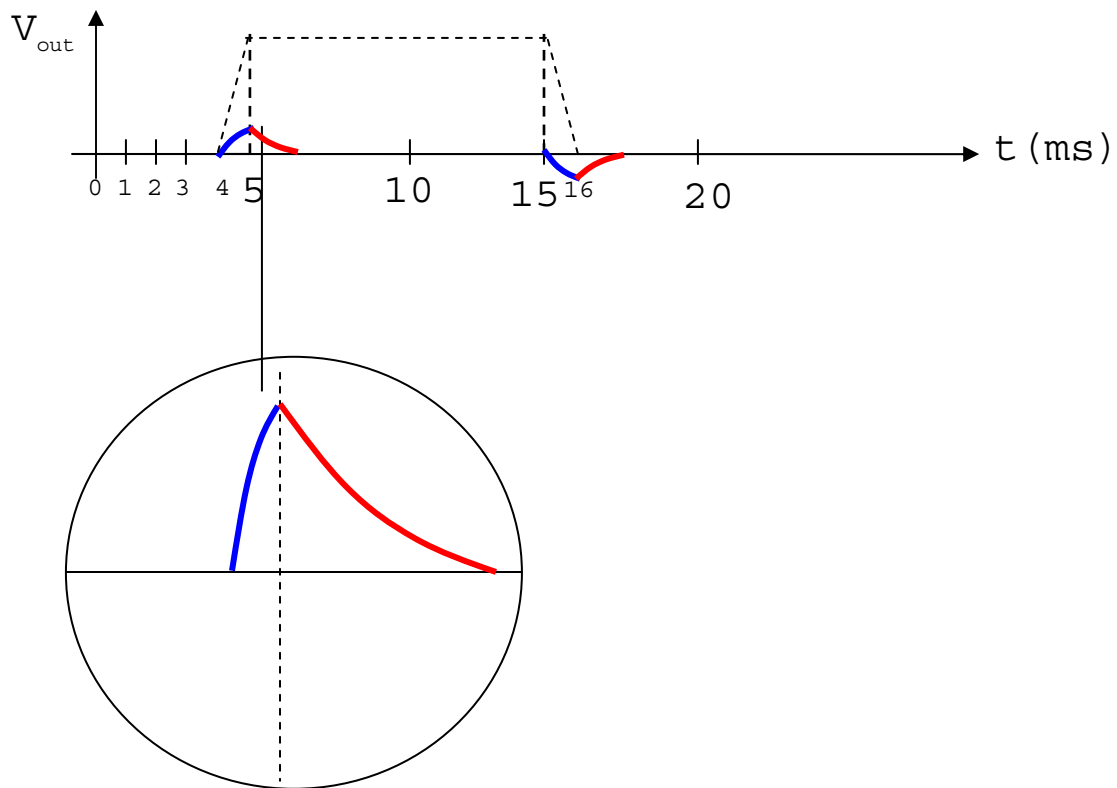The time scale ($\sim 1 \text{ ms}$) is much longer than the RC time constant (0.1 ms). At 1 ms , $V_{out} \sim KRC = 0.1 V_{in, \text{max}}$.



(d)

$$X_c = \frac{1}{i\omega C}$$

$$I = \frac{V_{in}}{R + X_c} = \frac{V_{in}}{R + \frac{1}{i\omega C}} = \frac{i\omega C V_{in}}{1 + i\omega CR}$$

$$= V_{in} \left(\frac{i\omega C}{1 + i\omega CR} \right)$$

$$V_{out} = IR = V_{in} \left(\frac{i\omega RC}{1 + i\omega CR} \right)$$

$$= V_{in} \left(\frac{i\omega RC}{1 + i\omega CR} \right) \left(\frac{1 - i\omega CR}{1 - i\omega CR} \right)$$

$$= V_{in} \left(\frac{\omega^2 C^2 R^2 + i\omega CR}{1 + \omega^2 C^2 R^2} \right)$$

$$\left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \left| \frac{\omega CR \sqrt{1 + \omega^2 C^2 R^2}}{1 + \omega^2 C^2 R^2} \right|$$

$$= \frac{\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}}$$

V_{out} leads V_{in} by a phase angle of $\tan^{-1} \left(\frac{1}{\omega RC} \right)$

$$RC = 10^{-4} \text{ s}$$


Input wave has a period of $1 \mu\text{s} \Rightarrow f = 1 \text{ MHz}$

$$\omega = 2\pi f = 6.283 \times 10^6 \text{ Hz}$$

$$\left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \frac{\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}} = \frac{6.283 \times 10^6 \times 10^{-4}}{\sqrt{1 + (6.283 \times 10^6 \times 10^{-4})^2}} = 1.000$$

With $|V_{\text{in}}| = 5\text{V}$, $|V_{\text{out}}| = 5\text{V}$

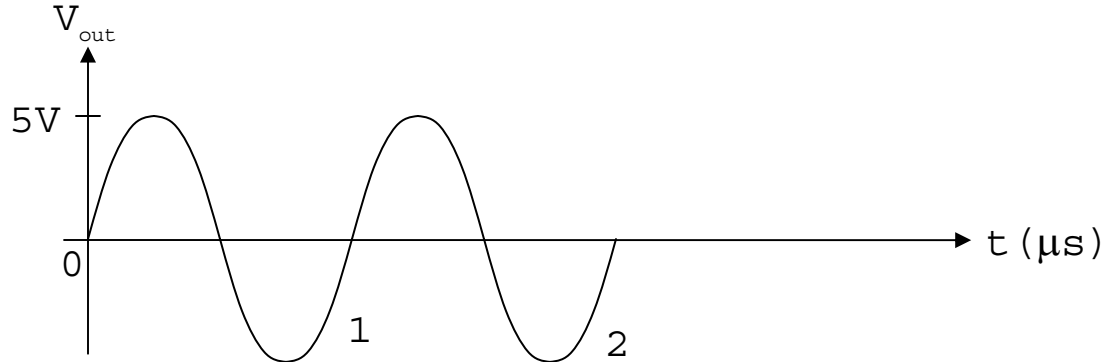
V_{out} leads V_{in} by a phase angle of $\tan^{-1} \left(\frac{1}{6.283 \times 10^6 \times 10^{-4}} \right) = 0.092^\circ$




In the case for an integrator (not asked by the question):

RC time constant :
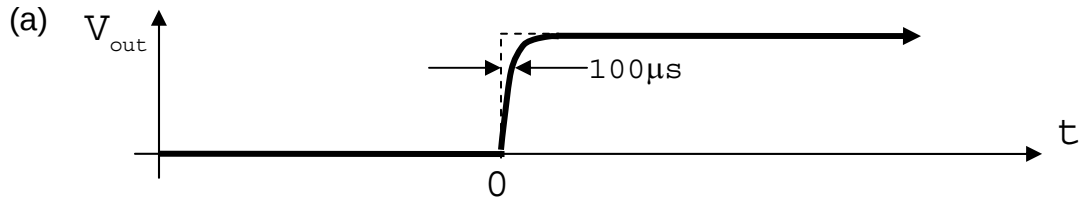
$$RC = (10 \times 10^3)(0.01 \times 10^{-6}) = 1 \times 10^{-4} \text{ s or } 100 \mu\text{s or } 0.1 \text{ ms}$$



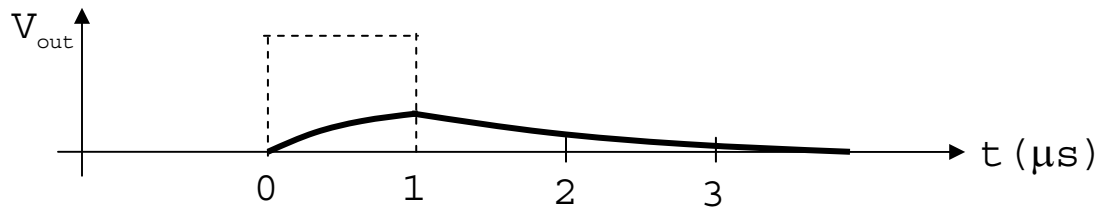(b) Note that the width of the pulse is much shorter than the time constant (1%).



(c)

At the leading edge,

$$V_{in} = \frac{Q}{C} + IR \Rightarrow \frac{dV_{in}}{dt} = \frac{1}{C} \frac{dQ}{dt} + R \frac{dI}{dt}$$

$$\Rightarrow K = \frac{I}{C} + R \frac{dI}{dt} \quad \left(\frac{dV_{in}}{dt} = K \right)$$

Integrating,

$$I = KC(1 - e^{-t/RC})$$


$$\therefore V_{out} = V_c = V_{in} - IR$$

$$= Kt - KCR(1 - e^{-t/RC})$$

At the discharging edge, similar mathematics show

$$V_{out} = (V_{max} - Kt) - KCR(e^{-t/RC} - 1)$$

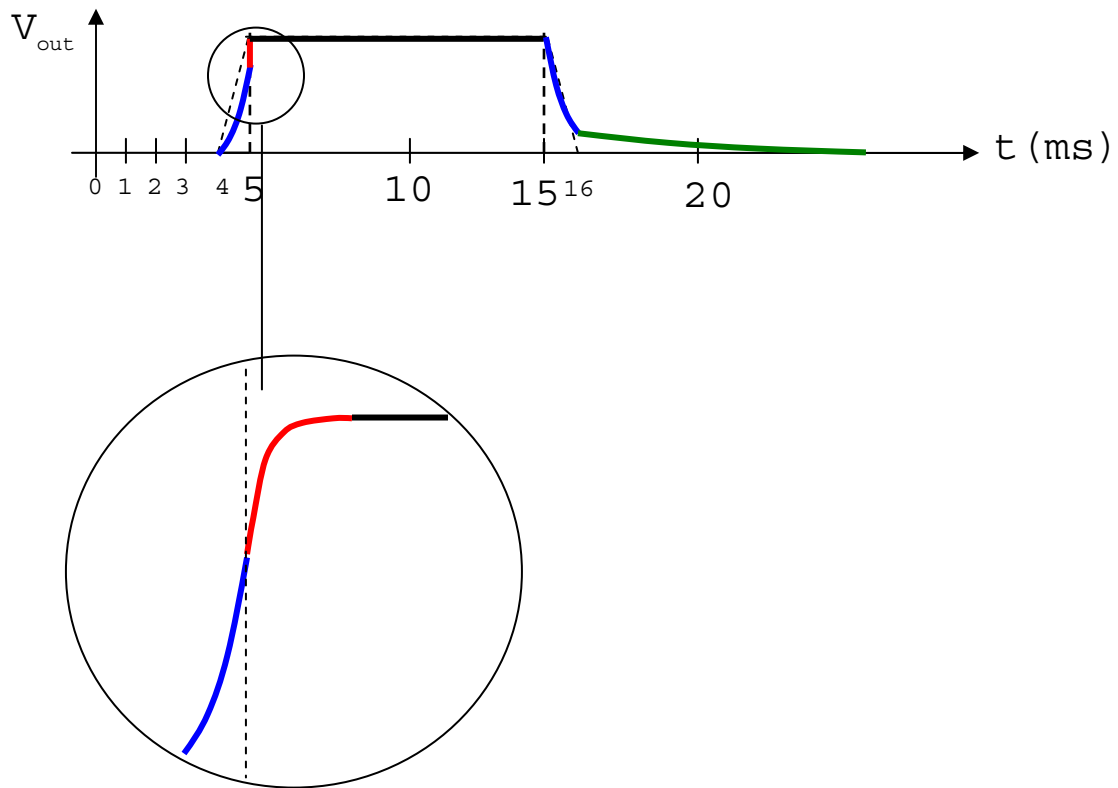The time scale ($\sim 1 \text{ ms}$) is much longer than the RC time constant (0.1 ms). At 1 ms , $V_{out} \sim K(1 \text{ ms}) - K(0.1 \text{ ms}) = K(0.9 \text{ ms})$, or 90% of the maximum voltage.



(d)

$$X_C = \frac{1}{i\omega C}$$

$$I = \frac{V_{in}}{R + X_C} = \frac{V_{in}}{R + \frac{1}{i\omega C}} = \frac{i\omega C V_{in}}{1 + i\omega CR}$$

$$= V_{in} \left(\frac{i\omega C}{1 + i\omega CR} \right)$$

$$V_{out} = IX_C = V_{in} \left(\frac{i\omega C}{1 + i\omega CR} \right) \left(\frac{1}{i\omega C} \right)$$

$$= V_{in} \left(\frac{1}{1 + i\omega CR} \right)$$

$$= V_{in} \left(\frac{1}{1 + i\omega CR} \right) \left(\frac{1 - i\omega CR}{1 - i\omega CR} \right)$$

$$= V_{in} \left(\frac{1 - i\omega CR}{1 + \omega^2 C^2 R^2} \right)$$

$$\begin{aligned}\left|\frac{V_{\text{out}}}{V_{\text{in}}}\right| &= \left|\frac{1 - i\omega CR}{1 + \omega^2 C^2 R^2}\right| \\ &= \frac{\sqrt{1 + \omega^2 C^2 R^2}}{1 + \omega^2 C^2 R^2} \\ &= \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}\end{aligned}$$

V_{out} lags V_{in} by a phase angle of $\tan^{-1}(\omega RC)$

$$RC = 10^{-4} \text{ s}$$

Input wave has a period of $1\mu\text{s} \Rightarrow f = 1 \text{ MHz}$

$$\omega = 2\pi f = 6.283 \times 10^6 \text{ Hz}$$

$$\left|\frac{V_{\text{out}}}{V_{\text{in}}}\right| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}} = \frac{1}{\sqrt{1 + (6.283 \times 10^6 \times 10^{-4})^2}} = 1.591 \times 10^{-3}$$

$$\text{With } |V_{\text{in}}| = 5\text{V}, |V_{\text{out}}| = 7.96\text{mV}$$

V_{out} lags V_{in} by a phase angle of $\tan^{-1}(6.283 \times 10^6 \times 10^{-4}) = 89.9^\circ$

