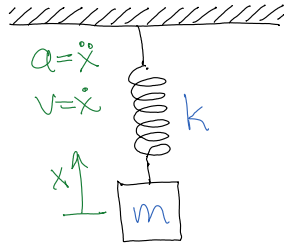


L17 Oscillators

Thursday, September 24, 2020 12:07



note: mg absorbed in equilibrium $x_0 = 0$.

$$F = ma = -kx$$

$$\ddot{x} + \omega_0^2 x = 0 \quad \omega_0^2 = k/m$$

$$\text{let } x = e^{st}$$


$$s^2 x + \omega_0^2 x = 0 \quad s = \pm i\omega_0$$

$$x = C_1 e^{i\omega_0 t} + C_2 e^{-i\omega_0 t} = \underbrace{B_1}_{C_1 + C_2} \cos \omega_0 t + \underbrace{B_2}_{i(C_1 - C_2)} \sin \omega_0 t$$

$$= \text{Re}\{ \underbrace{C e^{i\omega_0 t}}_{A e^{-i\delta}} \} = A \cos(\omega_0 t - \delta) = \underbrace{A \cos \delta}_{B_1} \cos \omega_0 t + \underbrace{A \sin \delta}_{B_2} \sin \omega_0 t$$

$$H = T + V = \frac{1}{2} m v^2 + \frac{1}{2} k x^2 = \text{const.} \quad T_{\max} = V_{\max}$$
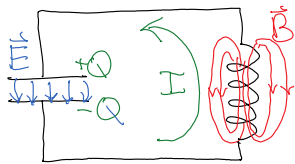
$$= \frac{1}{2} m \omega^2 A^2 \sin^2(\omega t - \delta) + \frac{1}{2} k A^2 \cos^2(\omega t - \delta) =$$




$$Q = CV \quad [\text{Coulombs}]$$

$$V = L I \quad [\text{Faraday}]$$

$$L \ddot{Q} + \frac{1}{C} Q = 0$$
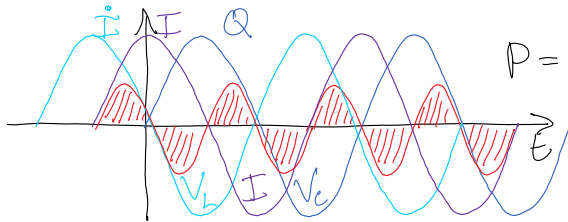
$$\ddot{Q} + \omega_0^2 Q = 0 \quad \omega_0^2 = \frac{1}{LC}$$



$$P = IV = \underbrace{Q_0 \omega \cos(\omega t - \delta)}_{[\text{capacitor}]} \cdot \underbrace{\frac{Q_0}{C} \sin(\omega t - \delta)}_{[\text{inductor}]} = \frac{Q_0^2 \omega}{2C} \sin 2(\omega t - \delta)$$

$$= I_0 \sin(\omega t - \delta) \cdot L(-I_0 \omega) \cos(\omega t - \delta) = -LI_0^2 \omega \sin(2\omega t - \delta)$$