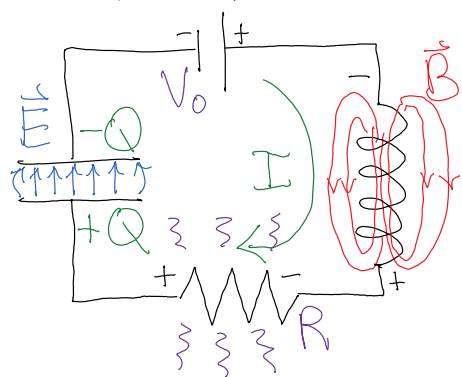


L18 Impedance analogy

Saturday, September 26, 2020 08:10

LRC - circuit



$$V_L = L \dot{I}$$

$$V_R = RI$$

$$V_C = \frac{1}{C} Q$$

$$V_0 = \mathcal{E}$$

$$L \ddot{Q}_0 + R \dot{Q}_0 + \frac{1}{C} (Q_0 + C \mathcal{E}) = 0$$

$\ddot{Q} \quad \dot{Q} \quad Q \rightarrow \mathcal{E}(t)$

$$\beta = R/2L \quad \omega_0^2 = 1/LC \quad f_0 = \mathcal{E}/L$$

Universal: $\ddot{X} + 2\beta \dot{X} + \omega_0^2 X = f_0$ or $\boxed{DX = f_0}$

let $x = e^{st}$, $(s^2 + 2\beta s + \omega_0^2)X = 0$

$$= (s + \beta)^2 - (\beta^2 - \omega_0^2) = (s + \beta - \beta_1)(s + \beta + \beta_1)$$

$$s = -\beta \pm \beta_1 = -\beta \pm i\omega_1$$

$$\beta^2 - \omega_0^2 = \beta_1^2 = -(\omega_1^2 = \omega_0^2 - \beta^2)$$

overdamped: β_1 real ($\omega_0 < \beta$)

$$x = C_1 e^{(-\beta + \beta_1)t} + C_2 e^{(-\beta - \beta_1)t} = e^{-\beta t} (B_1 \cosh(\beta_1 t) + B_2 \sinh(\beta_1 t))$$

underdamped: ω_1 real ($\beta < \omega_0$)


$$x = C_1 e^{(-\beta + i\omega_1)t} + C_2 e^{(-\beta - i\omega_1)t} = e^{-\beta t} (B_1 \cos(\omega_1 t) + B_2 \sin(\omega_1 t))$$

critically damped: $\omega_1 = \beta_1 = 0$ ($\beta = \omega_0$)

[absorb β or ω_1 into C_2]

$$x = B_1 e^{-\beta t} + B_2 t e^{-\beta t}$$

Damped Oscillator

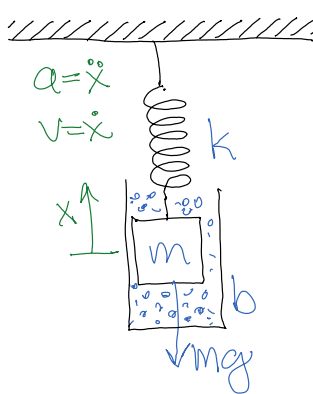

$$F_{\Sigma} = ma$$

$$F_k = -kx$$

$$F_b = -b\dot{x}$$


$$F_g = mg$$

$$m \ddot{x}_0 + b \dot{x}_0 + k(x_0 - \frac{mg}{k}) = 0$$

$\ddot{x} \quad \dot{x} \quad x \rightarrow F_0(t)$

$$\beta = b/2m \quad \omega_0^2 = k/m \quad f_0 = F_0/m$$

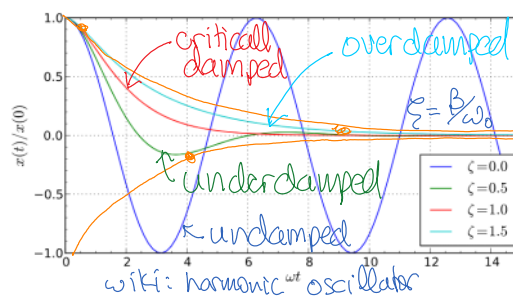inhomogeneous: $f_0 \neq 0$ or $\boxed{DX = f_0}$ $D = \frac{d^2}{dt^2} + 2\beta \frac{d}{dt} + \omega_0^2$ (linear operator / matrix)
homogeneous: $f_0 = 0$



Initial conditions:

$$\begin{aligned} x_0 &= B_1 \\ \dot{x}_0 &= -\beta B_1 + \omega_1 B_2 \\ \omega_1 B_2 &= \dot{x}_0 + \beta x_0 \end{aligned}$$

$$\begin{aligned} x &= e^{-\beta t} \left(x_0 \cos \omega_1 t + \frac{\dot{x}_0 + \beta x_0}{\omega_1} \sin \omega_1 t \right) \quad [\text{underdamped}] \\ &= e^{-\beta t} \left(x_0 \cosh \beta t + \frac{\dot{x}_0 + \beta x_0}{\beta} \sinh \beta t \right) \quad [\text{overdamped}] \\ &= e^{-\beta t} (x_0 + (\dot{x}_0 + \beta x_0)t) \quad [\text{critically damped}] \end{aligned}$$

Impedance Analogy:

$$I = I_0 e^{i\omega t} \rightarrow \dot{I} = i\omega I \quad Q = \frac{1}{\omega} I$$



$$V = RI \rightarrow (Z = R + iX) I \quad F = bv = Zv$$

$$\left[\underbrace{R}_{\text{resistance}} + \underbrace{\left(i\omega L + \frac{1}{i\omega C} \right)}_{\text{reactance}} \right] I$$

$$X = \omega L - \frac{1}{\omega C}$$

$$= [b + i(\omega m - k/\omega)] v$$

also treat m as "force"

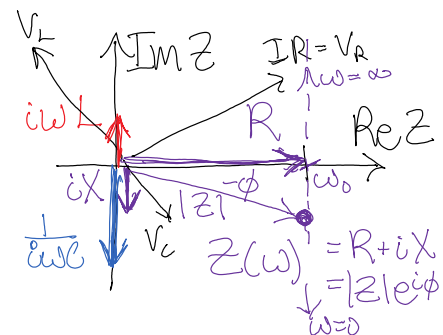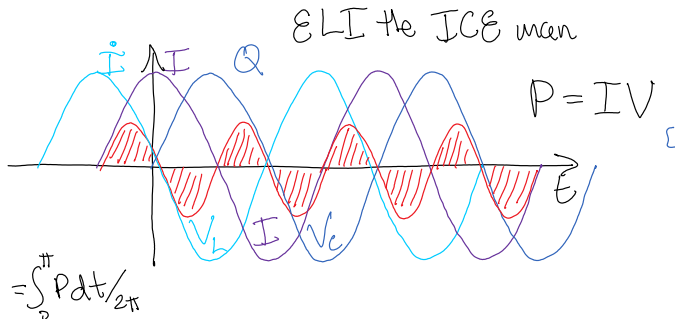

$$\langle P \rangle = \frac{1}{2} V I^* = \frac{1}{2} Z I^* I = \frac{1}{2} (R + iX) I^2$$

R: dissipative - heat loss
X: reactive - transferred.