
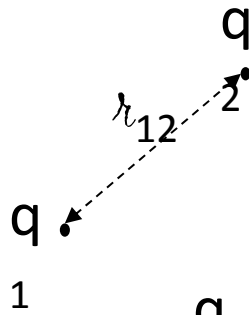


Energy stored in a capacitor

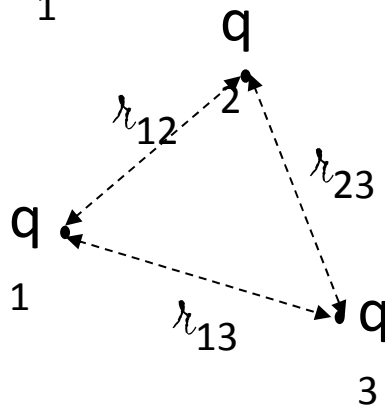
# Energy to Assemble a Collection of Charges



$$W = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r_{12}}$$



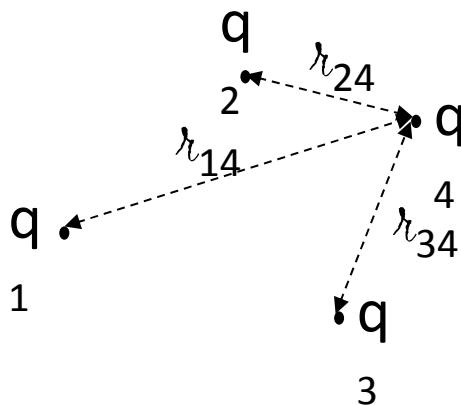
$$W = \left( \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r_{12}} \right) + \left( \frac{1}{4\pi\epsilon_0} \frac{q_1 q_3}{r_{13}} + \frac{1}{4\pi\epsilon_0} \frac{q_2 q_3}{r_{23}} \right)$$



$$W = \left( \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r_{12}} \right) + \left( \frac{1}{4\pi\epsilon_0} \frac{q_1 q_3}{r_{13}} + \frac{1}{4\pi\epsilon_0} \frac{q_2 q_3}{r_{23}} \right) + \left( \frac{1}{4\pi\epsilon_0} \frac{q_1 q_4}{r_{14}} + \frac{1}{4\pi\epsilon_0} \frac{q_2 q_4}{r_{24}} + \frac{1}{4\pi\epsilon_0} \frac{q_3 q_4}{r_{34}} \right)$$


## Energy Stored in a Capacitor

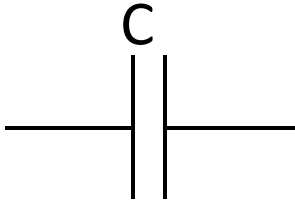

Energy stored in a charged capacitor:

$$U = \frac{1}{2} CV^2$$

(Do not forget  $C = \frac{Q}{V}$  .)

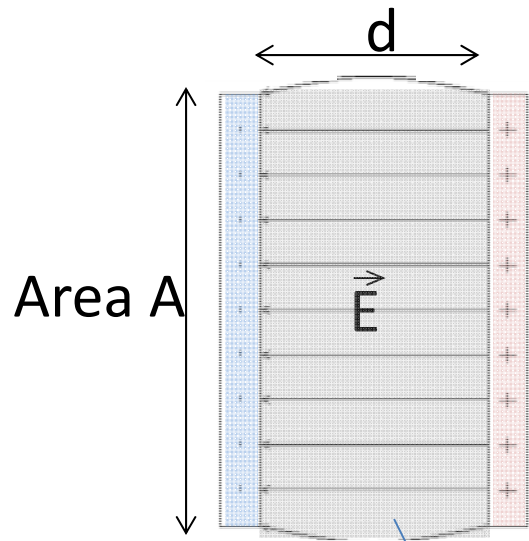


Volume  $\Omega = Ad$

Energy density stored in an electric field:

$$u_E = \frac{U}{\Omega} = \frac{1}{2} \epsilon_0 E^2$$

## Class 17. Capacitors in parallel and in series I

## Connecting Capacitors in Parallel

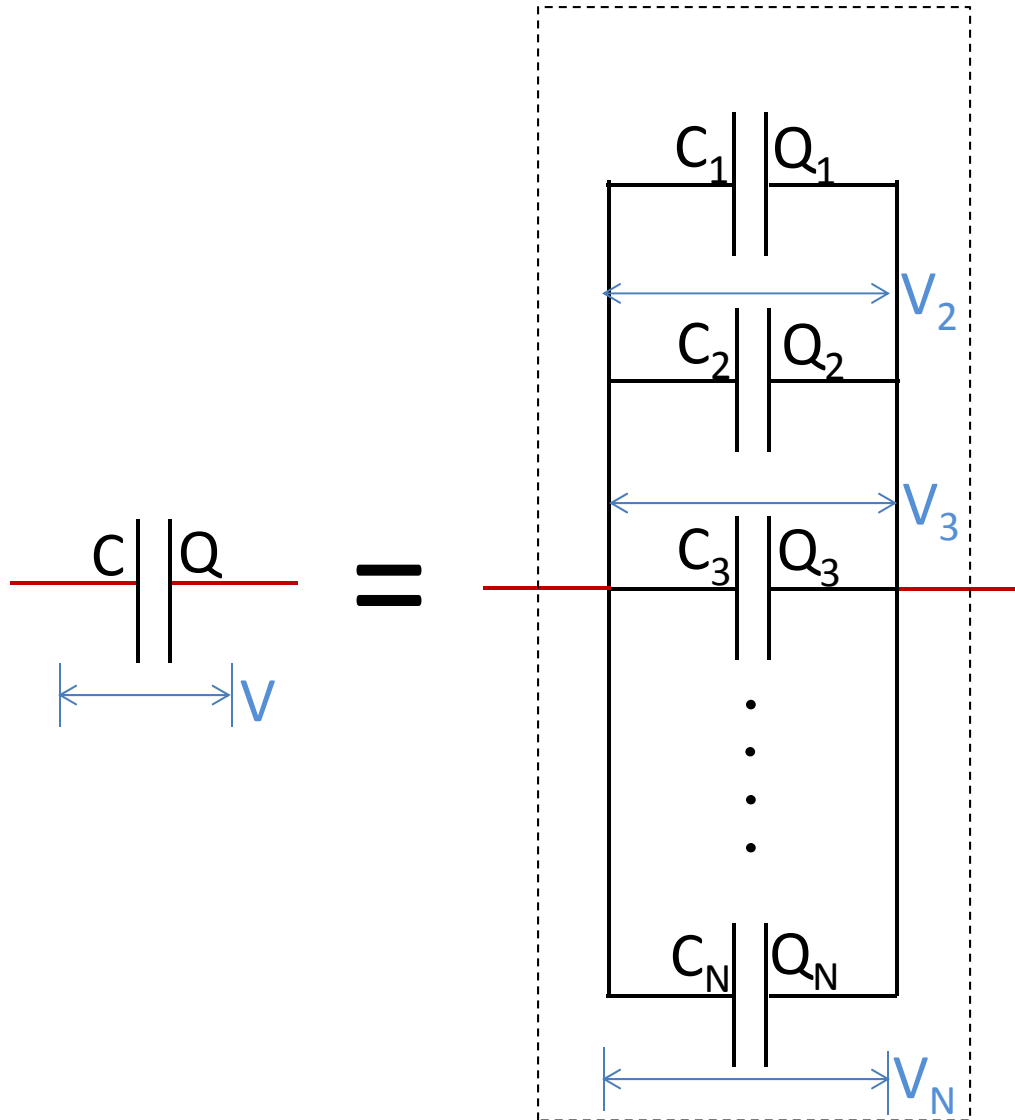

$$C = C_1 + C_2 + C_3 + \dots + C_N$$

$$Q = Q_1 + Q_2 + Q_3 + \dots + Q_N$$

$$V = V_1 = V_2 = V_3 = \dots = V_N$$


1. Potential difference across each individual capacitor is the same: (why?)

$$V = V_1 = V_2 = V_3 = \dots = V_N$$

$$\Rightarrow \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{Q_3}{C_3} = \dots = \frac{Q_N}{C_N}$$

2. Charge stored in each individual capacitor should be different (unless they have the same capacitance).

# Connecting Capacitors in Series

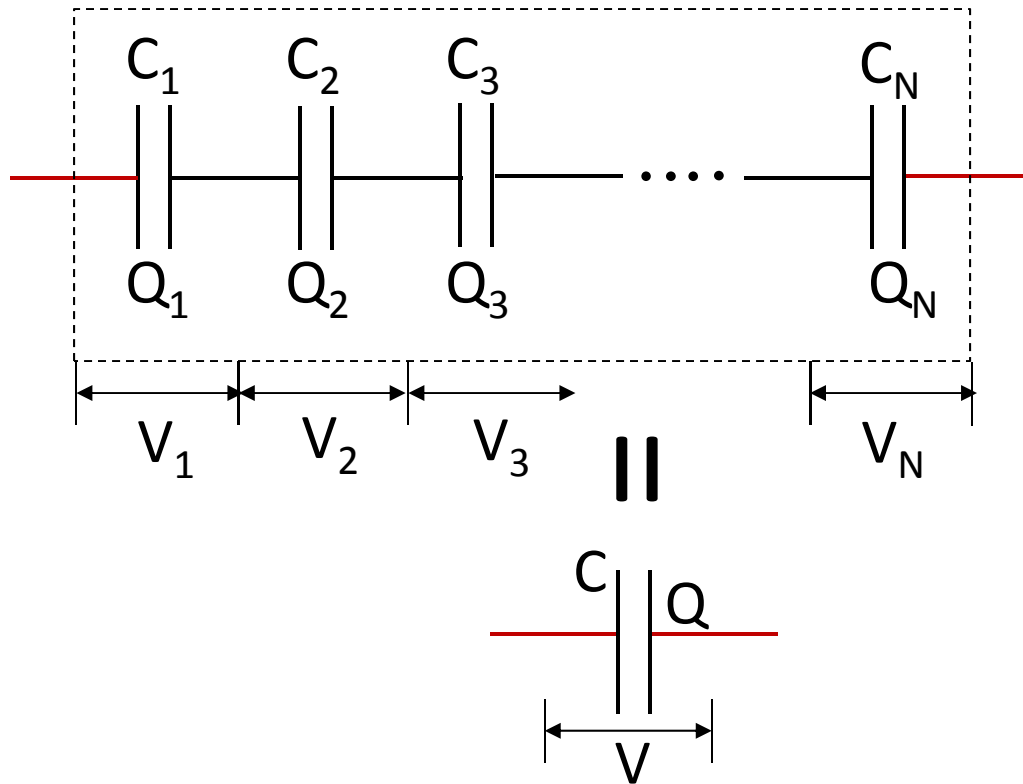

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

$$Q = Q_1 = Q_2 = Q_3 = \dots = Q_N$$

$$V = V_1 + V_2 + V_3 + \dots + V_N$$

1. Charge stored in each individual capacitor is the same: (why?)

$$Q = Q_1 = Q_2 = Q_3 = \dots = Q_N$$

$$\Rightarrow CV = C_1 V_1 = C_2 V_2 = C_3 V_3 = \dots = C_N V_N$$

2. Potential difference across each individual capacitor should be different (unless they have the same capacitance).