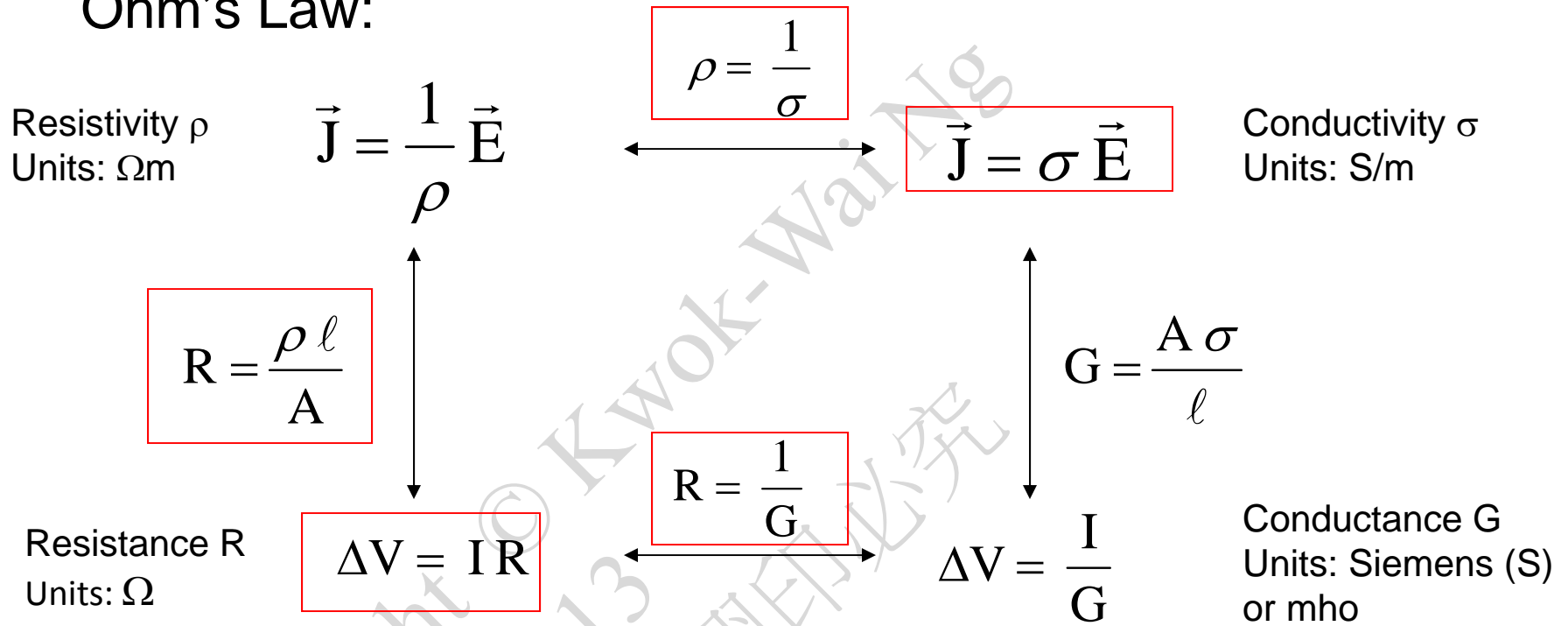


Resistance

Resistance, Conductance, Resistivity, and Conductivity

Ohm's Law:




1. Resistivity and conductivity depend on the materials only, Resistance and conductance depend on both the materials and also the geometry of the conductor.
2. Ohm's Law: $\Delta V = IR$ or $J = \sigma E$
3. $R = \frac{\rho \ell}{A}$
4. $\rho = \frac{1}{\sigma}$ and $R = \frac{1}{G}$

Power

Power dissipated
in resistance R:


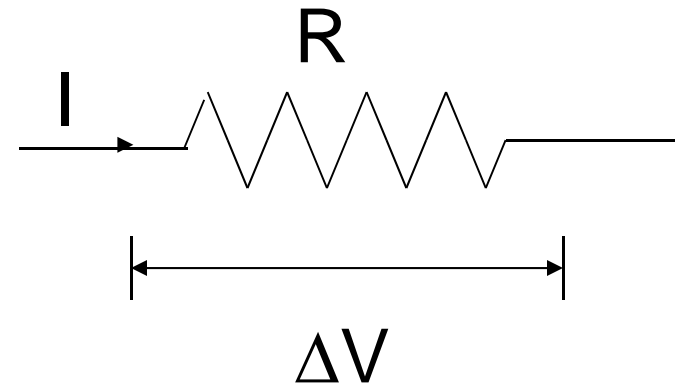
$$P = I\Delta V = I^2R = \frac{\Delta V^2}{R}$$



Units of power:
Watt (W) \equiv J/s

Class 21: Resistors in series and parallel

Connecting Resistors in Series

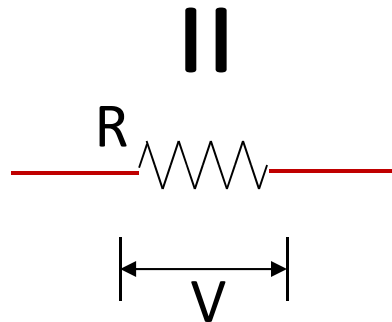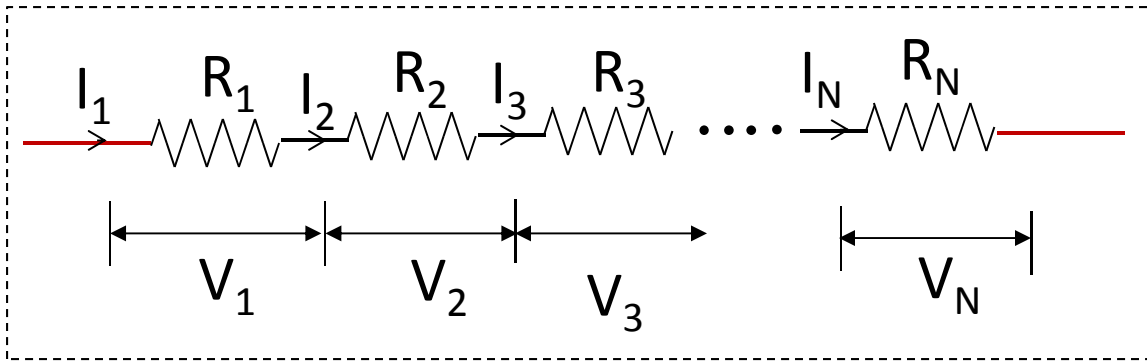

$$R_{\text{eff}} = R_1 + R_2 + R_3 + \dots + R_N$$

$$I = I_1 = I_2 = I_3 = \dots = I_N$$


$$V = V_1 + V_2 + V_3 + \dots + V_N$$

1. Current through each individual resistor is the same: (why?)

$$I = I_1 = I_2 = I_3 = \dots = I_N$$
$$\Rightarrow \frac{V}{R} = \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_3}{R_3} = \dots = \frac{V_N}{R_N}$$

2. Potential difference across each individual resistor should be different (unless they have the same resistance).

Connecting Resistors in Parallel

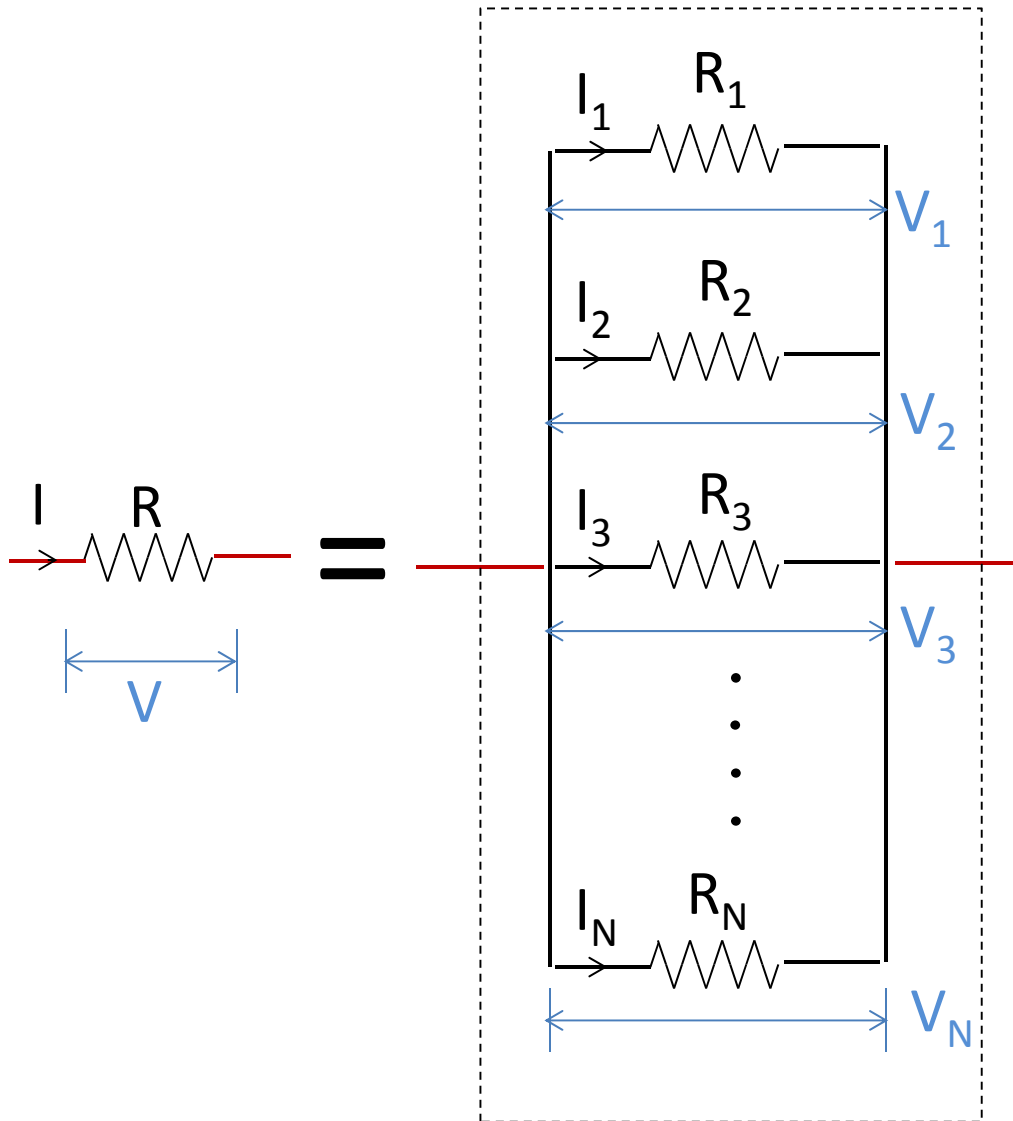

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

$$I = I_1 + I_2 + I_3 + \dots + I_N$$

$$V = V_1 = V_2 = V_3 = \dots = V_N$$

1. Potential difference across each individual resistor is the same: (why?)

$$V = V_1 = V_2 = V_3 = \dots = V_N$$

$$\Rightarrow I_1 R_1 = I_2 R_2 = I_3 R_3 = \dots = I_N R_N$$

2. Current through each individual resistor should be different (unless they have the same resistance).

Why so similar, but yet so opposite?

The formula for capacitors and resistors in parallel and series are oppositely switched:

	Resistors	Capacitors
In series	$R_{\text{eff}} = R_1 + R_2 + \dots R_N$	$\frac{1}{C_{\text{eff}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \frac{1}{C_N}$
In parallel	$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \frac{1}{R_N}$	$C_{\text{eff}} = C_1 + C_2 + \dots C_N$

$$R = \frac{V}{I} \quad \leftarrow$$

$$C = \frac{Q}{V} \quad \leftarrow$$

The formula will look the same if we use conductance $G=I / V$ instead of R .