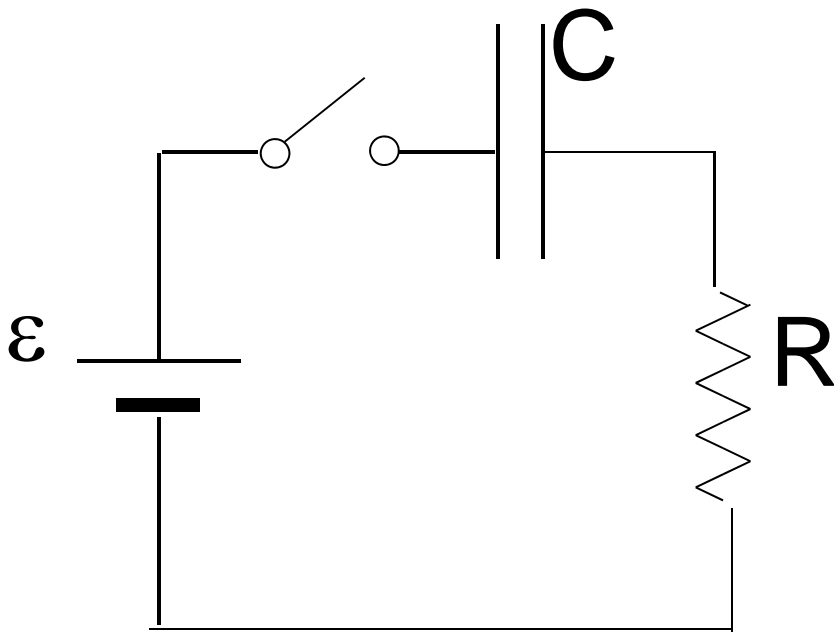


# RC Circuits

# RC Circuits – Charging




At  $t=0$ , capacitance is uncharged and  $Q=0$  (initial condition).

At  $t=0$ , switch is closed, the capacitor has no charge, it behaves like a conductor and  $I=\epsilon/R$ .

After the capacitor is completely charged,  $Q=C \epsilon$ ,  $\Delta V_C = \epsilon$  and  $\Delta V_R = 0$ .  $I=0$  and the capacitors behave like an insulator.

# RC Circuits – Charging

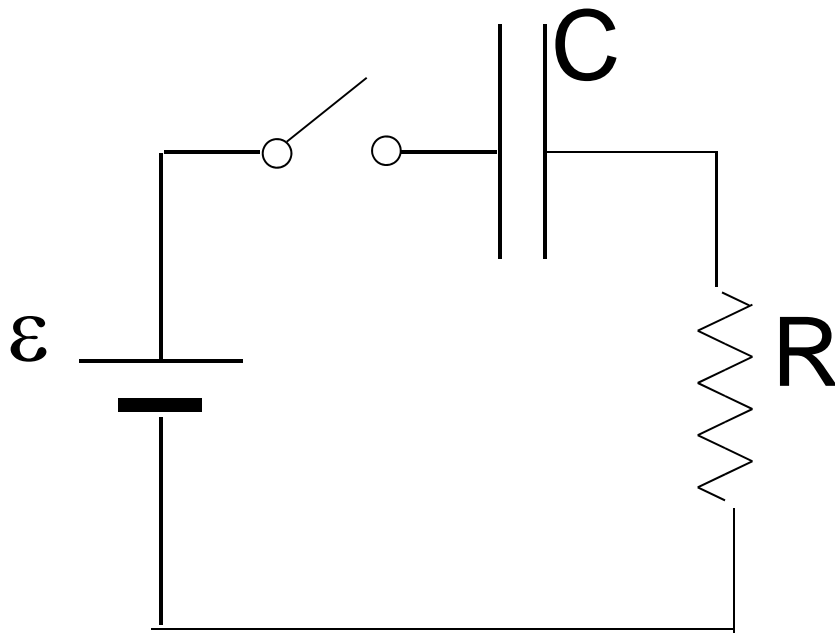

$$\varepsilon = \frac{q}{C} + IR \Rightarrow \frac{q}{C} + R \frac{dq}{dt} = \varepsilon$$

$$\Rightarrow CR dq = (C\varepsilon - q) dt$$

$$\Rightarrow \frac{dq}{q - C\varepsilon} = -\frac{1}{CR} dt \quad \text{Integration constant}$$

$$\Rightarrow \ln(q - C\varepsilon) = -\frac{t}{CR} + K'$$

$$\Rightarrow q - C\varepsilon = Ke^{-\frac{t}{CR}} \quad (K = e^{K'})$$

$$\Rightarrow q = C\varepsilon + Ke^{-\frac{t}{CR}}$$

$$\text{At } t = 0, q = 0 \Rightarrow 0 = C\varepsilon + K \Rightarrow K = -C\varepsilon$$

$$\therefore q = \underline{\underline{C\varepsilon(1 - e^{-\frac{t}{CR}})}}$$

$$I = \frac{dq}{dt} = \frac{C\varepsilon}{CR} e^{-\frac{t}{CR}} = \underline{\underline{\frac{\varepsilon}{R} e^{-\frac{t}{CR}}}}$$


$$\Delta V_R = IR = \underline{\underline{\varepsilon e^{-\frac{t}{CR}}}}$$

$$\Delta V_C = \frac{q}{C} = \underline{\underline{\varepsilon(1 - e^{-\frac{t}{CR}})}}$$

$$\left. \begin{array}{l} \leftarrow \\ \leftarrow \end{array} \right\} \Delta V_R + \Delta V_C = \varepsilon$$
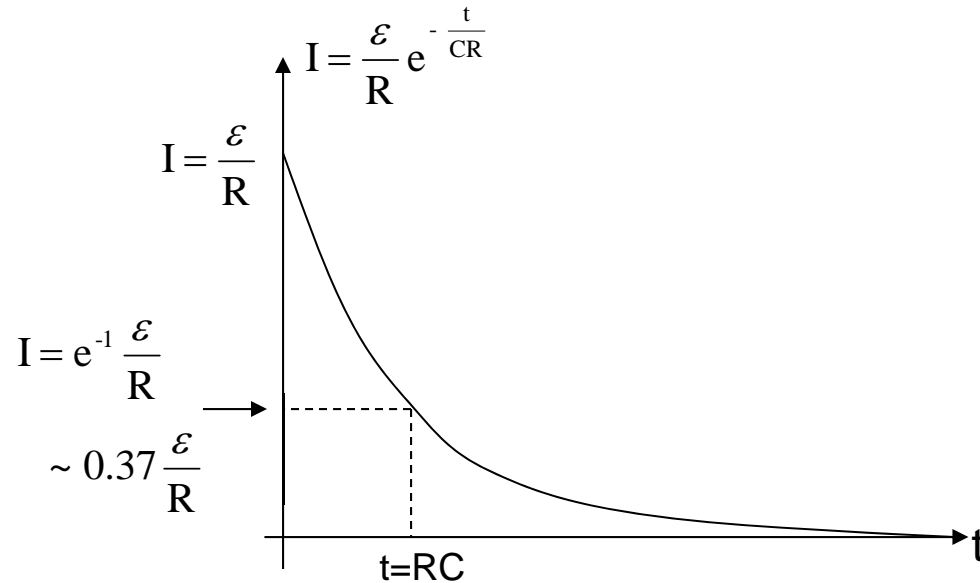
# RC time constant

$\tau=RC$  is known as the RC time constant. It indicates the response time (how fast you can charge up the capacitor) of the RC circuit.




$$e \approx 2.72$$

$$e^{-1} \approx 0.37$$


$$\sqrt{2} \approx 1.414$$

$$\frac{1}{\sqrt{2}} \approx 0.707$$

Nothing to do with RC circuits

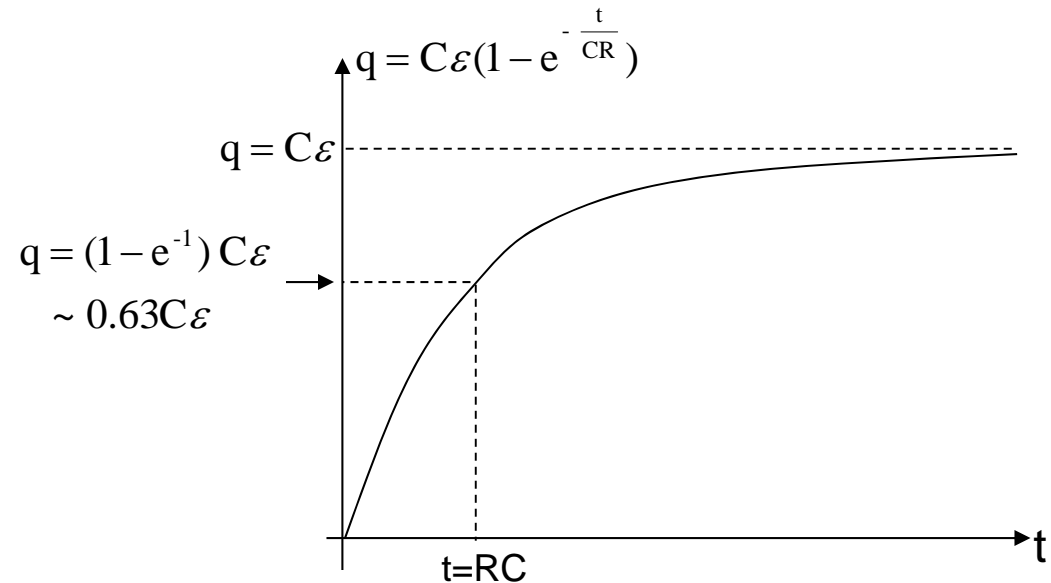

# RC Circuits – Discharging

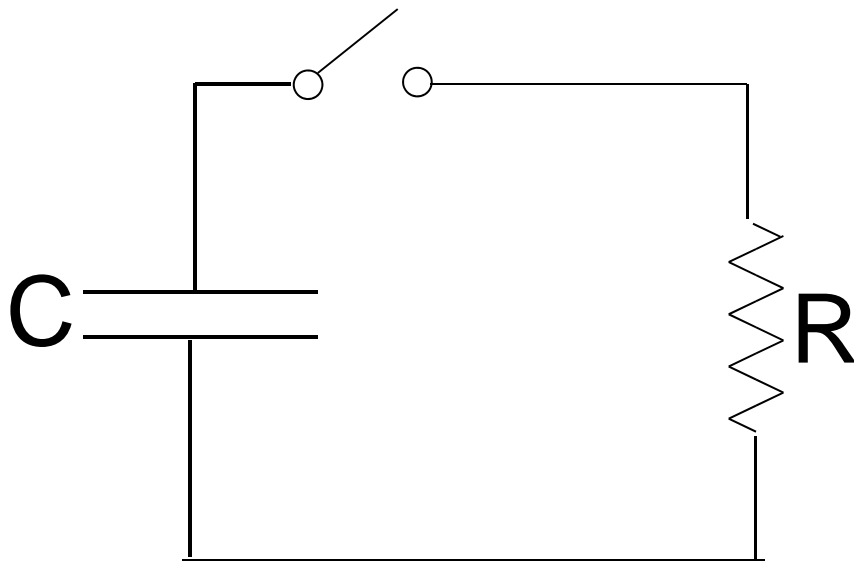


At  $t=0$ , capacitance is charged with a charge  $Q$  (initial condition).

At  $t=0$ , switch is closed, the capacitor starts to discharge.

After the capacitor is completely discharged,  $Q=0$ ,  $\Delta V_C=0$ ,  $\Delta V_R=0$  and  $I=0$ .

# RC Circuits – Discharging

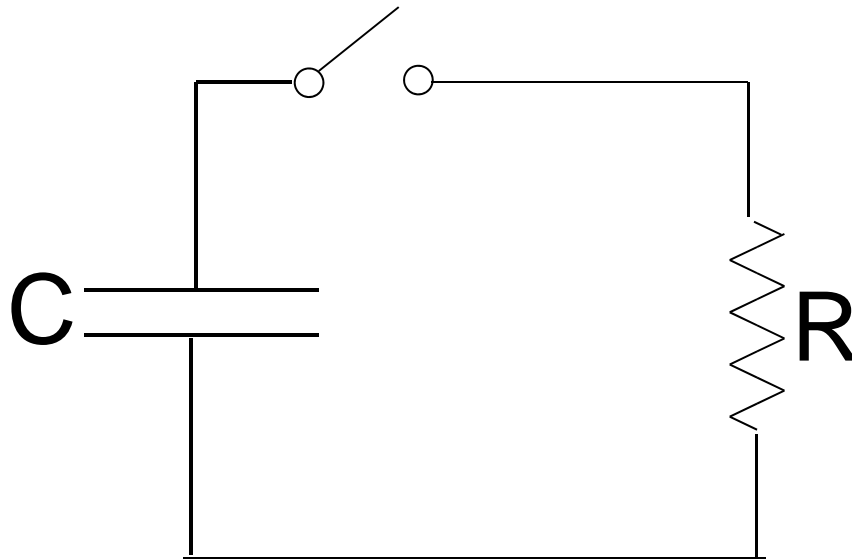

$$0 = \frac{q}{C} - IR \Rightarrow \frac{q}{C} + R \frac{dq}{dt} = 0 \quad \left(I = -\frac{dq}{dt}\right)$$

$$\Rightarrow CR \, dq = -q \, dt$$

$$\Rightarrow \frac{dq}{q} = -\frac{1}{CR} \, dt$$

Integration constant

$$\Rightarrow \ln q = -\frac{t}{CR} + K'$$

$$\Rightarrow q = K e^{-\frac{t}{CR}} \quad (K = e^{K'})$$

$$\Rightarrow q = K e^{-\frac{t}{CR}}$$

$$\text{At } t = 0, q = Q \Rightarrow Q = K$$

$$\therefore q = \underline{\underline{Q e^{-\frac{t}{CR}}}}$$

$$I = \frac{dq}{dt} = -\underline{\underline{\frac{Q}{RC} e^{-\frac{t}{CR}}}}$$


$$\Delta V_R = IR = -\underline{\underline{\frac{Q}{C} e^{-\frac{t}{CR}}}}$$

$$\Delta V_C = \frac{q}{C} = \underline{\underline{\frac{Q}{C} e^{-\frac{t}{CR}}}}$$

$$\left. \begin{array}{l} \leftarrow \\ \leftarrow \end{array} \right\} \Delta V_R + \Delta V_C = 0$$

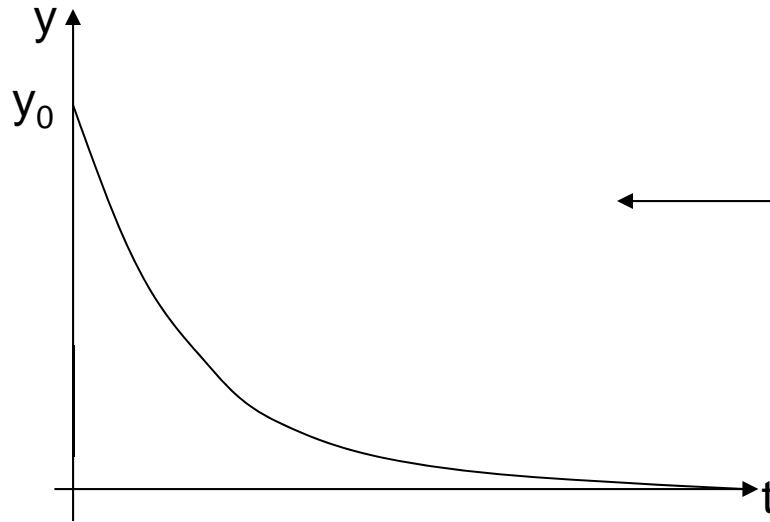
# In Summary

For both charge and discharge,  $Q$ ,  $I$ ,  $\Delta V_C$ , and  $\Delta V_R$  must be one of the following two cases:



$$y = y_0 e^{-\frac{t}{RC}}$$
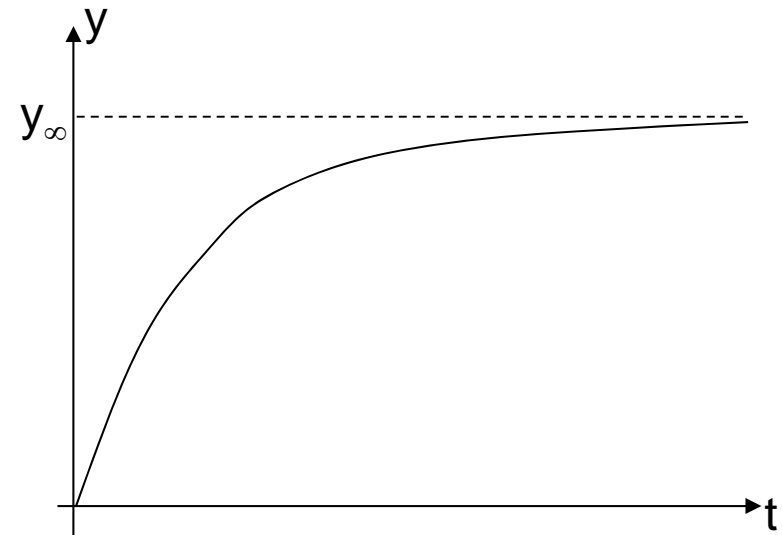
$$y = y_{\infty} (1 - e^{-\frac{t}{RC}})$$




$y$  can be  $Q$ ,  $I$ ,  $\Delta V_C$ , or  $\Delta V_R$

## Class 26: Magnetic force acting on a moving point charge



# Magnetic Field

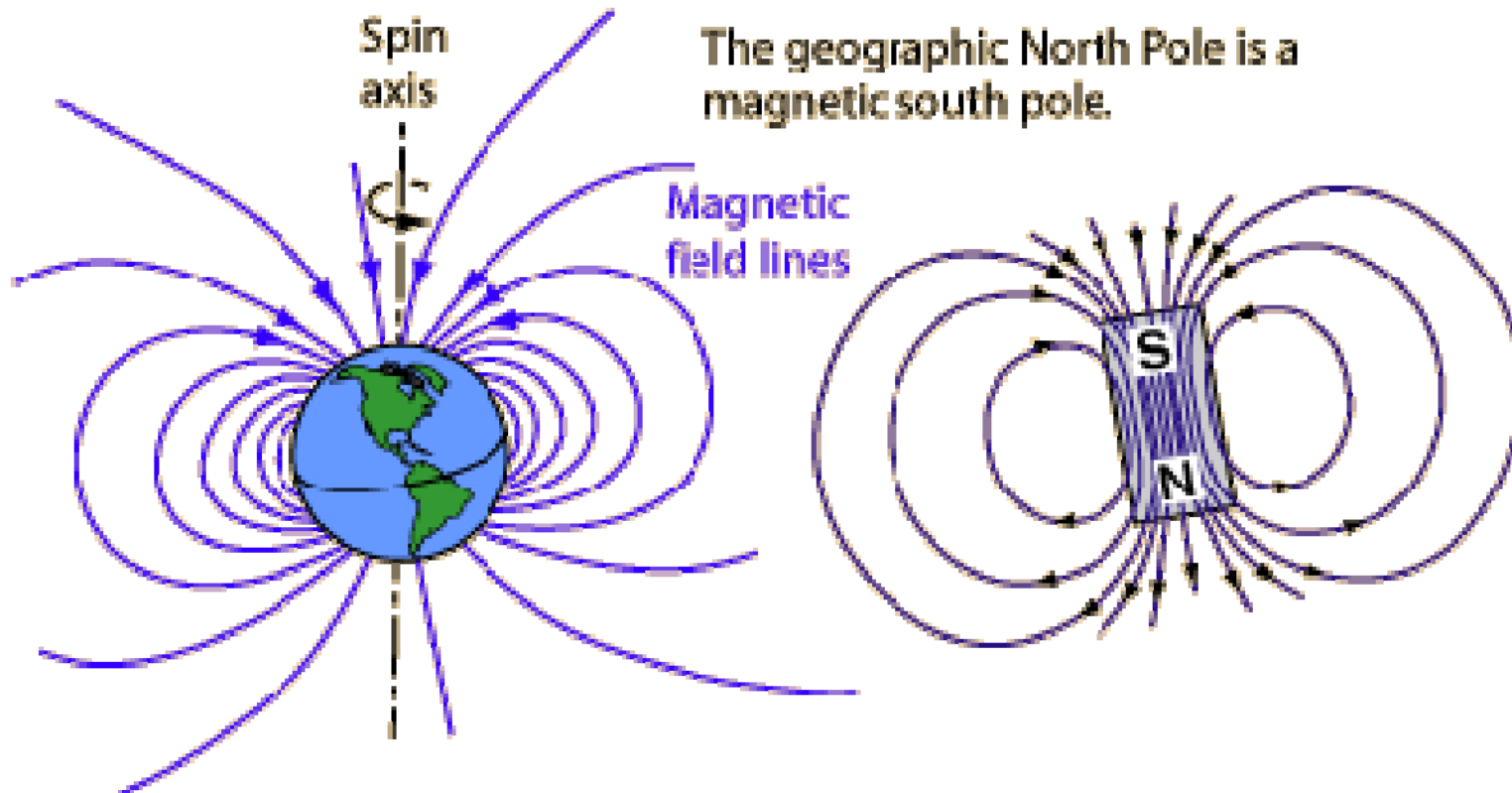


1. All single magnets have two poles, N and S.
2. Externally, magnetic field lines come out from the N pole and getting into the S pole.
3. Between two magnets, like poles repel and unlike poles attract.
4. The geographical north pole of earth is actually the S pole of a bar magnet.
5. We will explain why there is magnetic field later.

From class 3

# cross product between two vectors



Direction:

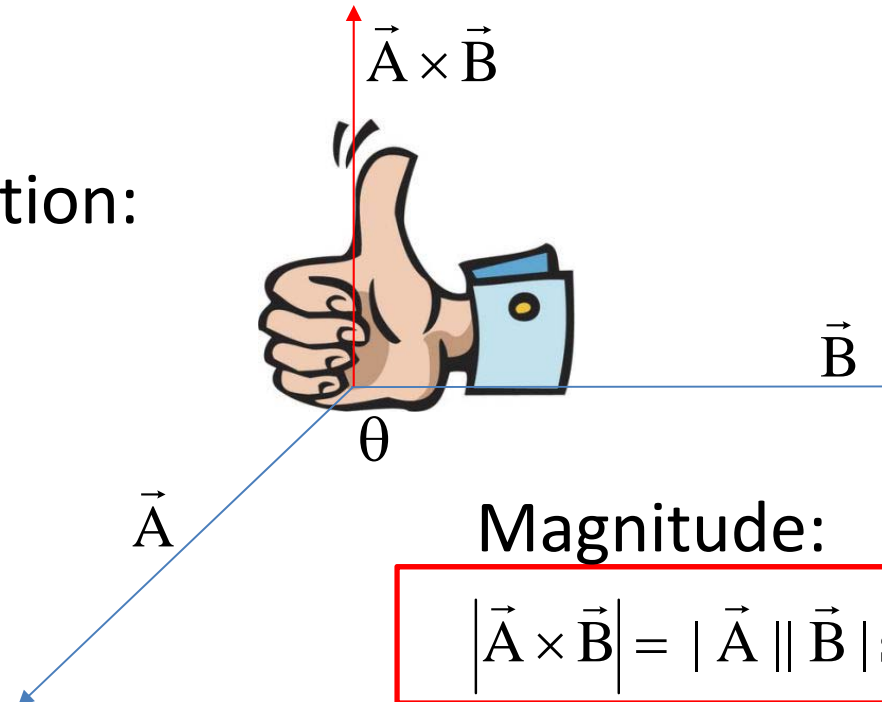

Magnitude:

$$|\vec{A} \times \vec{B}| = |\vec{A}| |\vec{B}| \sin \theta$$

$$\vec{A} \times \vec{B} = \begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ A_x & A_y & A_z \\ B_x & B_y & B_z \end{vmatrix} = \hat{i} \begin{vmatrix} A_y & A_z \\ B_y & B_z \end{vmatrix} - \hat{j} \begin{vmatrix} A_x & A_z \\ B_x & B_z \end{vmatrix} + \hat{k} \begin{vmatrix} A_x & A_y \\ B_x & B_y \end{vmatrix}$$

$$\begin{vmatrix} a & b \\ c & d \end{vmatrix} = ad - bc$$

## A common symbol



or



A vector perpendicular and pointing into the screen /paper.




or



A vector perpendicular and pointing out of the screen /paper.
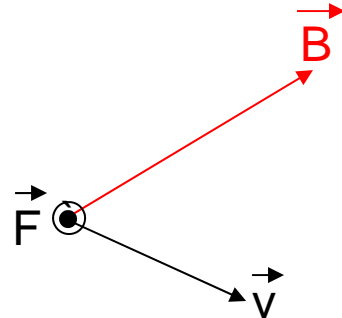
# Magnetic Force Acting on a Moving Charge

When a charge particle moves in a magnetic field  $\vec{B}$ , there will be magnetic force acting on the particle:



$$\vec{F}_B = q \vec{v} \times \vec{B}$$

1. Unit of magnetic field is Tesla (T).
2. If there is magnetic field, only under two conditions the magnetic force on the charge particle will be zero: (i) the particle is not moving ( $v=0$ ), or (ii) it is moving in parallel or antiparallel to the magnetic field ( $\sin\theta=0$ ).
3. The magnetic force is always perpendicular to the magnetic field and the velocity.
4. The magnetic force does no work because  $\vec{F}_B \cdot \vec{v} = 0$ .
5. If you want to determine the direction acting on a negative charge particle, treat it like a positive charge first, then reverse the force direction at the end.