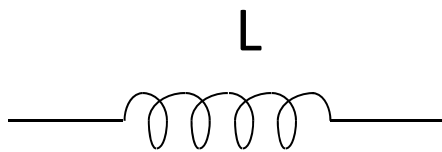


Energy stored in a magnetic field


Energy Stored in an Inductor



Energy stored in an inductor:

$$U = \frac{1}{2} LI^2$$


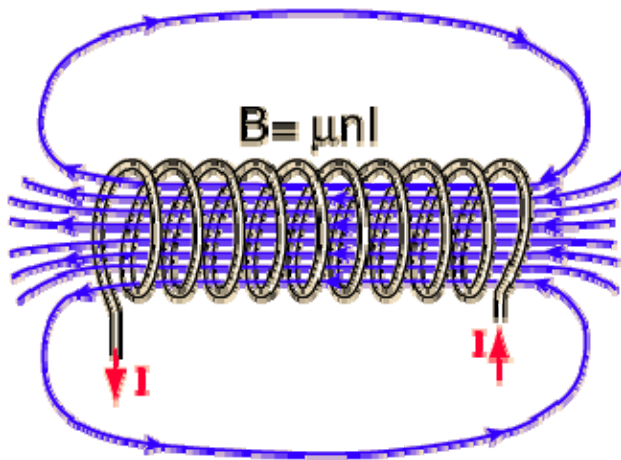
(Do not forget $\mathcal{E} = -L \frac{dI}{dt}$.)



Energy density stored in an electric field:

$$u_B = \frac{U_B}{\Omega} = \frac{1}{2\mu_0} B^2$$

Capacitor and Inductor

 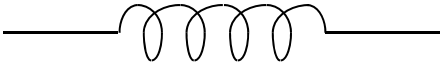
| Capacitor C | Inductor L |
|---|---|
|  |  |
| Charge Q | Current I |
| E field | B field |
| $V = \frac{Q}{C}$ | $\mathcal{E} = -L \frac{dI}{dt}$ |
| Parallel plate capacitor (uniform E field) $C = \frac{\epsilon_0 A}{d} \text{ and } E = \frac{V}{d}$ | Solenoid (uniform B field) $L = \mu_0 n N A \text{ and } B = \mu_0 n I$ |
| $U_E = \frac{1}{2} C V^2 \text{ and } u_E = \frac{1}{2} \epsilon_0 E^2$ | $U_B = \frac{1}{2} L I^2 \text{ and } u_B = \frac{1}{2 \mu_0} B^2$ |

Class 40 RL Circuits

From Class 25

RC Circuits – Charging

↑
Charge

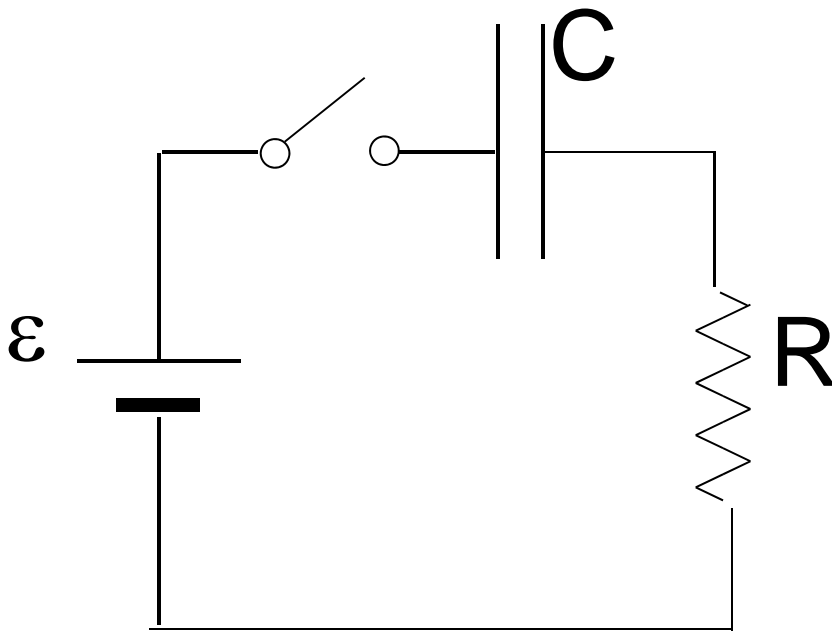


At $t=0$, capacitance is uncharged and $Q=0$ (initial condition).

At $t=0$, switch is closed, if the capacitor has no charge, it behaves like a conductor and $I=\varepsilon/R$.

After the capacitor is completely charged, $Q=C \varepsilon$, $\Delta V_C = \varepsilon$ and $\Delta V_R = 0$. $I=0$ and the capacitors behave like an insulator.

RL Circuits – Charging

↑
Current

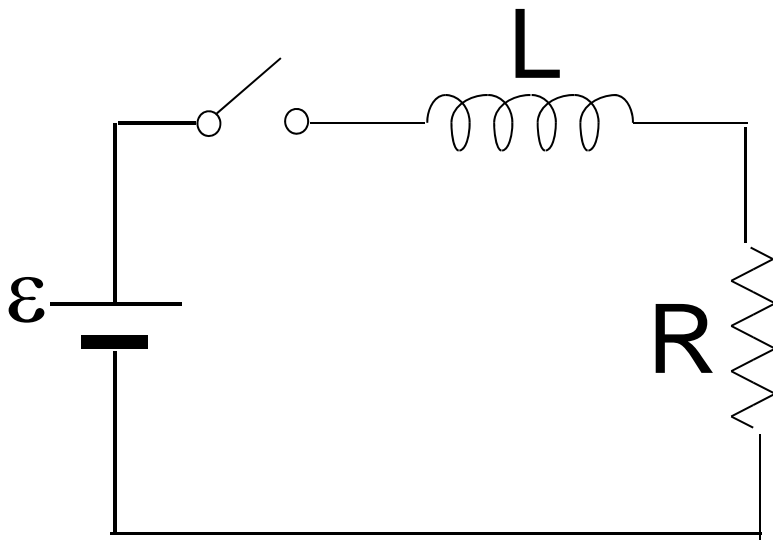

At $t=0$, inductor is uncharged and $I=0$ (initial condition).


At $t=0$, switch is closed, if the inductor has no current, it behaves like an insulator (opposes changes) and $I=0$.

After the inductor is completely charged (with current), $I=\epsilon/R$, $\Delta V_L=0$ and $\Delta V_R=\epsilon$. The inductor behaves like a conductor.

From Class 25

RC Circuits – Charging

← Charge

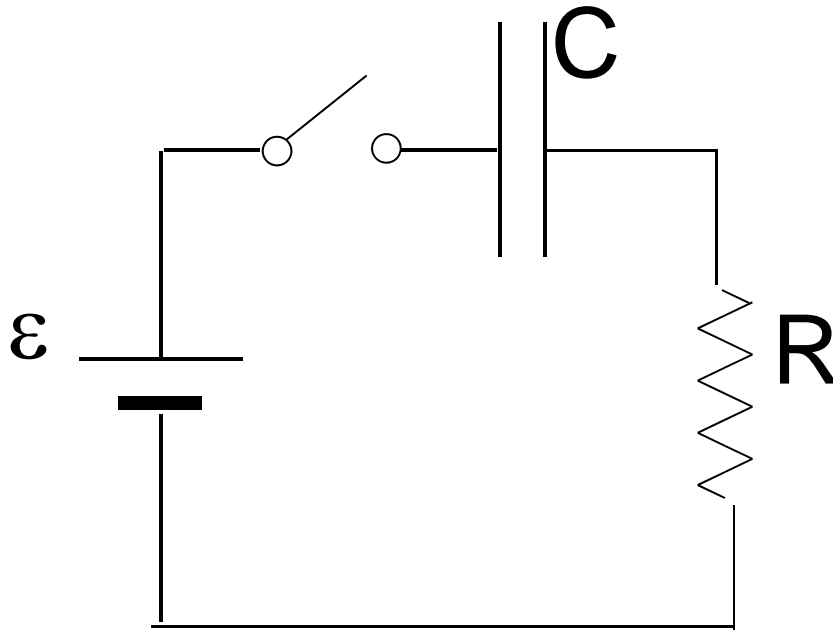

$$\varepsilon = \frac{q}{C} + IR \Rightarrow \frac{q}{C} + R \frac{dq}{dt} = \varepsilon$$

$$\Rightarrow CR dq = (C\varepsilon - q) dt$$

$$\Rightarrow \frac{dq}{q - C\varepsilon} = -\frac{1}{CR} dt \quad \text{Integration constant}$$

$$\Rightarrow \ln(q - C\varepsilon) = -\frac{t}{CR} + K'$$

$$\Rightarrow q - C\varepsilon = Ke^{-\frac{t}{CR}} \quad (K = e^{K'})$$

$$\Rightarrow q = C\varepsilon + Ke^{-\frac{t}{CR}}$$

$$\text{At } t = 0, q = 0 \Rightarrow 0 = C\varepsilon + K \Rightarrow K = -C\varepsilon$$

$$\therefore \underline{\underline{q = C\varepsilon(1 - e^{-\frac{t}{CR}})}}$$

$$I = \frac{dq}{dt} = \frac{C\varepsilon}{CR} e^{-\frac{t}{CR}} = \underline{\underline{\frac{\varepsilon}{R} e^{-\frac{t}{CR}}}}$$


$$\Delta V_R = IR = \underline{\underline{\varepsilon e^{-\frac{t}{CR}}}}$$

$$\Delta V_C = \frac{q}{C} = \underline{\underline{\varepsilon(1 - e^{-\frac{t}{CR}})}}$$

$$\left\{ \begin{array}{l} \Delta V_R + \Delta V_C = \varepsilon \end{array} \right.$$

RL Circuits – Charging

← Current

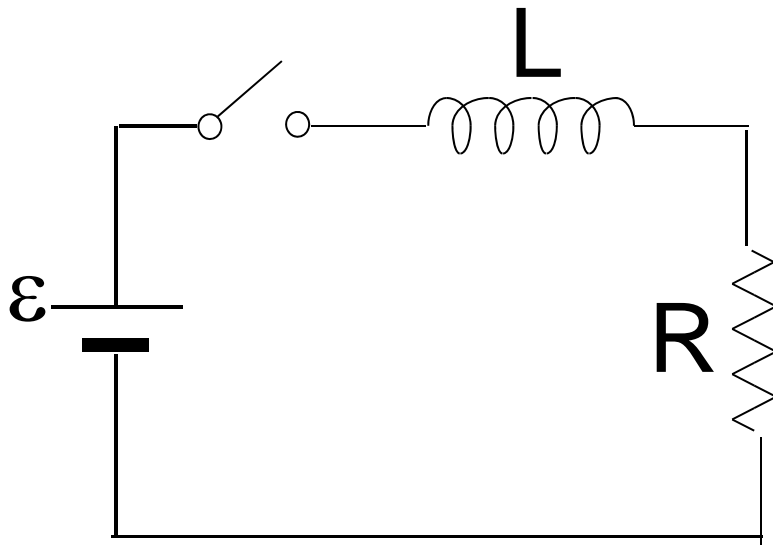

$$\varepsilon = L \frac{dI}{dt} + IR \Rightarrow L dI + I R dt = \varepsilon dt$$

$$\Rightarrow L dI = (\varepsilon - IR)dt$$

$$\Rightarrow \frac{L dI}{\varepsilon - IR} = dt$$

Integration constant

$$\Rightarrow \frac{L}{R} \ln(\varepsilon - IR) = t + K'$$

$$\Rightarrow \ln(\varepsilon - IR) = \frac{R}{L} t + \frac{R}{L} K'$$

$$\Rightarrow \varepsilon - IR = K e^{-\frac{R}{L} t} \quad (K = e^{\frac{R}{L} K'})$$

$$\Rightarrow IR = \varepsilon - K e^{-\frac{R}{L} t}$$

$$\text{At } t = 0, I = 0 \Rightarrow 0 = \varepsilon - K \Rightarrow K = \varepsilon$$

$$\therefore IR = \varepsilon(1 - e^{-\frac{R}{L} t}) \Rightarrow \underline{\underline{I = \frac{\varepsilon}{R}(1 - e^{-\frac{R}{L} t})}}$$


$$\Delta V_R = IR = \underline{\underline{\varepsilon(1 - e^{-\frac{R}{L} t})}}$$

$$\Delta V_L = L \frac{dI}{dt} = \underline{\underline{\varepsilon e^{-\frac{R}{L} t}}}$$

$$\left\{ \begin{array}{l} \leftarrow \\ \rightarrow \end{array} \right. \Delta V_R + \Delta V_L = \varepsilon$$

RC time constant

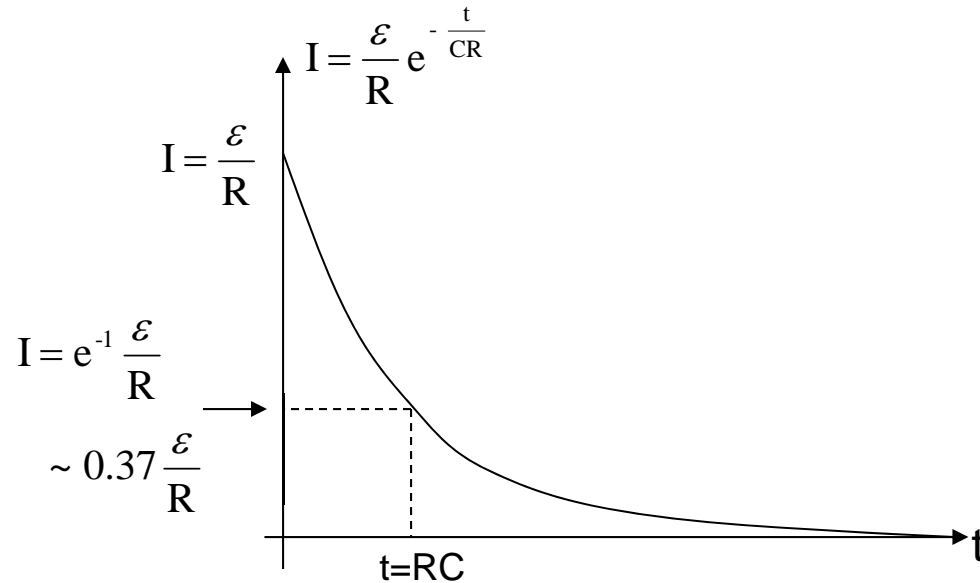$\tau = RC$ is known as the RC time constant. It indicates the response time (how fast you can charge up the capacitor) of the RC circuit.




$$e \approx 2.72$$

$$e^{-1} \approx 0.37$$

$$\sqrt{2} \approx 1.414$$


$$\frac{1}{\sqrt{2}} \approx 0.707$$

Nothing to do with RC circuits

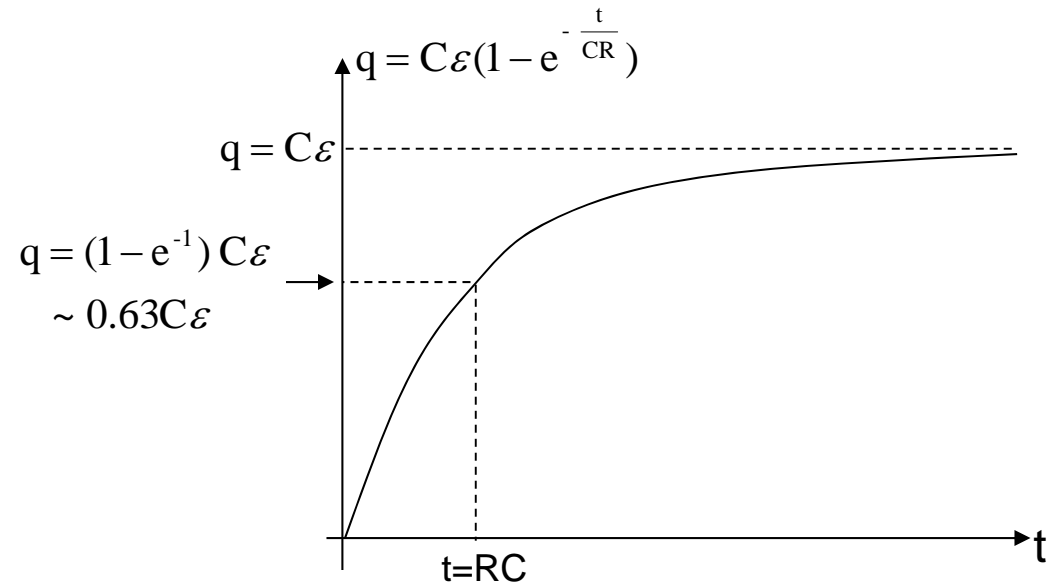

L/R time constant

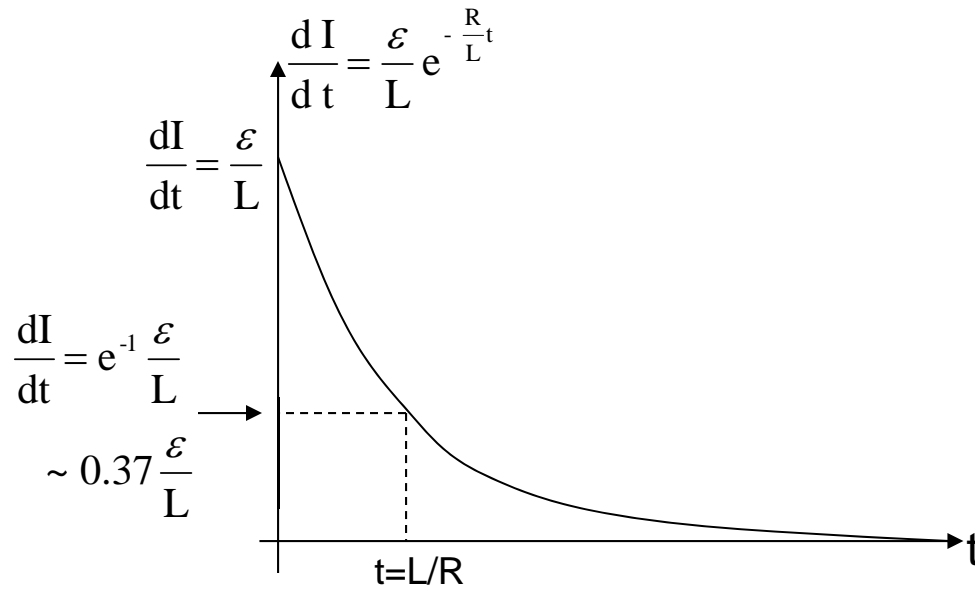$\tau = L/R$ is known as the time constant. It indicates the response time (how fast you can up a current) of the RC circuit.




$$e \approx 2.72$$

$$e^{-1} \approx 0.37$$

$$\sqrt{2} \approx 1.414$$


$$\frac{1}{\sqrt{2}} \approx 0.707$$

Nothing to do with RL circuits

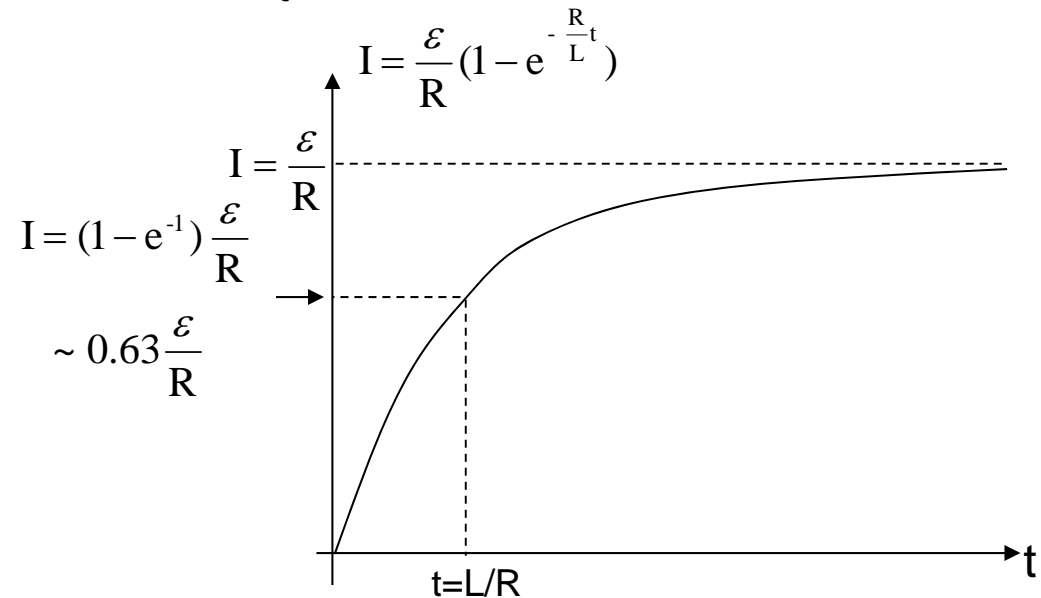

From Class 25

RC Circuits – Discharging ← Charge

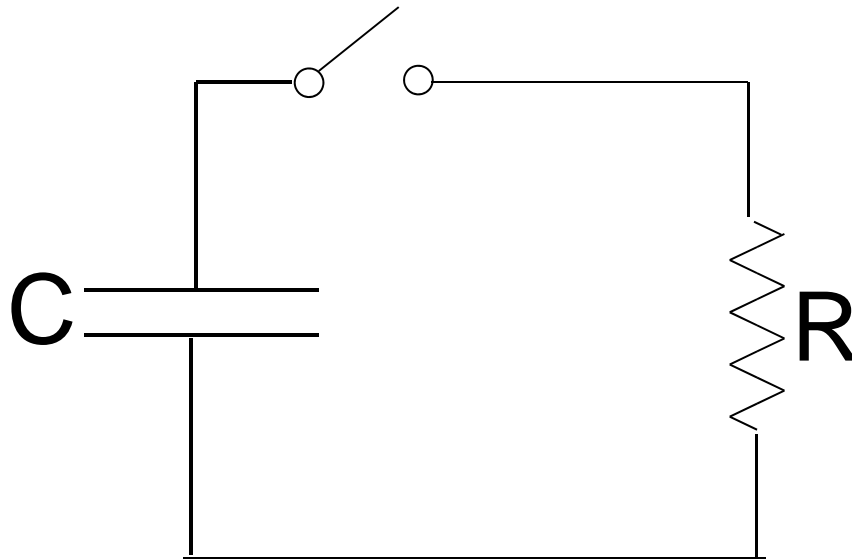

$$0 = \frac{q}{C} + IR \Rightarrow \frac{q}{C} + R \frac{dq}{dt} = 0$$

$$\Rightarrow CR \, dq = -q \, dt$$

$$\Rightarrow \frac{dq}{q} = -\frac{1}{CR} dt$$

Integration constant

$$\Rightarrow \ln q = -\frac{t}{CR} + K'$$

$$\Rightarrow q = Ke^{-\frac{t}{CR}} \quad (K = e^{K'})$$

$$\Rightarrow q = Ke^{-\frac{t}{CR}}$$

$$\text{At } t = 0, q = Q \Rightarrow Q = K$$

$$\therefore q = \underline{\underline{Qe^{-\frac{t}{CR}}}}$$

$$I = \frac{dq}{dt} = -\frac{Q}{RC} e^{-\frac{t}{CR}}$$

$$\Delta V_R = IR = -\frac{Q}{C} e^{-\frac{t}{CR}}$$

$$\Delta V_C = \frac{q}{C} = \frac{Q}{C} e^{-\frac{t}{CR}}$$

$$\left. \begin{array}{l} \leftarrow \\ \leftarrow \end{array} \right\} \Delta V_R + \Delta V_C = 0$$