


Name: _____

Sec: _____

PHY 232 Fall 2017 Class Work and Supplementary Work (Not to be collected)

Class 22. Resistors in series and parallel


Part 1.

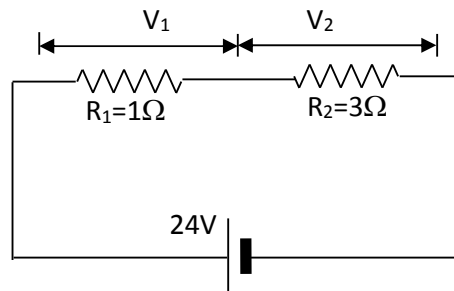

(a) What is the current through R_1 ? What is the current through R_2 ?

(b) What is the voltage V_1 across R_1 ? What is the voltage V_2 across R_2 ?

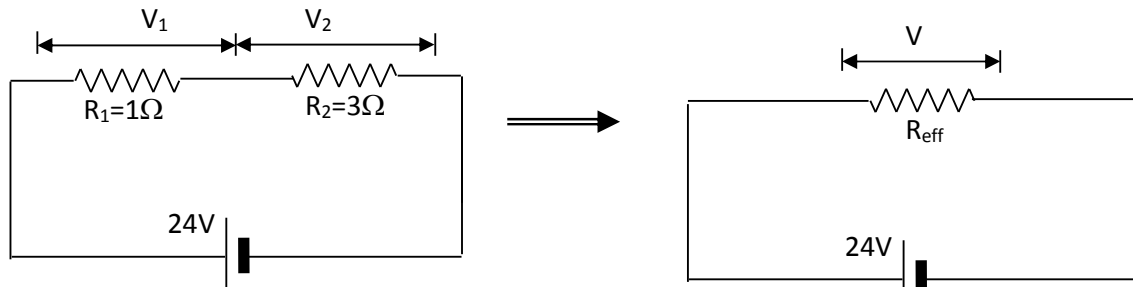(c) What is the power dissipated in R_1 ? What is the power dissipated in R_2 ?




(d) If the two resistors are replaced with one, what should be the effective resistance R_{eff} of the replacement?

(e) What is the current through R_{eff} ? How is this answer compared with that of part (a)?


(f) What is the voltage across R_{eff} ? How is this answer compared with that of part (b)?

(g) What is the power dissipated R_{eff} ? How is this answer compared with that of part (c)?

Part 2.

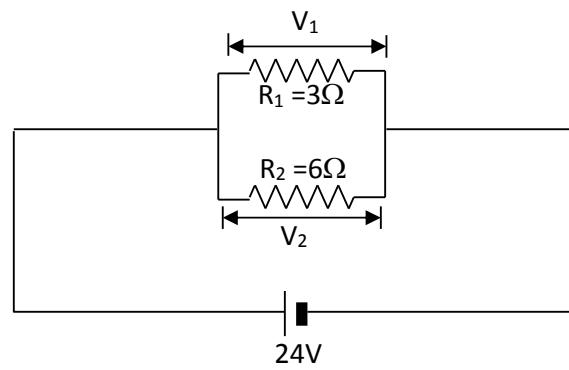

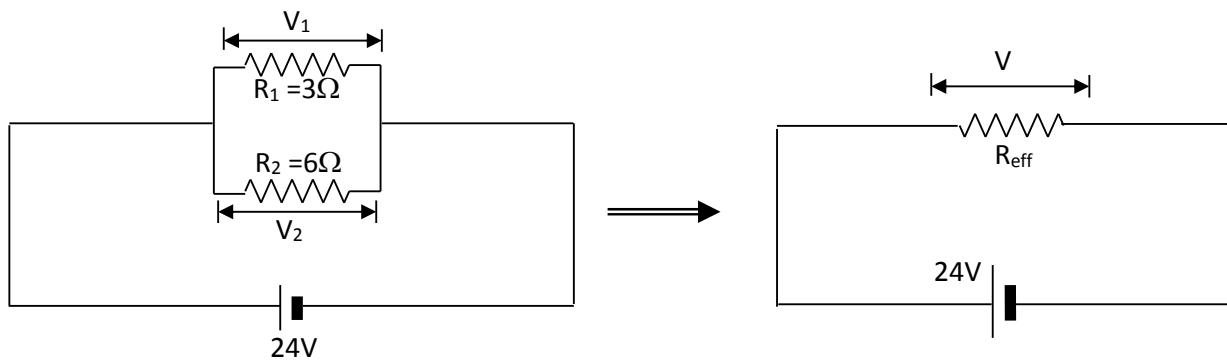- (a) What is the current through R_1 ? What is the current through R_2 ?
- (b) What is the voltage V_1 across R_1 ? What is the voltage V_2 across R_2 ?
- (c) What is the power dissipated in R_1 ? What is the power dissipated in R_2 ?




(d) If the two resistors are replaced with one, what should be the effective resistance R_{eff} of the replacement?

(e) What is the current through R_{eff} ? How is this answer compared with that of part (a)?

(f) What is the voltage across R_{eff} ? How is this answer compared with that of part (b)?

(g) What is the power dissipated R_{eff} ? How is this answer compared with that of part (c)?

Part 3.

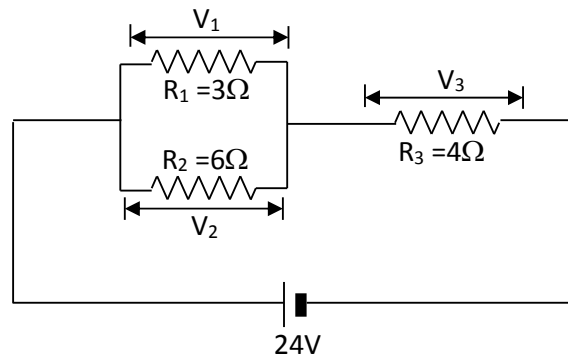

(a) What is the current through R_1 ? What is the current through R_2 ? What is the current through R_3 ?

(b) What is the voltage V_1 across R_1 ? What is the voltage V_2 across R_2 ? What is the voltage V_3 across R_3 ?

(c) What is the power dissipated R_1 ? What is the power dissipated R_2 ? What is the power dissipated R_3 ?