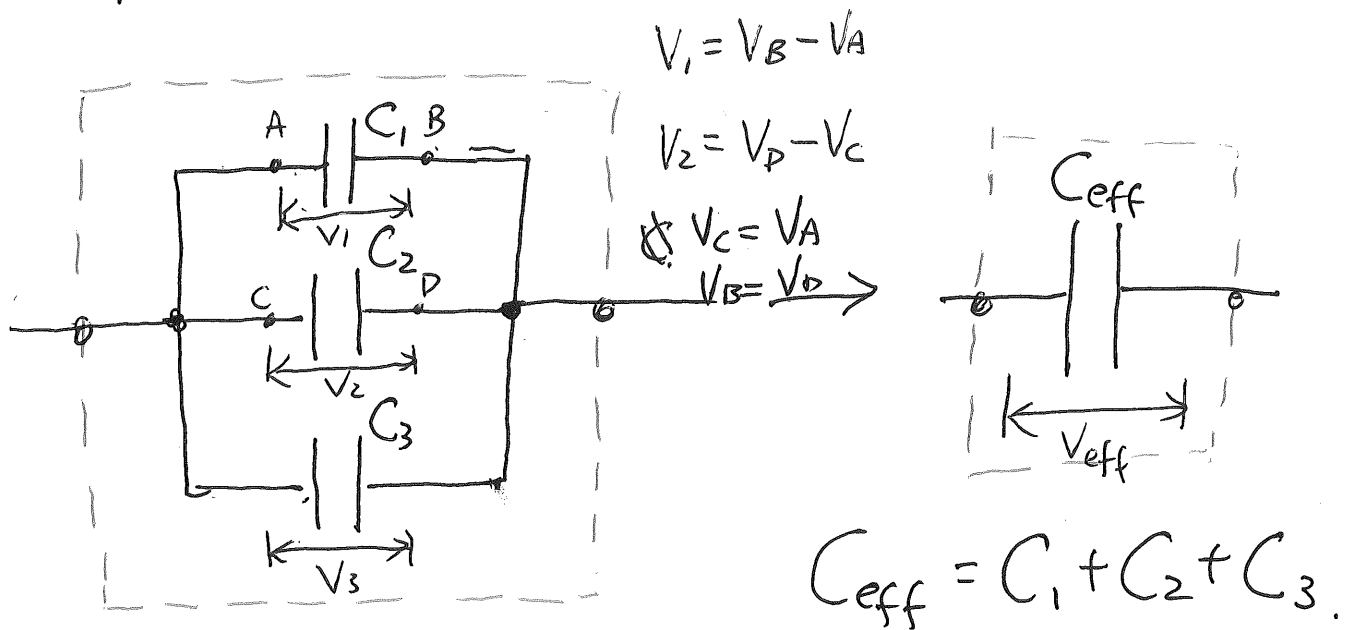


Capacitors in parallel.




$$\underline{V_1 = V_2 = V_3 = V_{eff}}$$

$$C = \frac{Q}{V} \Rightarrow Q = CV$$

$$Q_1 \neq Q_2 \neq Q_3 \neq Q_{eff} \text{ if } C_1 \neq C_2 \neq C_3 \neq C_{eff}$$

$$Q_{eff} = Q_1 + Q_2 + Q_3$$

Capacitors in series.

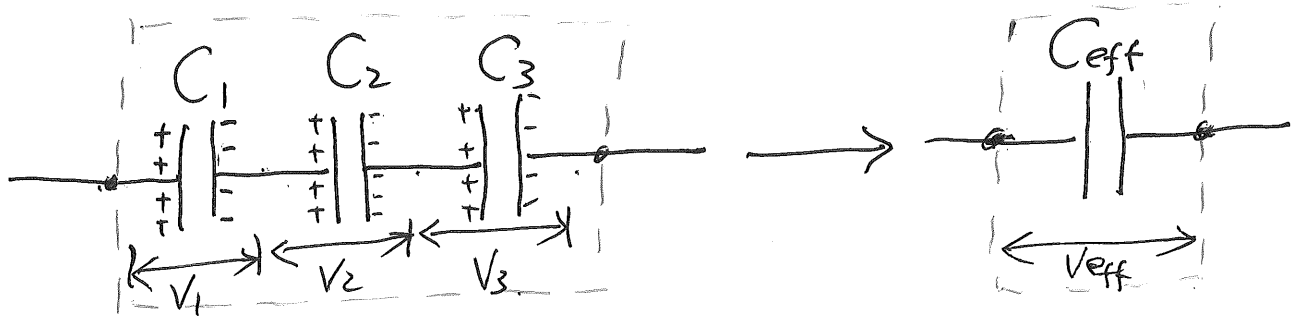

$$\frac{1}{C_{eff}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}.$$

$$Q_1 = Q_2 = Q_3 = Q_{eff} \leftarrow$$

$$C = \frac{Q}{V} \Rightarrow V = \frac{Q}{C}.$$


$$V_1 \neq V_2 \neq V_3 \neq V_{eff} \text{ if } C_1 \neq C_2 \neq C_3 \neq C_{eff}.$$

$$V_{eff} = V_1 + V_2 + V_3.$$

$$V = \frac{Q}{C}$$

$$= \frac{26.66}{3}$$

$$= 8.89V$$

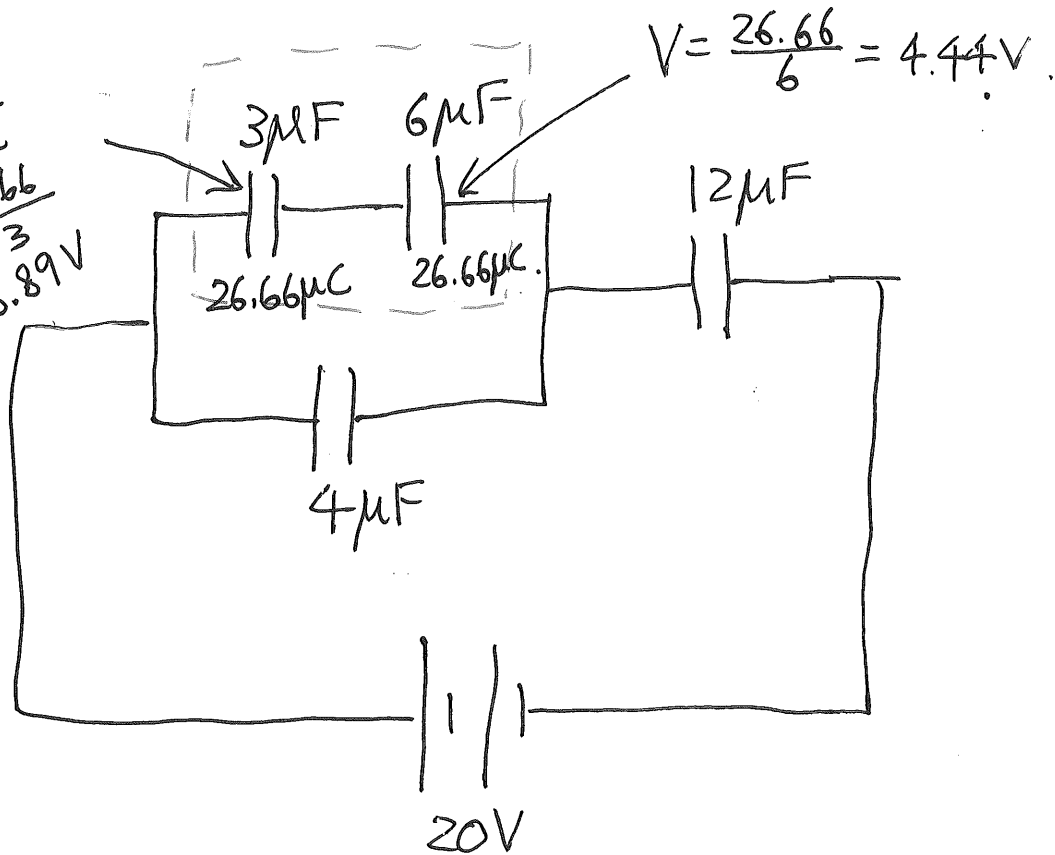


$$Q = 2\mu F \times 13.33$$

$$= 26.66\mu C$$


$$C_{eff1} = 2\mu F$$

$$\frac{1}{C_{eff1}} = \frac{1}{3} + \frac{1}{6} = \frac{1}{2}$$

$$\Rightarrow C_{eff1} = 2\mu F$$

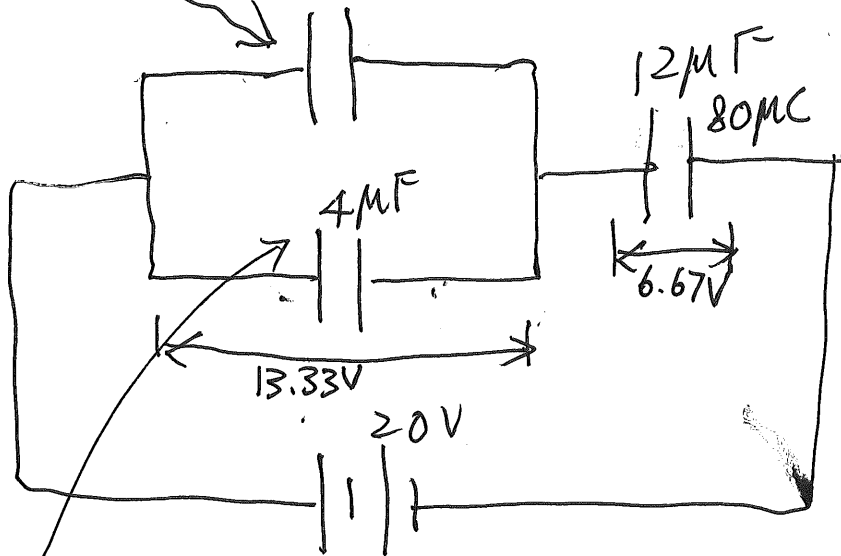

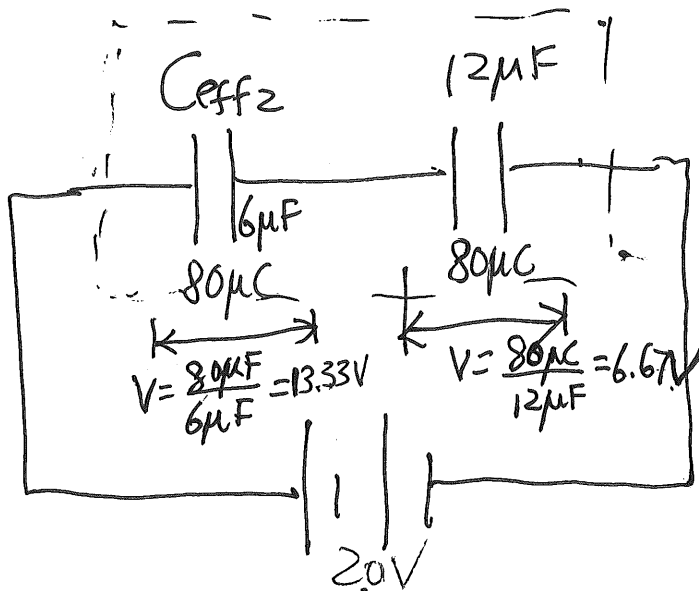
$$\downarrow C_{\text{eff}2} = 2 + 4 = 6\mu\text{F}$$





$$\downarrow \frac{1}{C_{\text{eff}3}} = \frac{1}{C_{\text{eff}2}} + \frac{1}{12}$$

$$= \frac{1}{6} + \frac{1}{12} = \frac{3}{12} \neq$$
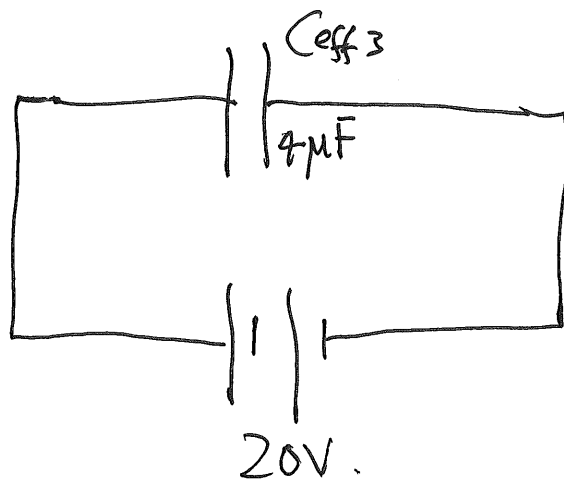
$$\therefore C_{\text{eff}3} = 4\mu\text{F}$$


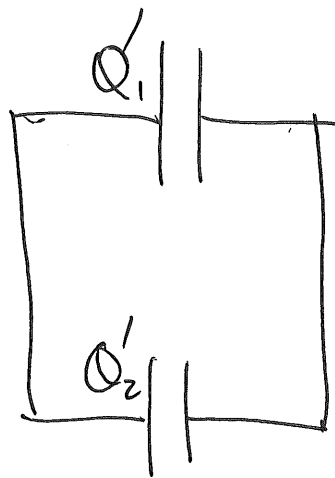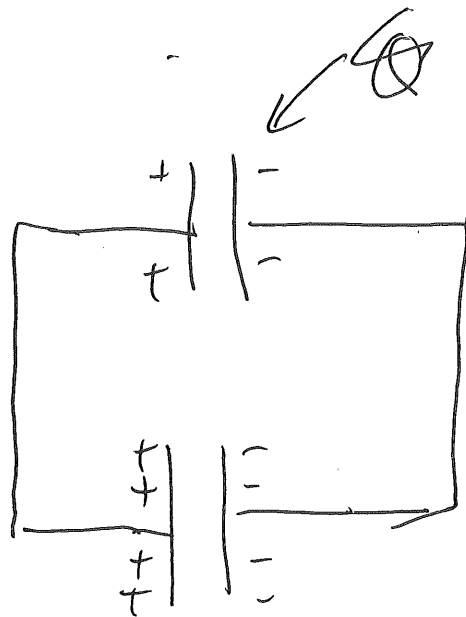
$$\cancel{Q} Q = CV = 4 \times 20 = 80\mu\text{C}.$$



$$Q_1 = (15 \mu F)(27)$$


$$Q_2 = (12 \mu F)(14).$$

$$Q_1' + Q_2' = (15 \mu F)(27) + (12 \mu F)(14) \quad \text{--- (1)}$$



$$C = \frac{Q}{V} \Rightarrow V = \frac{C}{Q}.$$

$$\frac{15 \mu F}{Q_1'} = \frac{12 \mu F}{Q_2'} \quad \text{--- (2)}$$

$$Q_1 = C_1 V_1$$

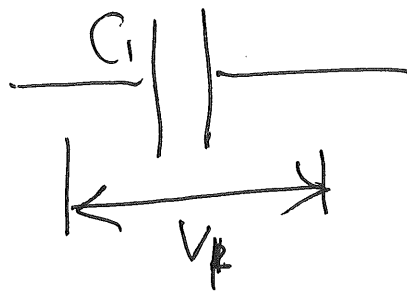

$$Q_2 = C_2 V_2$$

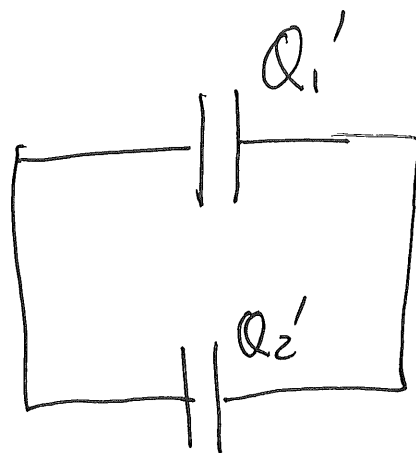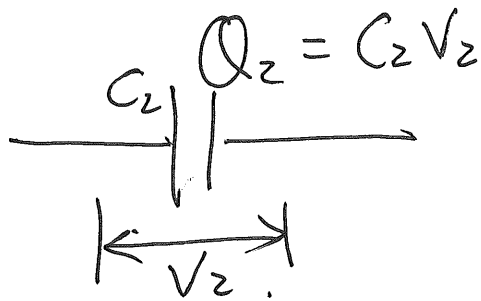

$$Q_1' + Q_2' = Q_1 + Q_2 \quad \text{--- (1)}$$

$$\cancel{Q} V_1 = V_2$$

$$C = \frac{Q}{V}$$

$$\Rightarrow \frac{Q_1'}{C_1} = \frac{Q_2'}{C_2} \quad \text{--- (2)}$$