
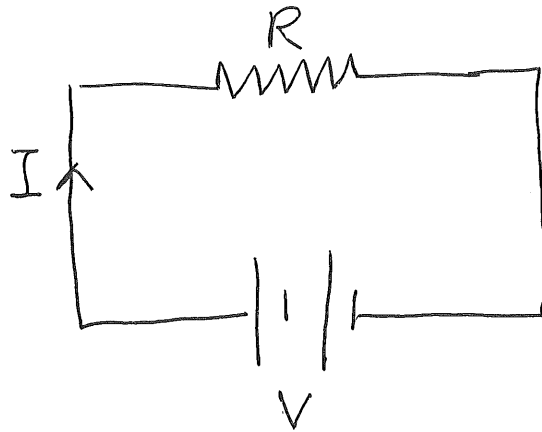


Ohm's Law.

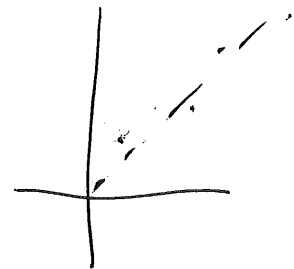

$\Rightarrow V = IR$ or $\vec{J} = \sigma \vec{E}$

V	I
2V	30mA
4V	72mA.
6V	115mA
8V	155mA
<u>10V</u>	<u>200mA.</u>



$$R = \frac{V}{I} = \frac{10V}{200mA} = \frac{10}{0.2} = 50 \underline{\underline{\Omega}}$$


$$\cancel{P} \quad W = QV$$

$$\begin{aligned}
 P &= \frac{W}{t} = \frac{Q}{t} V = IV \leftarrow \\
 &= I^2 R \\
 &= \frac{V^2}{R}.
 \end{aligned}$$

Resistors in series.




$$R_{\text{eff}} = R_1 + R_2 + R_3$$

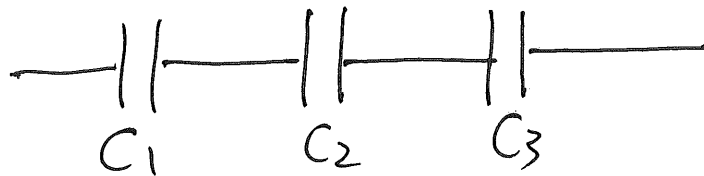


$$\cancel{R} \quad \frac{1}{C_{\text{eff}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}.$$

~~Answer~~

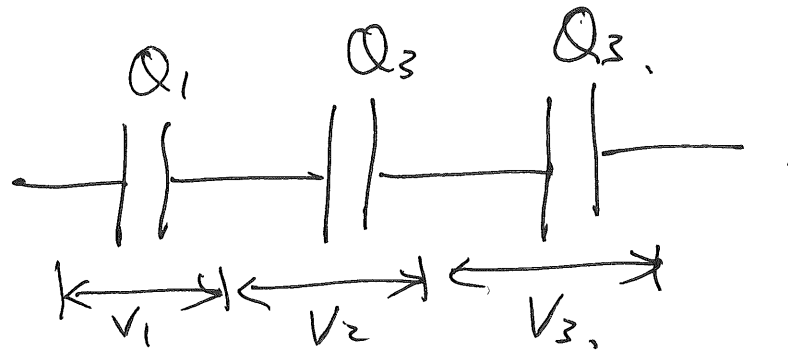

$$Q_1 = Q_2 = Q_3 = Q_{\text{eff}}$$

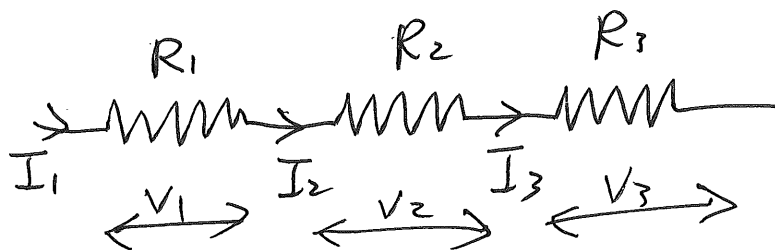
$$V_1 \neq V_2 \neq V_3 \neq V_{\text{eff}} \quad \cancel{V=V_1} \quad V_{\text{eff}} = V_1 + V_2 + V_3.$$




$$I_1 = I_2 = I_3 = I_{\text{eff}}$$

$$V_1 \neq V_2 \neq V_3 \neq V_{\text{eff}}$$

$$V_{\text{eff}} = V_1 + V_2 + V_3.$$

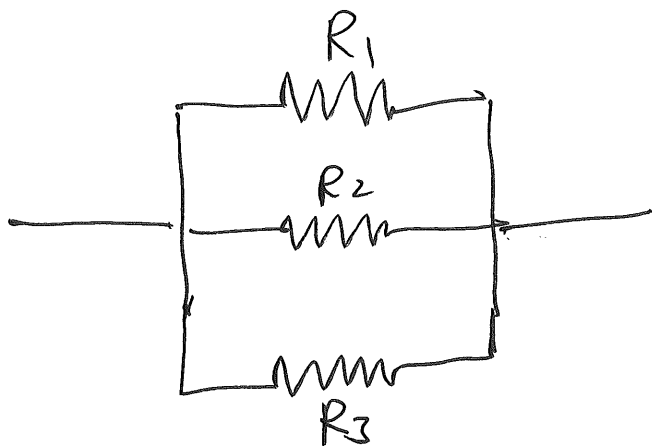

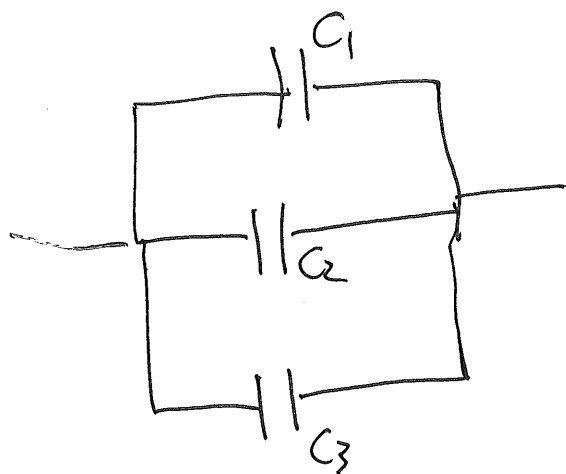
$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$C_{\text{eff}} = C_1 + C_2 + C_3.$$


~~Series~~
~~Parallel~~

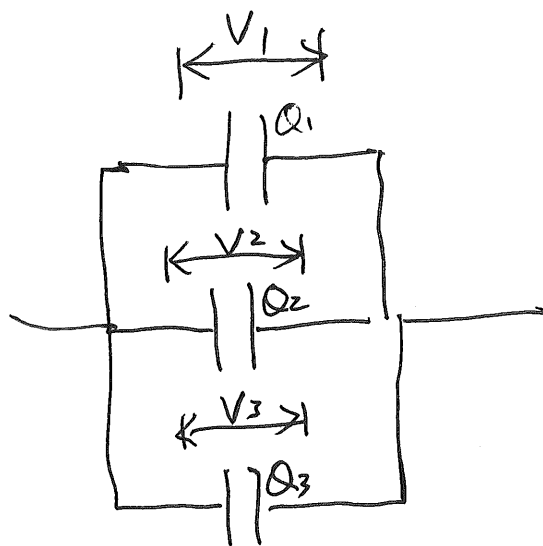

$$V_1 = V_2 = V_3 = V_{\text{eff}}$$

$$Q_1 \neq Q_2 \neq Q_3 \neq Q_{\text{eff}}$$


$$Q_{\text{eff}} = Q_1 + Q_2 + Q_3$$

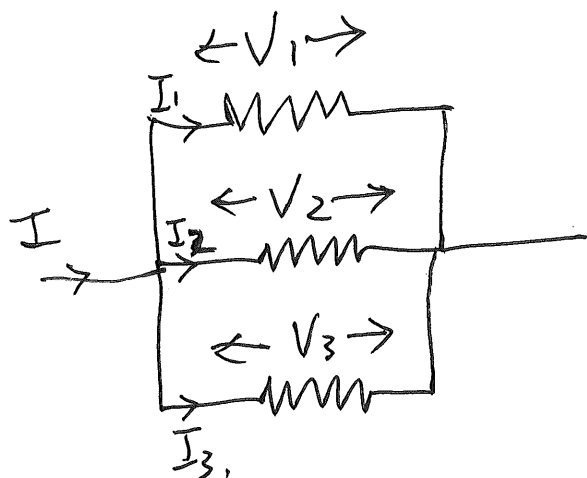

$$V_1 = V_2 = V_3 = V_{\text{eff}}$$

$$I_1 \neq I_2 \neq I_3 \neq I_{\text{eff}}$$



$$I_{\text{eff}} = I_1 + I_2 + I_3$$

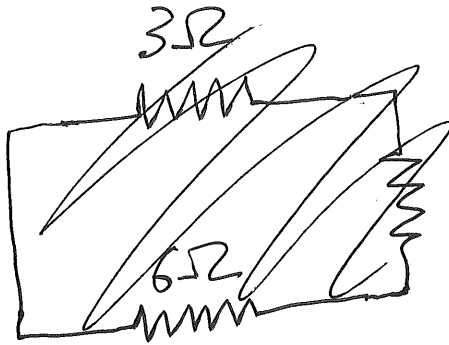


$$\frac{1}{3} + \frac{1}{6} = \frac{1}{R_{\text{eff}}}$$

$$\Rightarrow \frac{1}{R_{\text{eff}}} = \frac{2+1}{6}$$

$$\Rightarrow R_{\text{eff}} = 2\Omega$$

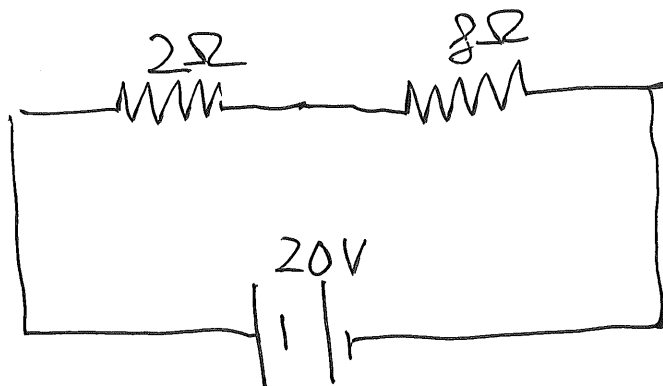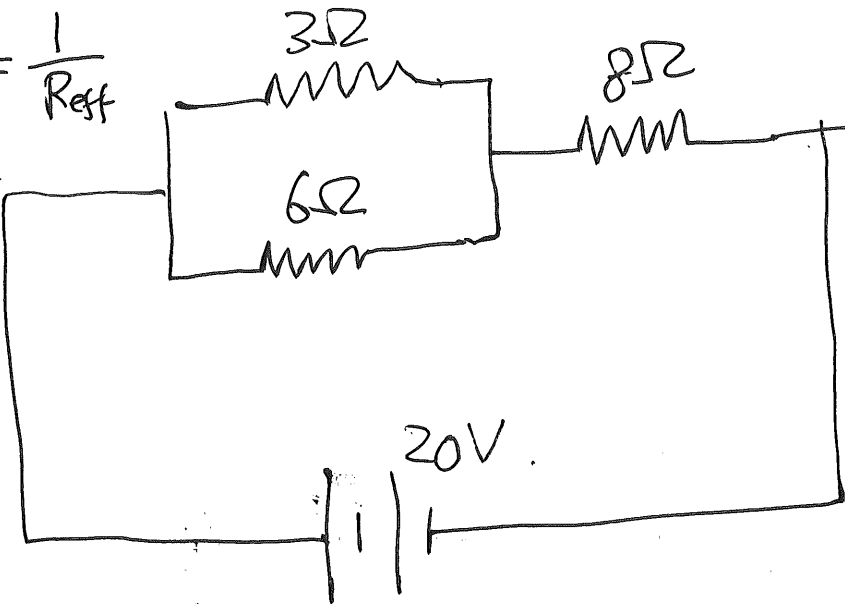


$$I = \frac{20}{10} = 2A.$$

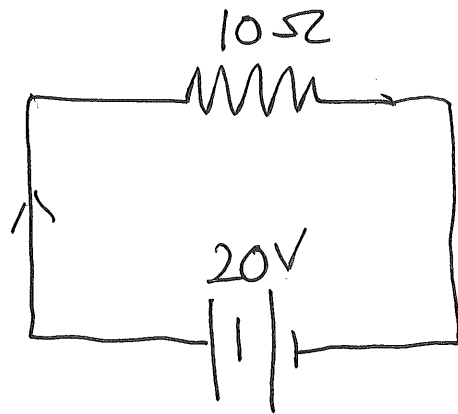

Total power dissipated

$$= I^2 R.$$

$$= (2)^2 (10) = 40W.$$

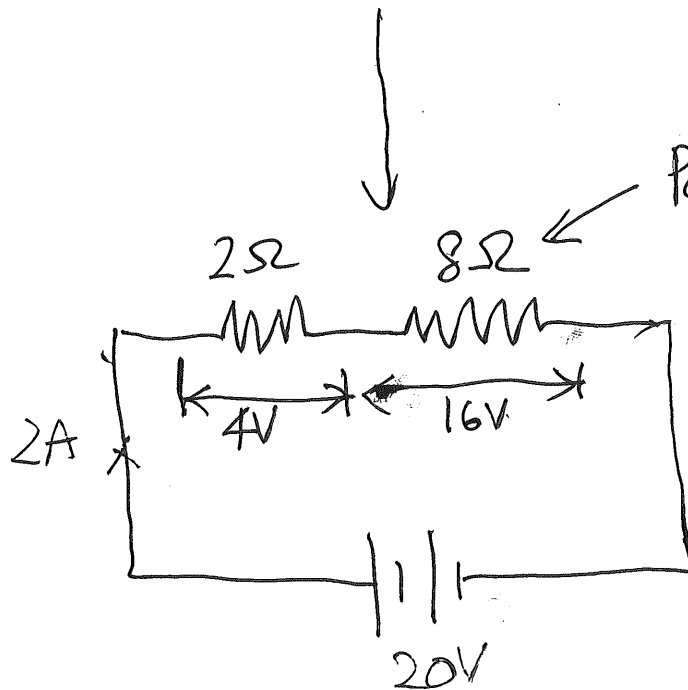


Power dissipated in 8Ω

$$= (2)^2 (8).$$

$$= 32W.$$



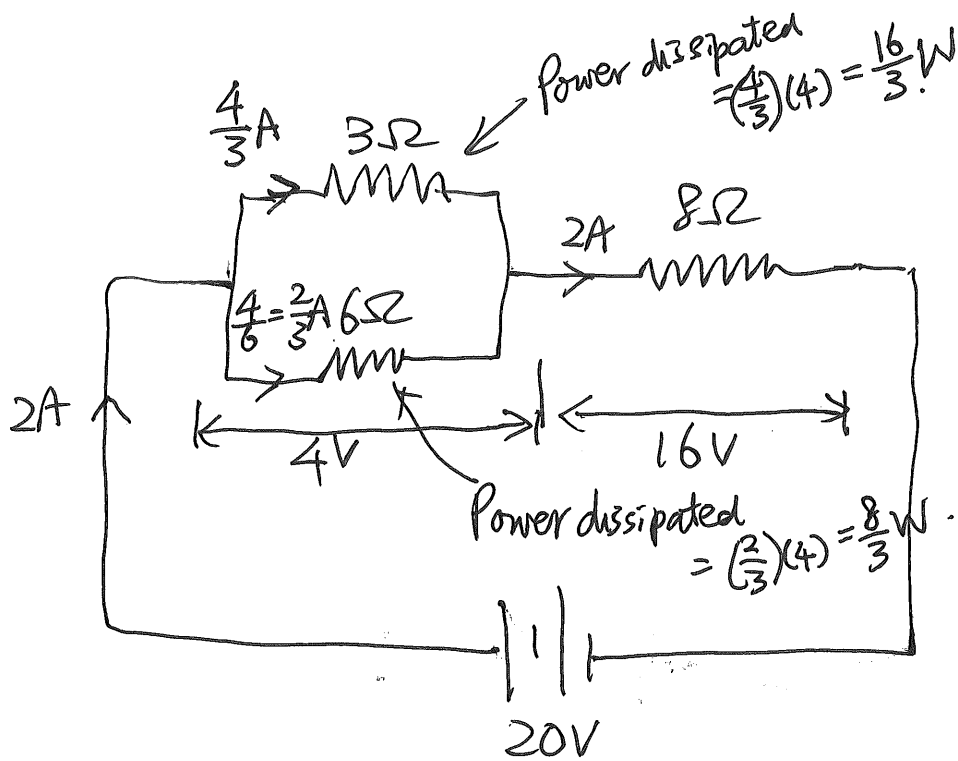

$$\begin{aligned}
 \text{Total power dissipated} &= \frac{16}{3} + \frac{8}{3} + 32 \\
 &= 8 + 32 = 40W
 \end{aligned}$$