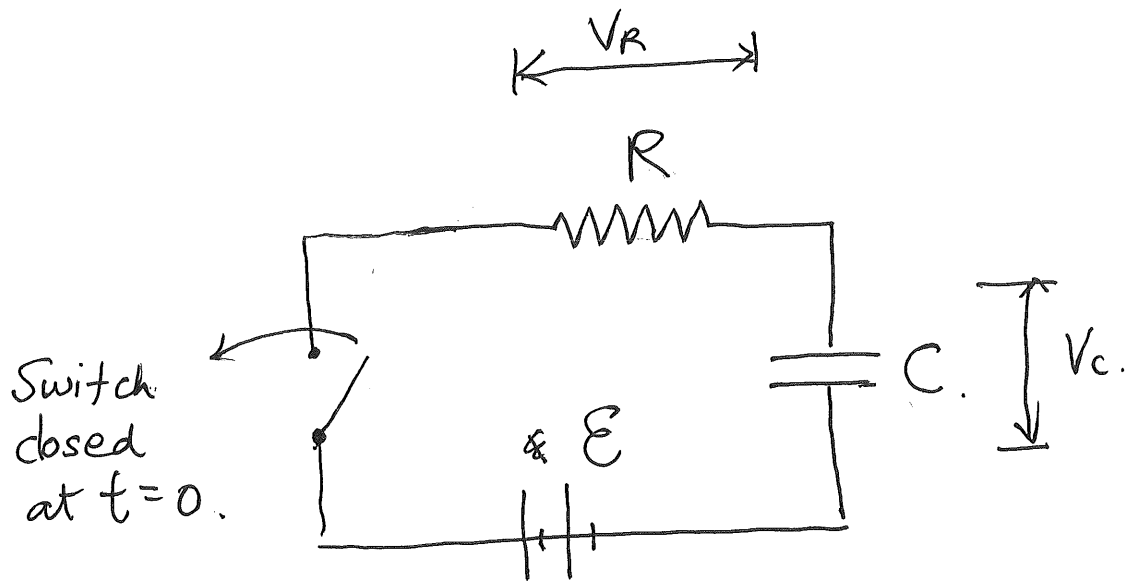


$$V_c = \mathcal{E} \left(1 - e^{-\frac{t}{RC}} \right)$$

Constant.

~~At what t , $V_c = \frac{1}{2} \mathcal{E}$?~~

At $t = 2RC$, $V_c = \text{?} \mathcal{E}$.



If R is larger, it takes longer/shorter time to charge the capacitor.

If C is larger, it takes longer/shorter time to charge the capacitor.

As time proceeds,

I increases/decreases.

Q increases/decreases.

V_R increases/decreases.

V_C increases/decreases.




RC is a value that determines how fast to charge up the capacitor.

Bigger RC means Longer time.

$$[R] = \frac{V}{\cancel{Q} A} \quad [C] = \frac{C}{V}$$

~~Coulomb~~

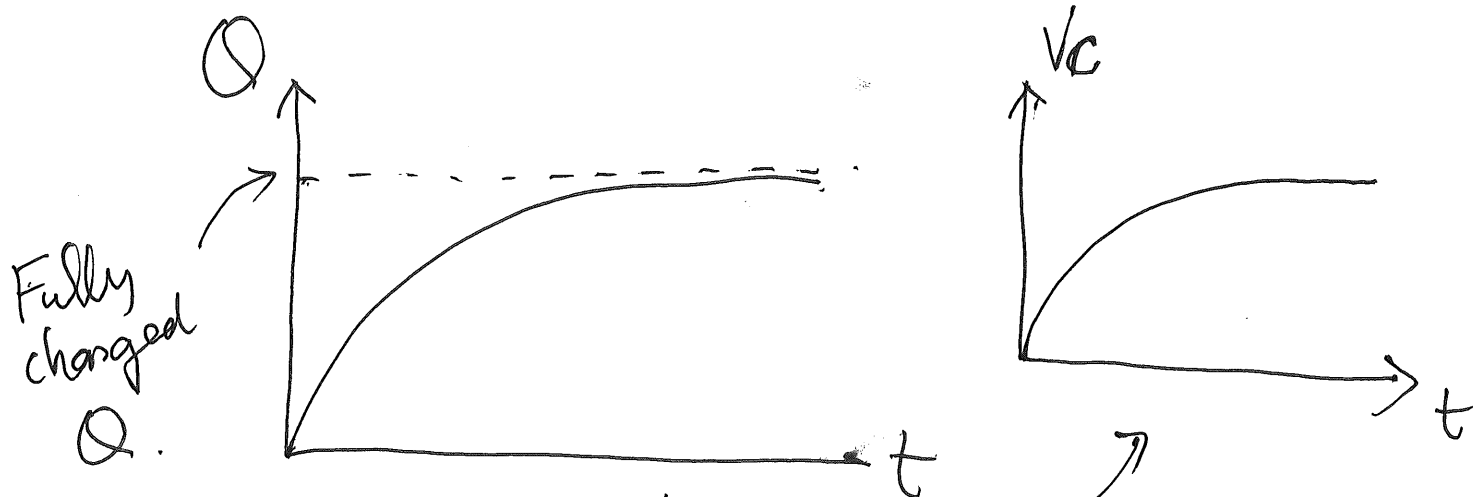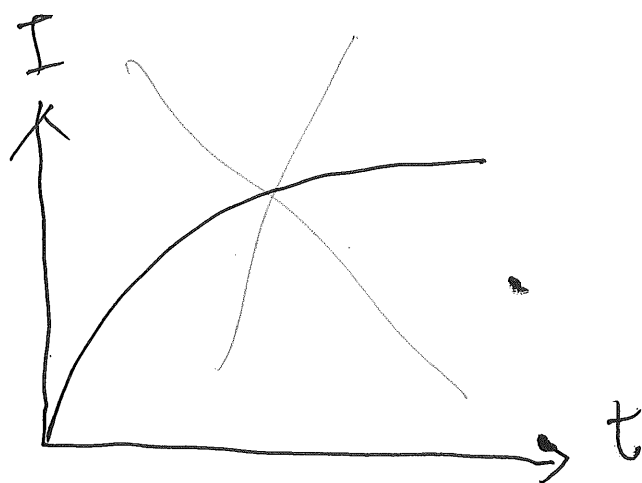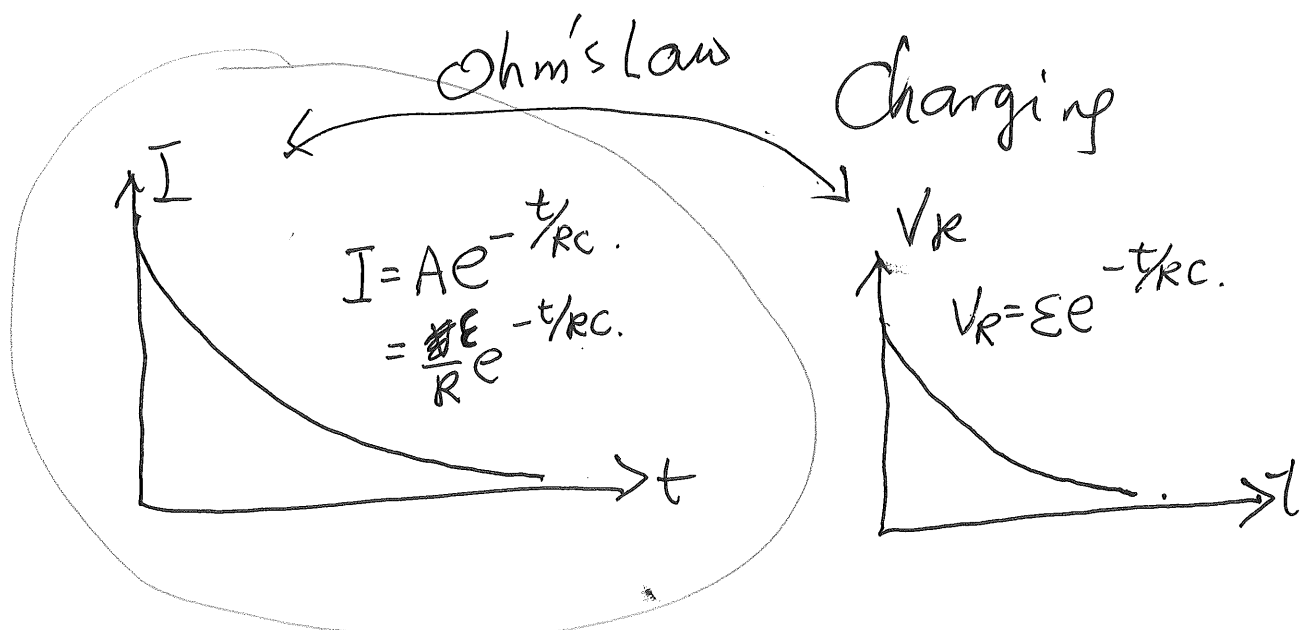
$$[RC] = \frac{V}{A} \cdot \frac{C}{V} = \frac{C}{A} = \frac{C}{\frac{C}{s}} = s.$$



$$Q = CE(1 - e^{-t/RC})$$

$C = \frac{Q}{V}$ or $Q = CV$.

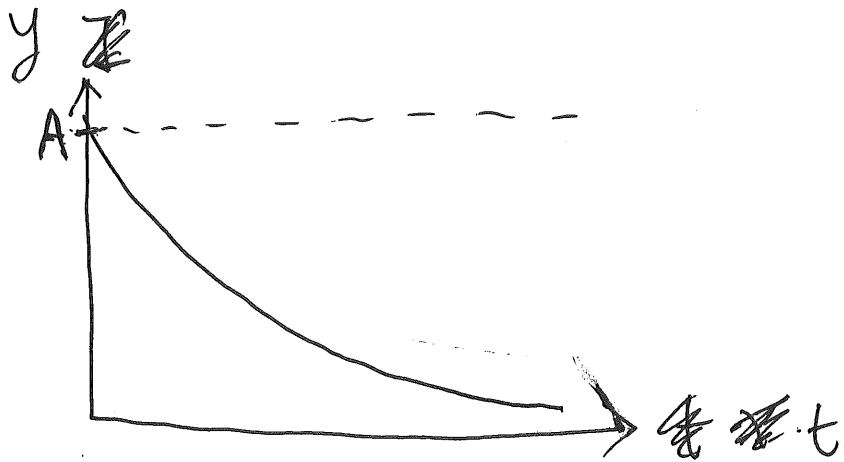
$V_C = \frac{Q}{C} \rightarrow V_C = E(1 - e^{-t/RC})$



$$y = Ae^{-at}$$

$\uparrow$ $y = A$ when $t = 0$.

~~Why not
e^{+at}~~

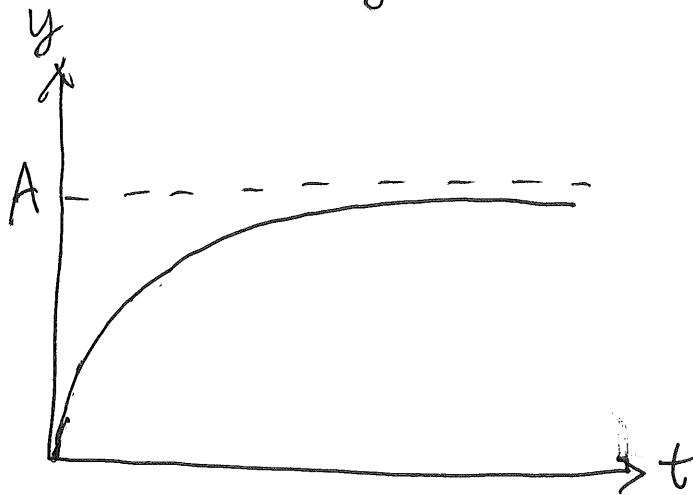


$$y = A(1 - e^{-at})$$

$\uparrow$

$y = A$ when $t = \infty$.

Discharging.

Switch
closed
at $t=0$.

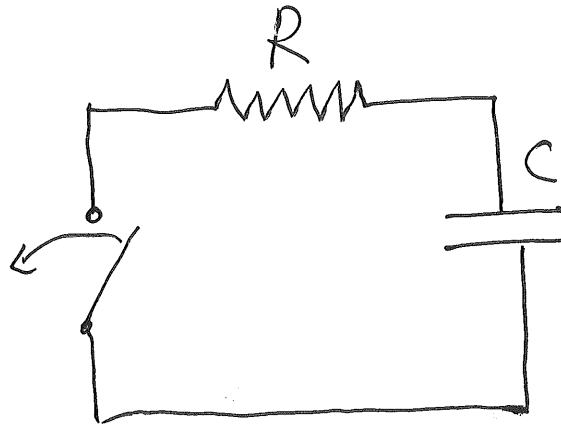

Fully charge
with $Q = Q_0$
at $t=0$

$$Q = Q_0 e^{-t/RC}.$$

$$V_C = \frac{Q_0}{C} e^{-t/RC}.$$

$$I = I_0 e^{-t/RC} = \frac{Q_0}{RC} e^{-t/RC}.$$

$(I_0 = \frac{V_C}{R}).$

$$V_R = IR = \frac{Q_0}{C} e^{-t/RC}.$$

$$V_C = 1V \text{ at } t = 10s.$$

$$V_C = 385 e^{-t/RC}$$

$$I = 385 e^{-10/RC}$$

CW