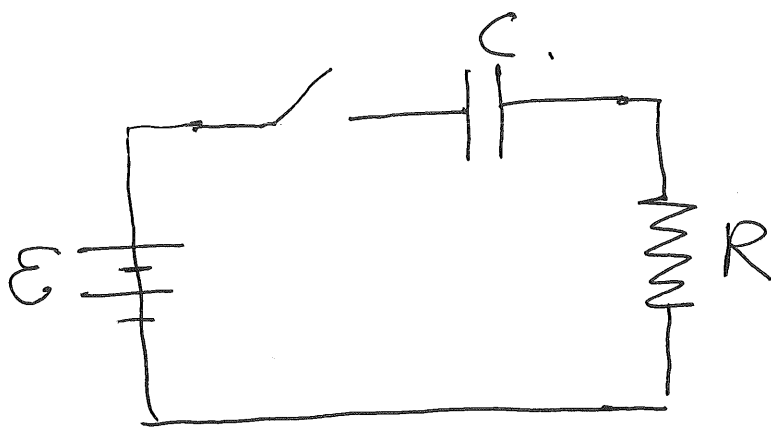




$$Q = Q_{\infty} (1 - e^{-t/RC})$$

$$= C\varepsilon (1 - e^{-t/RC})$$


$$I = \frac{dQ}{dt} = \cancel{C\varepsilon} C\varepsilon \left(\frac{+1}{RC} \right) e^{-t/RC}$$

$$= \frac{\varepsilon}{R} e^{-t/RC}$$

$$I = I_0 e^{-t/RC} = \frac{\varepsilon}{R} e^{-t/RC}$$

$$\text{Power dissipated in } R = I^2 R = \left(\frac{\varepsilon}{R} e^{-t/RC} \right)^2 \cdot R$$

$$= \frac{\varepsilon^2}{R} e^{-2t/RC}$$

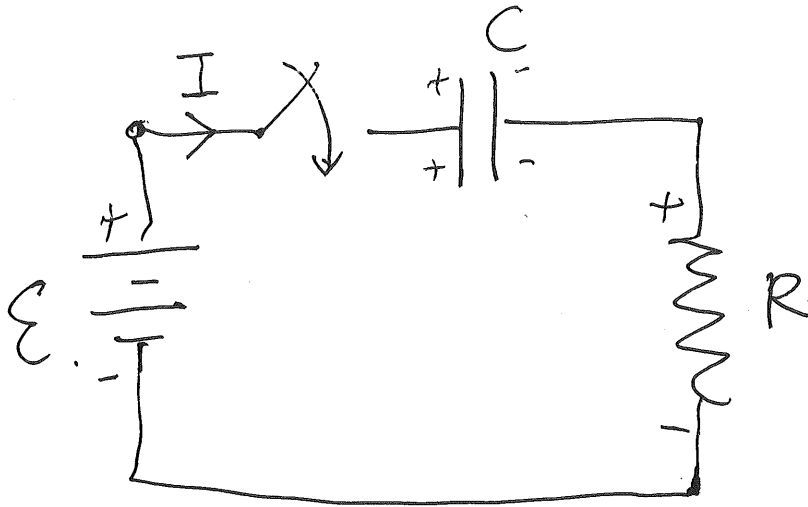

$$-\frac{Q}{C} - IR + \epsilon = 0.$$

$$I = + \frac{dQ}{dt} \leftarrow \text{Sign of } I \text{ and } dQ.$$

$$-\frac{Q}{C} - R \frac{dQ}{dt} + \epsilon = 0.$$

$$\Rightarrow R \frac{dQ}{dt} = \epsilon - \frac{Q}{C}$$

$$\Rightarrow R \frac{dQ}{dt} = \frac{\epsilon C - Q}{C}.$$


$$\Rightarrow RC dQ = (\epsilon C - Q) dt$$

$$\Rightarrow \int \frac{dQ}{\varepsilon C - Q} = \int \frac{dt}{RC}.$$

$$\Rightarrow -\ln(\varepsilon C - Q) = \frac{t}{RC}$$

Use initial condition $Q=0$ at $t=0$.
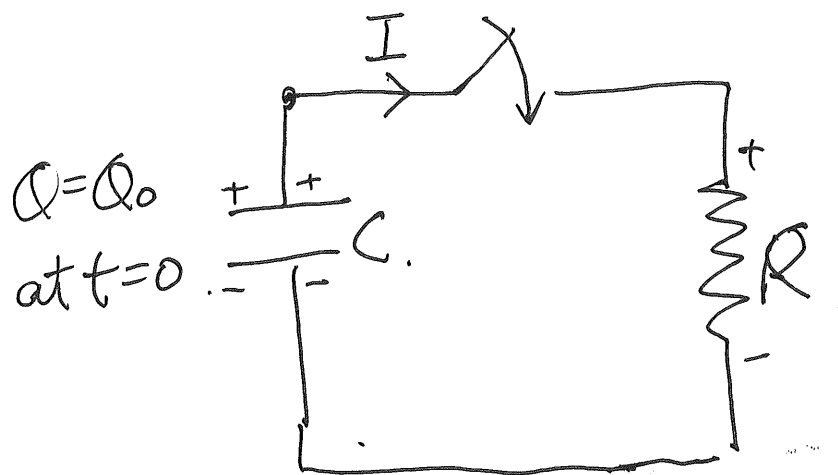
$$\text{Ans: } Q = C\varepsilon (1 - e^{-t/RC}).$$





$$-IR + \frac{Q}{C} = 0.$$

$$I = - \frac{dQ}{dt}$$


↑
★

$$\cancel{I} + R \frac{dQ}{dt} + \frac{Q}{C} = 0. \leftarrow$$

Charging & Discharging in RC circuit

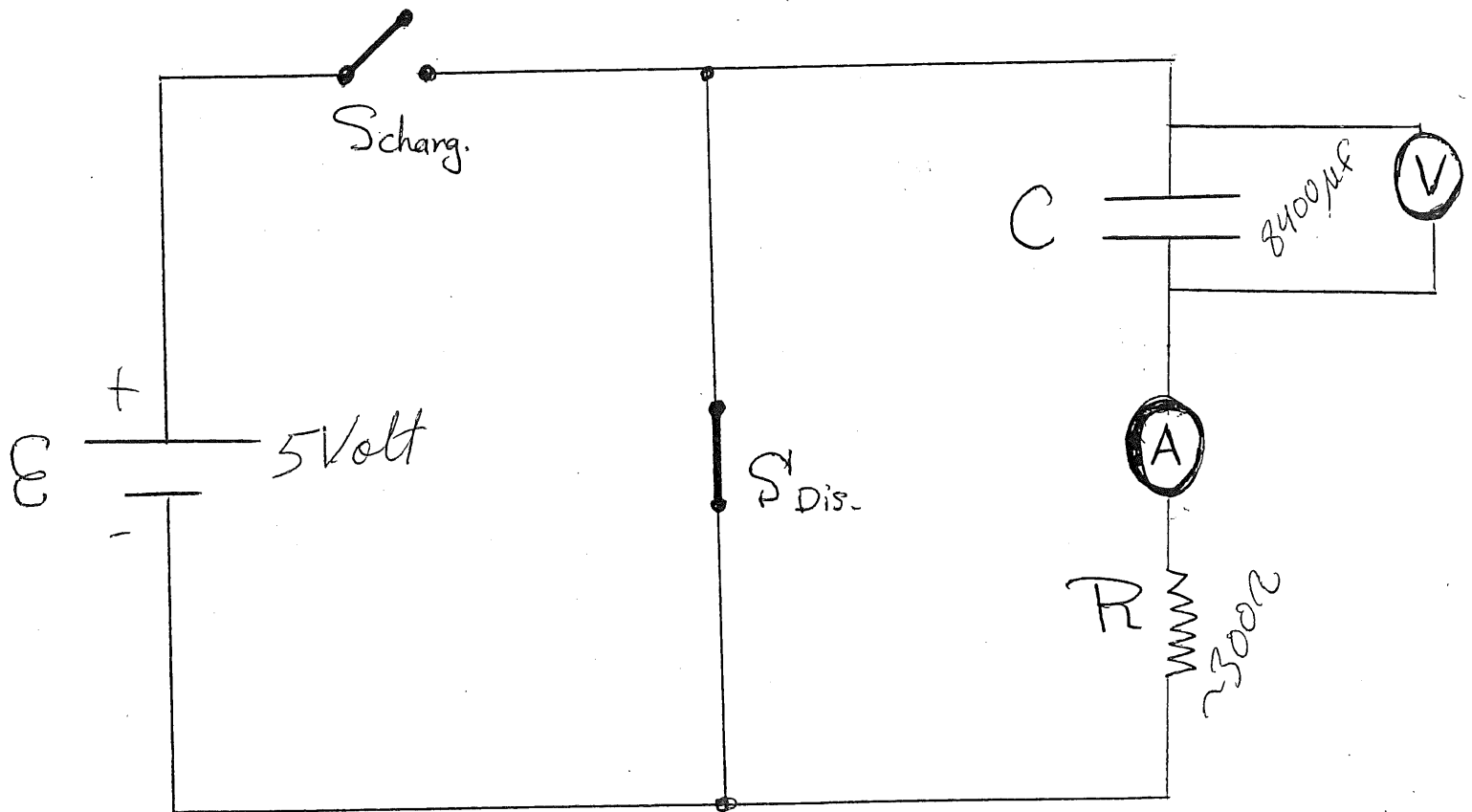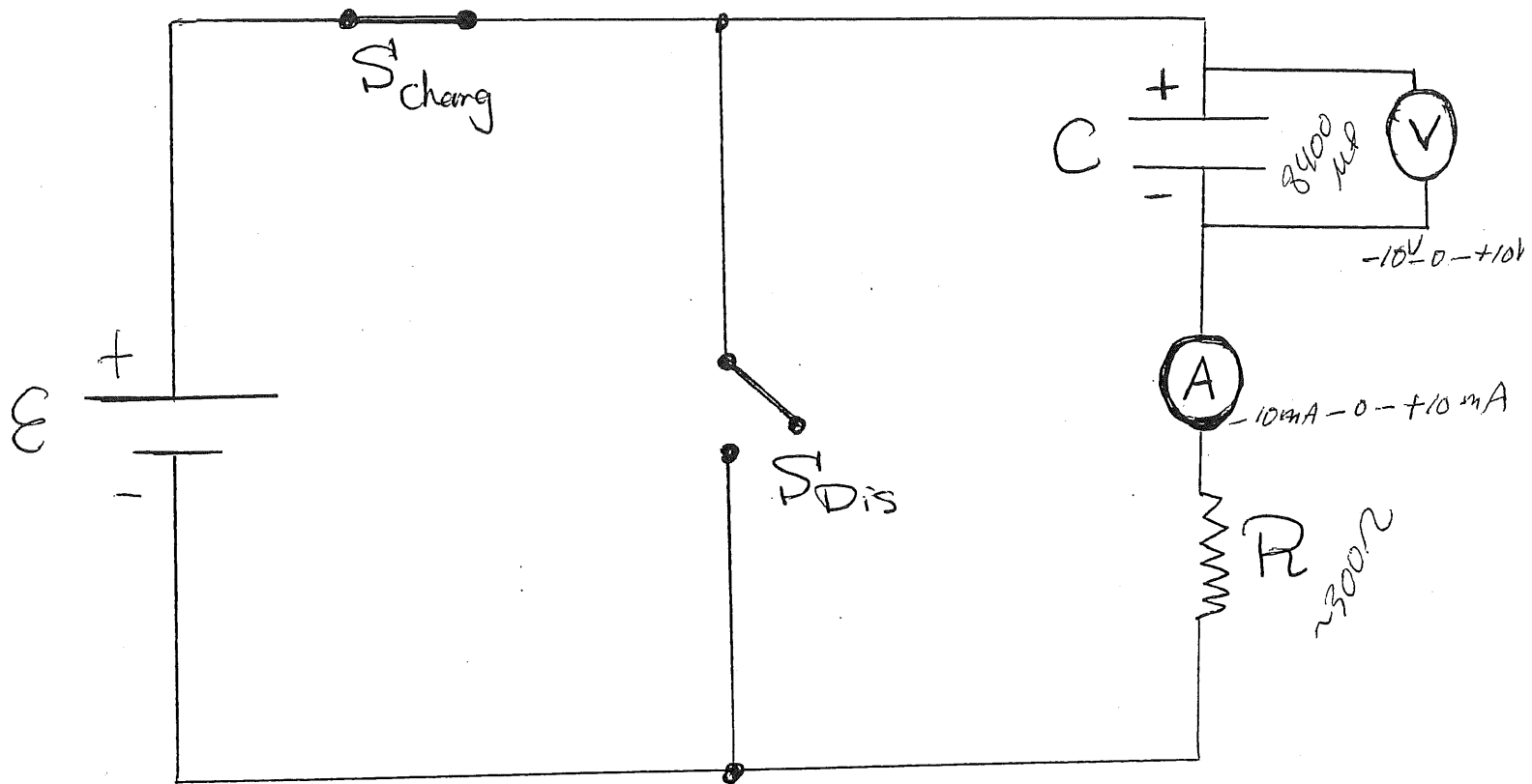


Electric

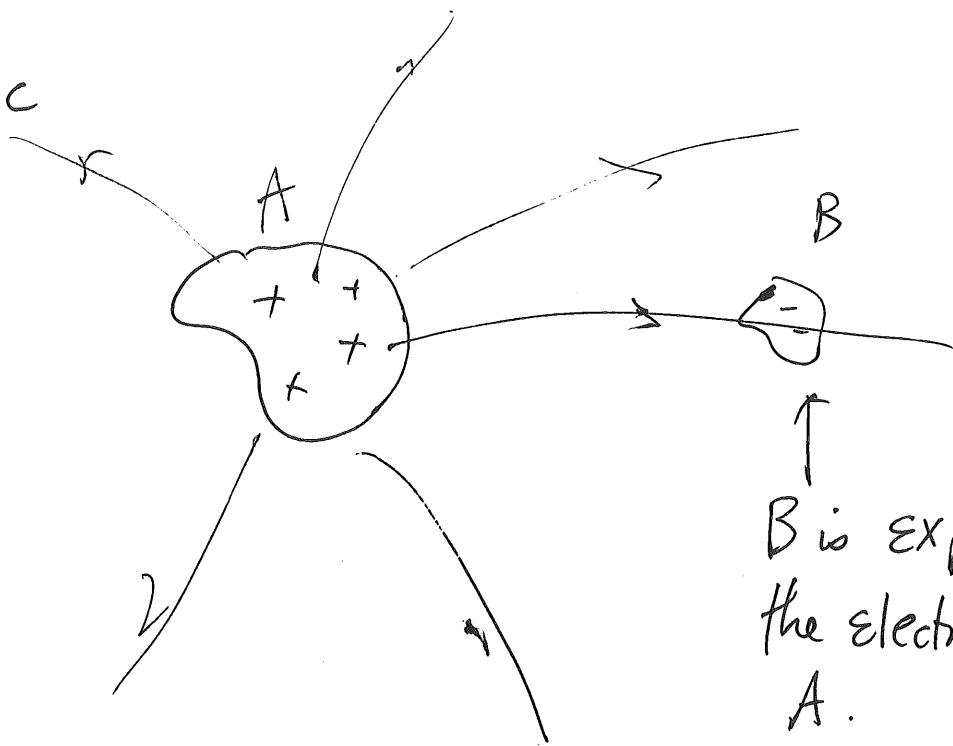

B is experiencing
the electric field of
A.

Magnetic

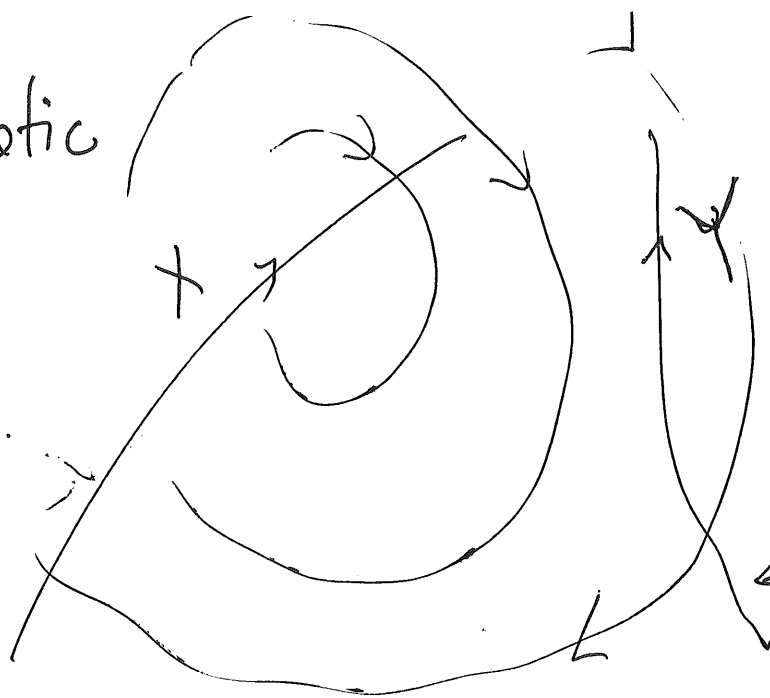

← Current Y is
experiencing the
magnetic field of
X.