
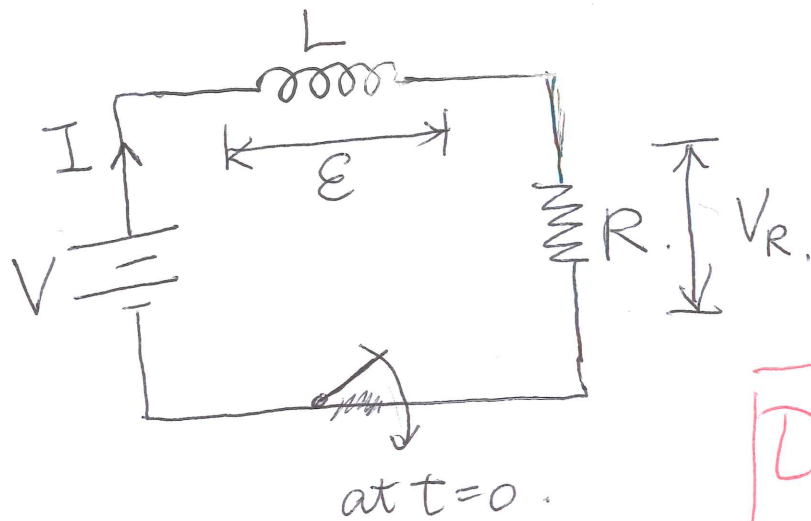


Charging RL

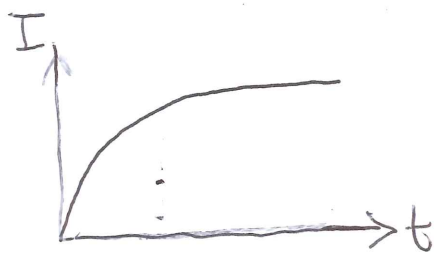

$$\tau = \frac{L}{R}$$




$$I = I_0 (1 - e^{-t/\tau})$$

$$= \frac{V}{R} (1 - e^{-t/\tau})$$





$$\varepsilon = \varepsilon_0 e^{-t/\tau}$$

$$= V e^{-t/\tau}$$

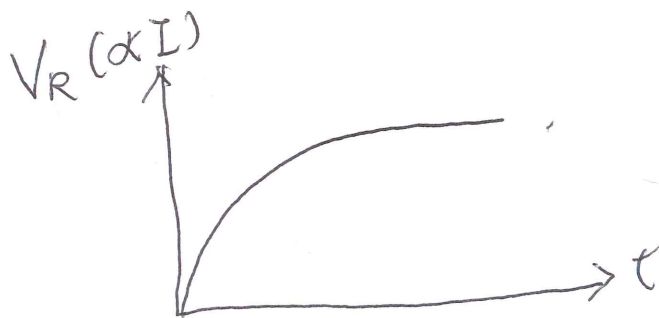

$$V = V_0 (1 - e^{-t/\tau})$$

$$= V (1 - e^{-t/\tau})$$

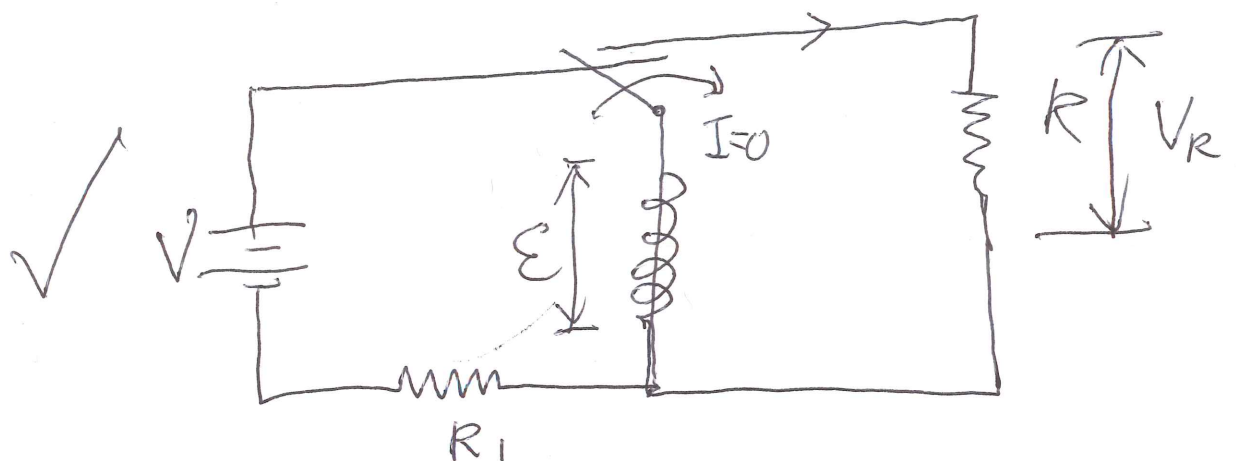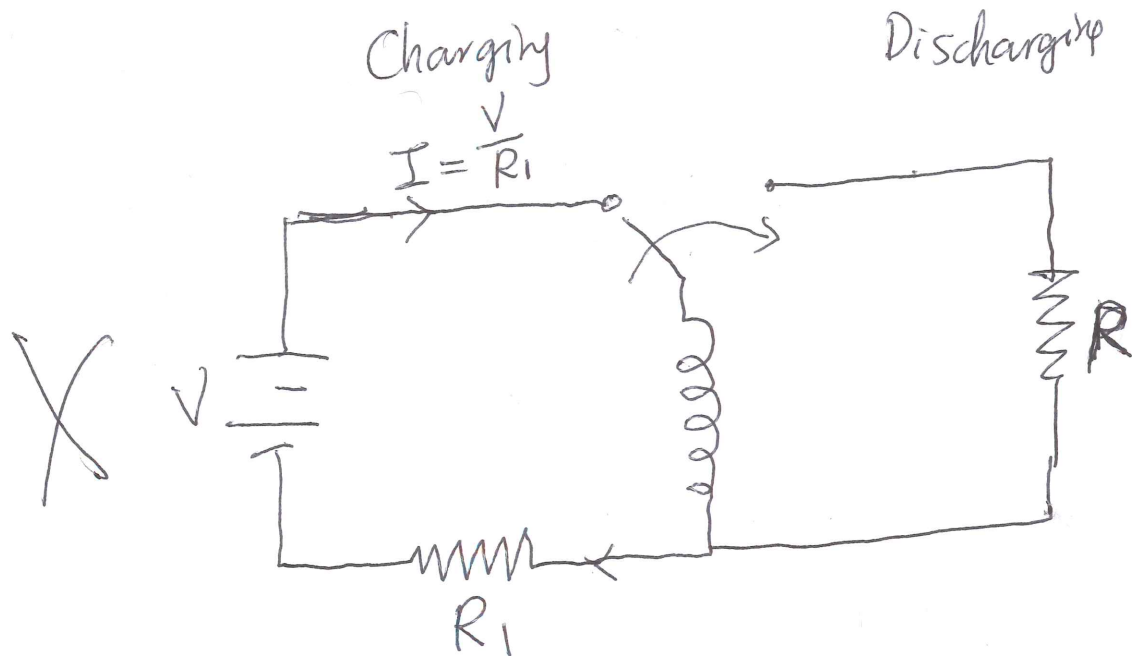

i

t

$$I = I_0 e^{-t/\tau} = \frac{V}{R} e^{-t/\tau}$$

$$\epsilon = \cancel{V_R} = \epsilon e^{-t/\tau}$$

↑

$$\epsilon = \cancel{\frac{V}{R_1}}$$

RC Circuit ✓


RL circuit ✓.

LC Circuit now.

Newton's viewpoint:

$$-kx = ma$$

Eq.
position

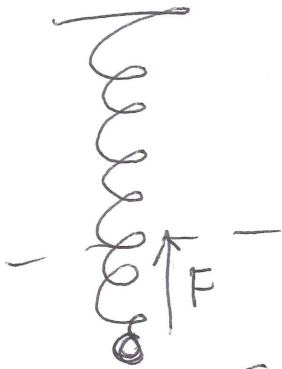

$$\Rightarrow -kx = m \frac{d^2x}{dt^2}$$

Energy view point:

$$\frac{d^2x}{dt^2} = v \frac{dv}{dx}$$

$$\underbrace{\frac{1}{2}mv^2}_{KE} + \underbrace{\frac{1}{2}kx^2}_{PE} = \text{Total Energy}$$


Constant

$$\uparrow \frac{1}{2}kA^2 \text{ or } \frac{1}{2}mV_{\max}^2$$


$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

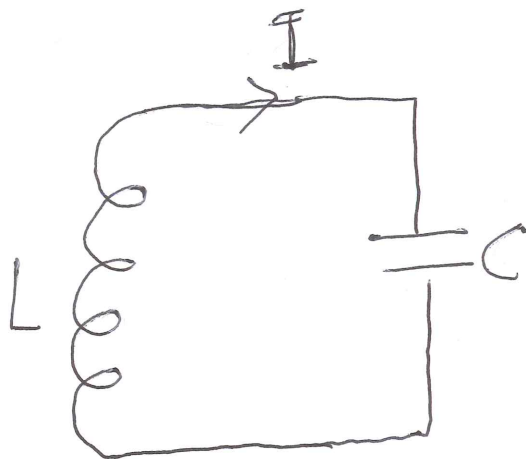Integration constants to be determined by initiation condition.



Details:

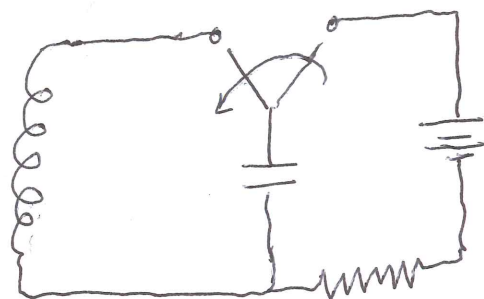

$$L \frac{dI}{dt} + \frac{Q}{C} = 0. \quad \leftarrow$$

differentiation:

~~$$L \frac{d^2 I}{dt^2} + \frac{I}{C} = 0 \quad \text{Equation of motion.}$$~~

$$I = \frac{dQ}{dt}.$$

$$L \leftrightarrow m$$

$$Q \leftrightarrow x, I \leftrightarrow v$$

$$C \leftrightarrow \frac{1}{k}.$$

$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0.$$

$$m \frac{d^2 x}{dt^2} + kx = 0.$$

$$\omega = \sqrt{\frac{k}{m}} \Rightarrow \sqrt{\frac{1}{LC}}.$$

Conservation of Energy:

$$\frac{1}{2}mv^2 + \frac{1}{2}kx^2 = \text{Total Energy}$$

↓

$$\frac{1}{2}LI^2 + \frac{1}{2C}Q^2 = \text{Total Energy}$$