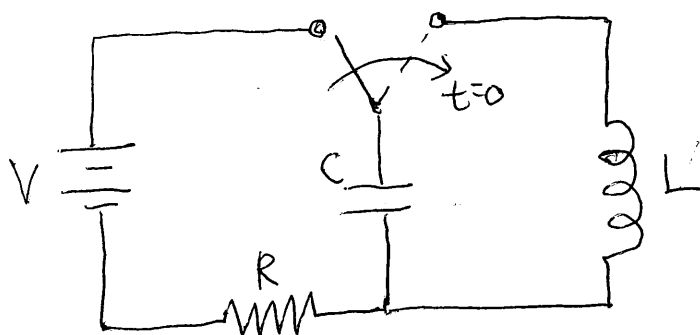


Example.




$$Q_0(\text{at } t=0) = \cancel{V} CV$$


$$I_0(\text{at } t=0) = 0.$$

Charging circuit
(Define initial condition).

LC resonance circuit.

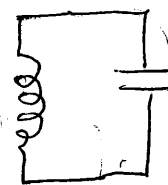


or

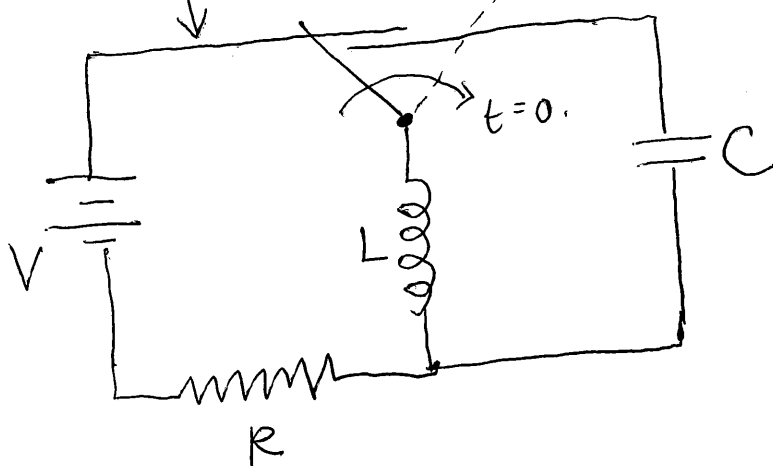

$$Q_0(\text{at } t=0) = 0.$$

$$I_0(\text{at } t=0) = \frac{V}{R}.$$

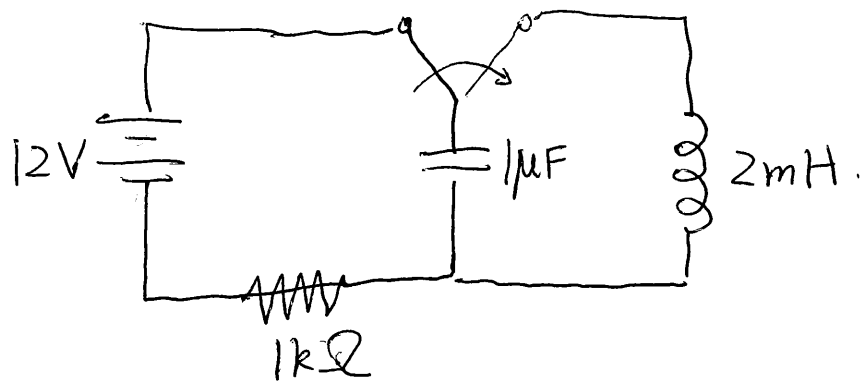

At $t=0$.

$$I_0 = 0.$$

$$Q_0 = (1\mu F)(12V) = 12 \times 10^{-6} C.$$

$$U = \frac{1}{2} CV^2 = \frac{1}{2} (1 \times 10^{-6}) (12)^2.$$

$$= 7.2 \times 10^{-5} J.$$

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 10^{-3} \times 1 \times 10^{-6}}}.$$

$$= \frac{1}{\sqrt{2 \times 10^{-9}}}$$

$$= 2.236 \times 10^4 \text{ rad/s.}$$

$$f = \frac{\omega}{2\pi} = 3558.8 \text{ Hz.}$$

$$T = \frac{1}{f} = 2.81 \times 10^{-4} \text{ s. or } 0.281 \text{ ms.}$$

What are I and Q at $t = 0.05 \text{ ms}$?

$$Q = A \sin(\omega t + \phi)$$

$$\text{At } t=0, Q_0 = 12 \times 10^{-6} \text{ C.}$$

$$12 \times 10^{-6} = A \sin \phi. \quad \text{--- (1)}$$

$$\text{At } t=0, I_0 = 0.$$

$$I = \frac{dQ}{dt} = A \omega \cos(\omega t + \phi).$$

$$\therefore A \omega \cos \phi = 0. \quad \text{--- (2)}$$

$$\Rightarrow \cos \phi = 0. \Rightarrow \phi = \frac{\pi}{2}.$$

$$\therefore A \sin \frac{\pi}{2} = 12 \times 10^{-6}.$$

$$\Rightarrow A = 12 \times 10^{-6}.$$

$$\underline{Q = (12 \times 10^{-6}) \sin \left(2.236 \times 10^4 t + \frac{\pi}{2} \right).}$$

$$\text{At } t = 0.05 \text{ ns.}$$

$$Q = (12 \times 10^{-6}) \sin \left(2.236 \times 10^4 \times 5 \times 10^{-5} + \frac{\pi}{2} \right),$$

$$= \underline{\underline{5.250 \times 10^{-6} \text{ C}}}.$$

$$I = \frac{dQ}{dt} = (12 \times 10^{-6}) (2.236 \times 10^4) \cos \left(2.236 \times 10^4 t + \frac{\pi}{2} \right),$$

$$= \cancel{2.236 \times 10^{-1}} \underline{\underline{0.241 \text{ A}}}$$

$$U_E = \cancel{\frac{1}{2} C} \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(5.25 \times 10^{-6})^2}{1 \times 10^{-6}}$$

$$= 1.378 \times 10^{-5} \text{ J.}$$

$$U_B = \frac{1}{2} L I^2 = \frac{1}{2} (2 \times 10^{-3}) (0.241)^2$$

$$= 5.808 \times 10^{-5} \text{ J.}$$

$$U_{\text{total}} = 1.378 \times 10^{-5} + 5.808 \times 10^{-5}$$

$$= \cancel{7.186 \times 10^{-5} \text{ J.}} \sim 7.2 \times 10^{-5} \text{ J.}$$