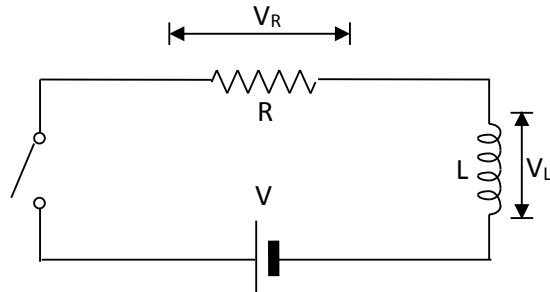


Name: \_\_\_\_\_

PHY 232 Summer 2016 Class Work  
Class 35. Work on Last Class - RL Circuit

PART A.



Switch is closed at  $t=0$ .

(a) What is the value of the following quantities at  $t=0$  (in terms of  $V$ ,  $R$ , and  $L$ ):

$I =$  \_\_\_\_\_  $V_L =$  \_\_\_\_\_  $V_R =$  \_\_\_\_\_

(b) What is the value of the following quantities at  $t=\infty$  (in terms of  $V$ ,  $R$ , and  $L$ ):

$I =$  \_\_\_\_\_  $V_L =$  \_\_\_\_\_  $V_R =$  \_\_\_\_\_

(c) Write down the following quantities as a function of time (in terms of  $V$ ,  $R$ ,  $L$ , and  $t$ ):

$I(t) =$  \_\_\_\_\_


$V_L(t) =$  \_\_\_\_\_

$V_R(t) =$  \_\_\_\_\_

$P_R(t) =$  \_\_\_\_\_ ( $P_R$  = Power dissipated in  $R$ )

$U_L(t) =$  \_\_\_\_\_ ( $U_L$  = Energy stored in  $R$ )

PART B.

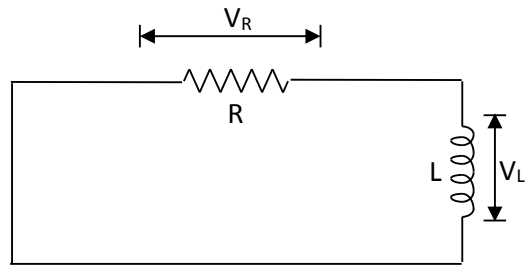

If current through the resistor is  $I_0$  at  $t=0$ .

(a) What is the value of the following quantities at  $t=0$  (in terms of  $R$ ,  $L$ , and  $I_0$ ):

$$I = \underline{I_0} \quad V_L = \underline{\hspace{2cm}} \quad V_R = \underline{\hspace{2cm}}$$

(b) What is the value of the following quantities at  $t=\infty$  (in terms of  $R$ ,  $L$ , and  $I_0$ ):

$$I = \underline{\hspace{2cm}} \quad V_L = \underline{\hspace{2cm}} \quad V_R = \underline{\hspace{2cm}}$$

(c) Write down the following quantities as a function of time (in terms of  $R$ ,  $L$ ,  $I_0$  and  $t$ ):

$$I(t) = \underline{\hspace{4cm}}$$

$$V_L(t) = \underline{\hspace{4cm}}$$

$$V_R(t) = \underline{\hspace{4cm}}$$

$$P_R(t) = \underline{\hspace{4cm}} \quad (P_R = \text{Power dissipated in } R)$$

$$U_L(t) = \underline{\hspace{4cm}} \quad (U_L = \text{Energy stored in } R)$$