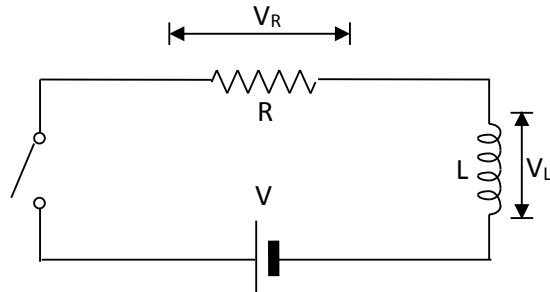


Name: _____

PHY 232 Summer 2016 Class Work
Class 35. Work on Last Class - RL Circuit

PART A.



Switch is closed at $t=0$.

(a) What is the value of the following quantities at $t=0$ (in terms of V , R , and L):

$$I = \underline{0} \quad V_L = \underline{V} \quad V_R = \underline{0}$$

(b) What is the value of the following quantities at $t=\infty$ (in terms of V , R , and L):

$$I = \underline{V/R} \quad V_L = \underline{0} \quad V_R = \underline{V}$$

(c) Write down the following quantities as a function of time (in terms of V , R , L , and t):

$$I(t) = \underline{\frac{V}{R}(1 - e^{-\frac{R}{L}t})}$$


$$V_L(t) = \underline{Ve^{-\frac{R}{L}t}}$$

$$V_R(t) = \underline{V(1 - e^{-\frac{R}{L}t})}$$

$$P_R(t) = \underline{\frac{V^2}{R}(1 - e^{-\frac{R}{L}t})^2} \quad (P_R = \text{Power dissipated in } R)$$

$$U_L(t) = \underline{\frac{LV^2}{2R}(1 - e^{-\frac{R}{L}t})^2} \quad (U_L = \text{Energy stored in } R)$$

PART B.

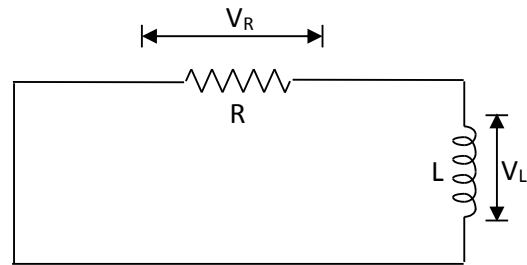

If current through the resistor is I_0 at $t=0$.

(a) What is the value of the following quantities at $t=0$ (in terms of V , R , L and I_0):

$$I = \underline{I_0 \text{ (Given)}} \quad V_L = \underline{I_0 R} \quad V_R = \underline{I_0 R}$$

(b) What is the value of the following quantities at $t=\infty$ (in terms of V , R , L and I_0):

$$I = \underline{0} \quad V_L = \underline{0} \quad V_R = \underline{0}$$

(c) Write down the following quantities as a function of time (in terms of V , R , L , I_0 and t):

$$I(t) = \underline{I_0 e^{-\frac{R}{L}t}}$$

$$V_L(t) = \underline{I_0 R e^{-\frac{R}{L}t}}$$

$$V_R(t) = \underline{I_0 R e^{-\frac{R}{L}t}}$$

$$P_R(t) = \underline{I_0^2 R e^{-\frac{2R}{L}t}} \quad (P_R = \text{Power dissipated in } R)$$

$$U_L(t) = \underline{\frac{1}{2} L I_0^2 e^{-\frac{2R}{L}t}} \quad (U_L = \text{Energy stored in } R)$$