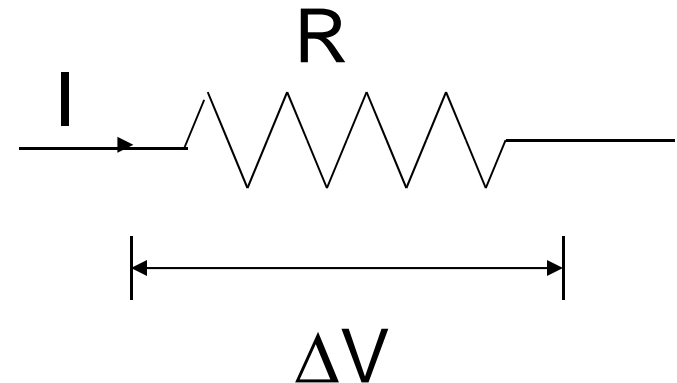


# Class 18 Resistors in Parallel and Series

# Power


Power dissipated  
in resistance R:

$$P = I\Delta V = I^2R = \frac{\Delta V^2}{R}$$




Units of power:  
Watt (W)  $\equiv$  J/s
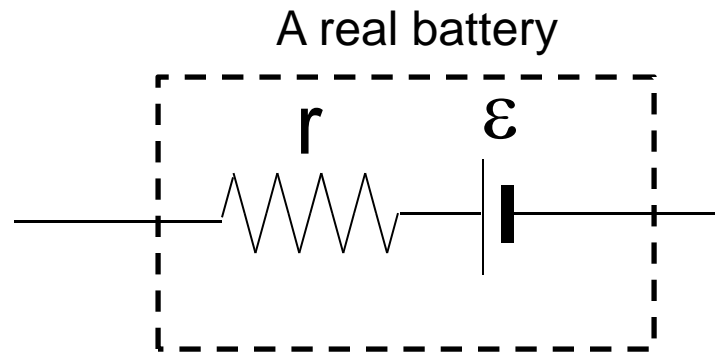
# Electromotive Force and Internal Resistance



Electromotive force (emf  $\varepsilon$ ) is the maximum possible voltage the battery can provide between its terminal. You can think it like the voltage of an ideal battery with no internal resistance.

When connected externally:


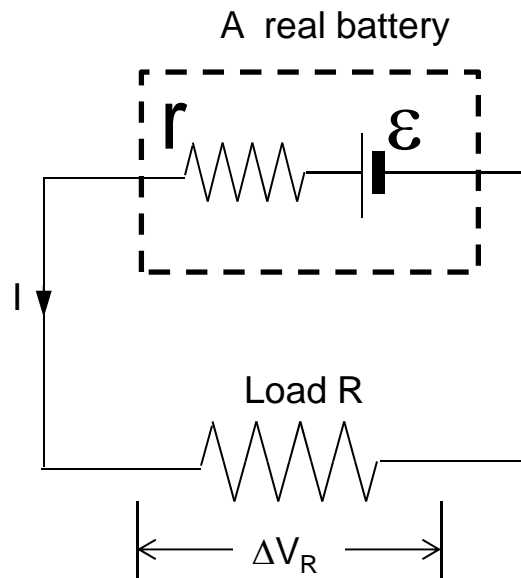


$$I = \frac{\varepsilon}{R + r}$$

$$\Delta V_R = IR = \frac{\varepsilon R}{R + r}$$

Voltage across the load resistance  $R$  will drop if more current is drawn from the battery (by making  $R$  smaller).

# Connecting Resistors in Series

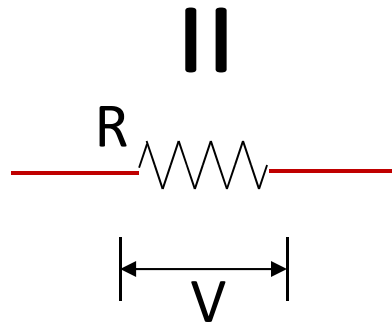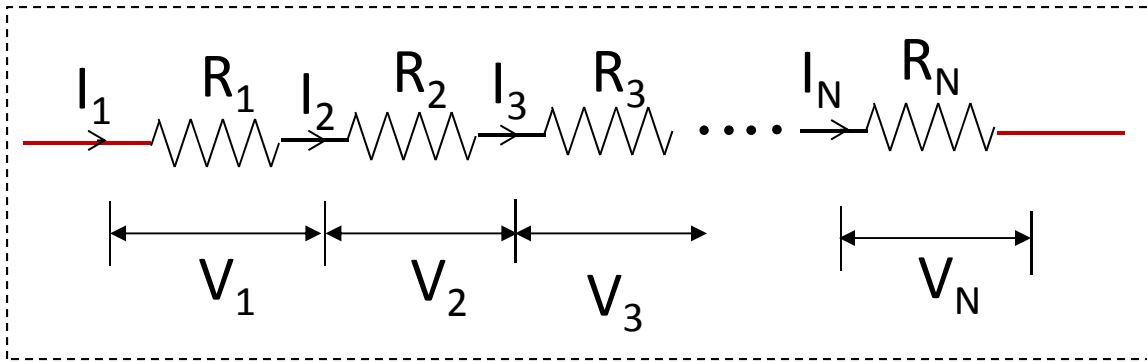

$$R_{\text{eff}} = R_1 + R_2 + R_3 + \dots + R_N$$

$$I = I_1 = I_2 = I_3 = \dots = I_N$$


$$V = V_1 + V_2 + V_3 + \dots + V_N$$

1. Current through each individual resistor is the same: (why?)

$$I = I_1 = I_2 = I_3 = \dots = I_N$$
$$\Rightarrow \frac{V}{R} = \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_3}{R_3} = \dots = \frac{V_N}{R_N}$$

2. Potential difference across each individual resistor should be different (unless they have the same resistance).

# Connecting Resistors in Parallel

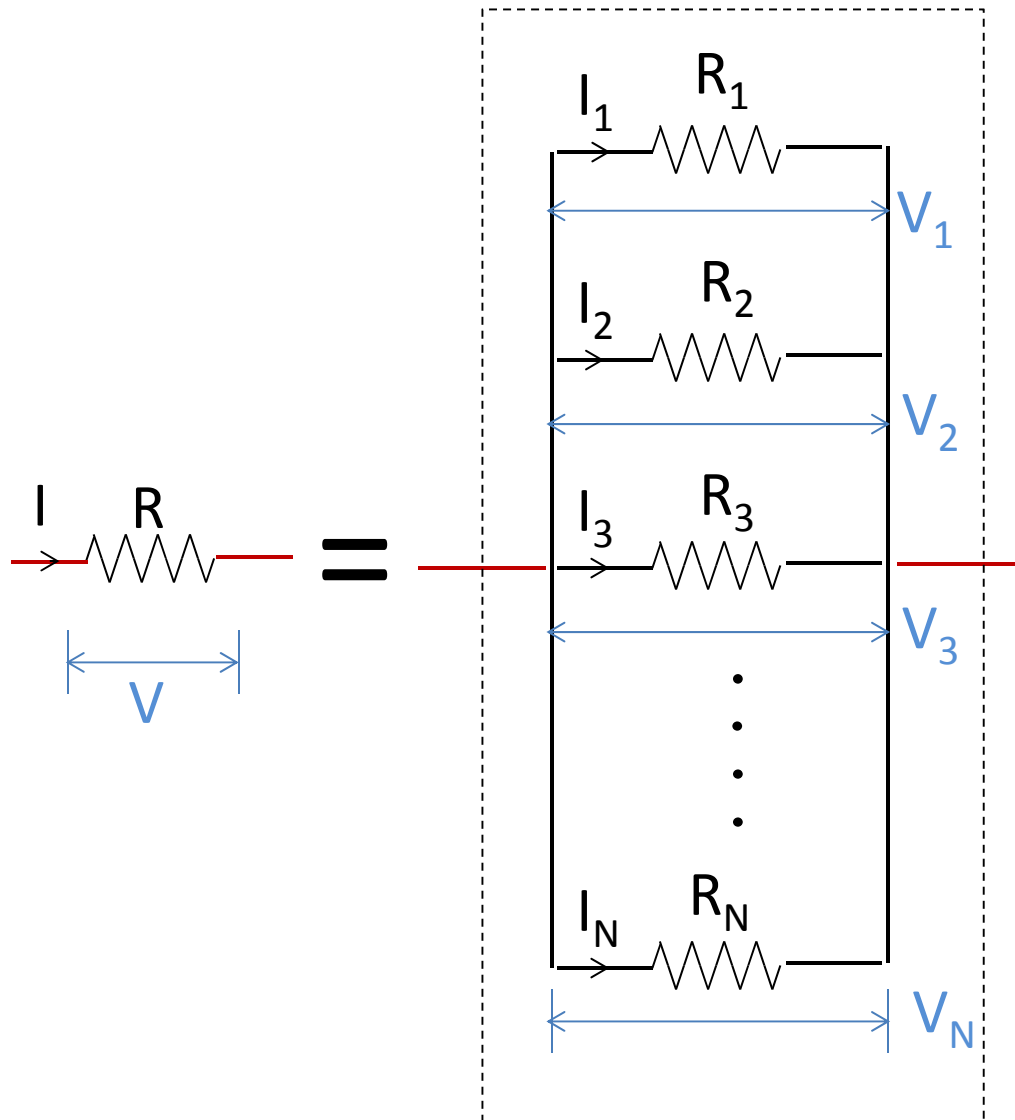

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

$$I = I_1 + I_2 + I_3 + \dots + I_N$$

$$V = V_1 = V_2 = V_3 = \dots = V_N$$

1. Potential difference across each individual resistor is the same: (why?)

$$V = V_1 = V_2 = V_3 = \dots = V_N$$

$$\Rightarrow I_1 R_1 = I_2 R_2 = I_3 R_3 = \dots = I_N R_N$$

2. Current through each individual resistor should be different (unless they have the same resistance).