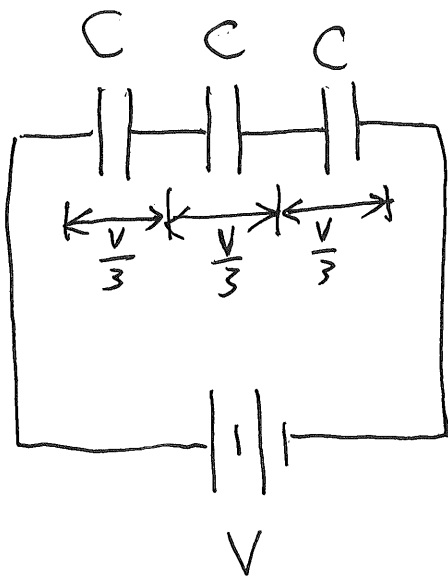



$$C = \frac{Q}{V}$$

$$U = \frac{1}{2} C V^2$$




$$U = \left[\frac{1}{2} C \left(\frac{V}{3} \right)^2 \right] \times 3$$
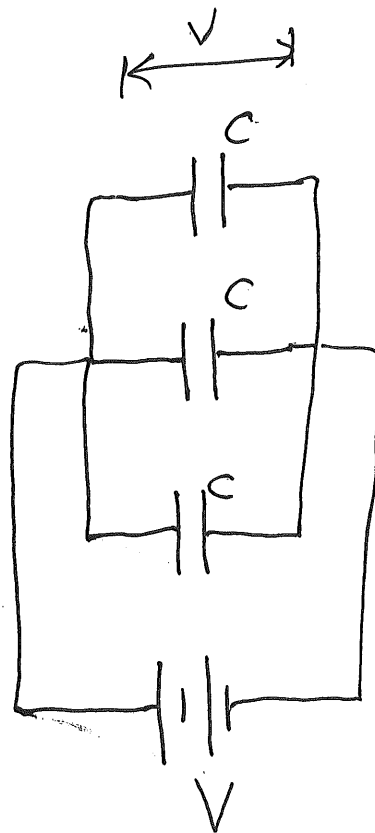
$$= \frac{1}{3} \times \left(\frac{1}{2} C V^2 \right)$$




$$U = \left(\frac{1}{2} C V^2 \right) \times 3$$
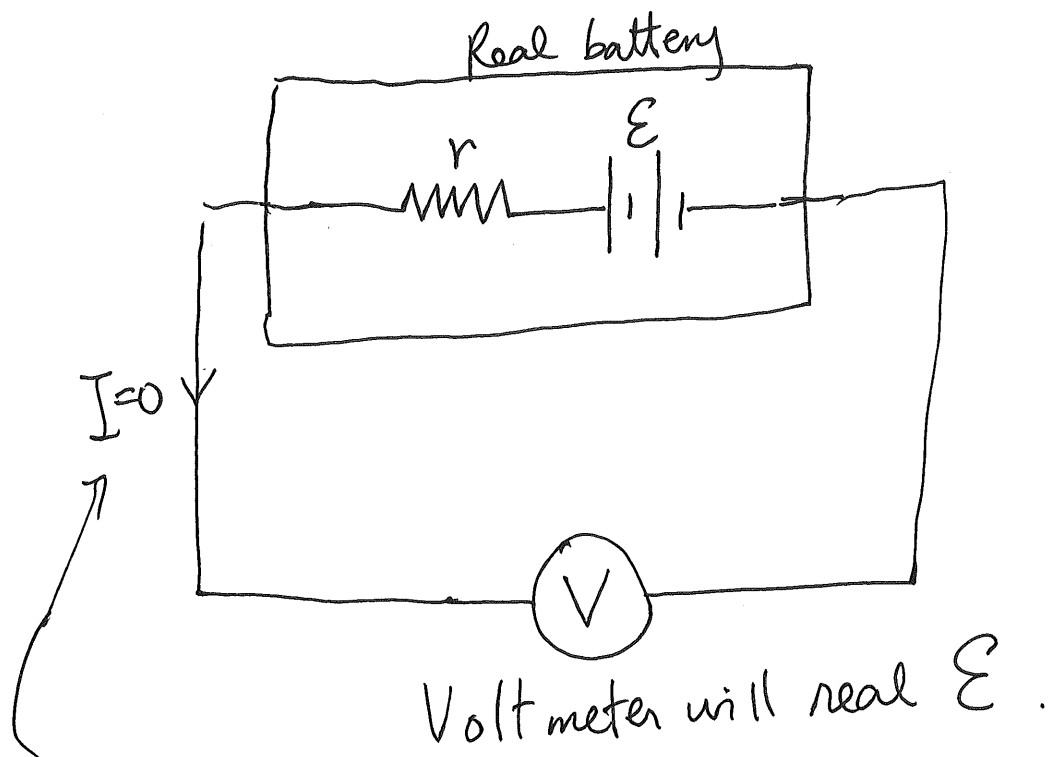
$$= 3 \times \left(\frac{1}{2} C V^2 \right)$$



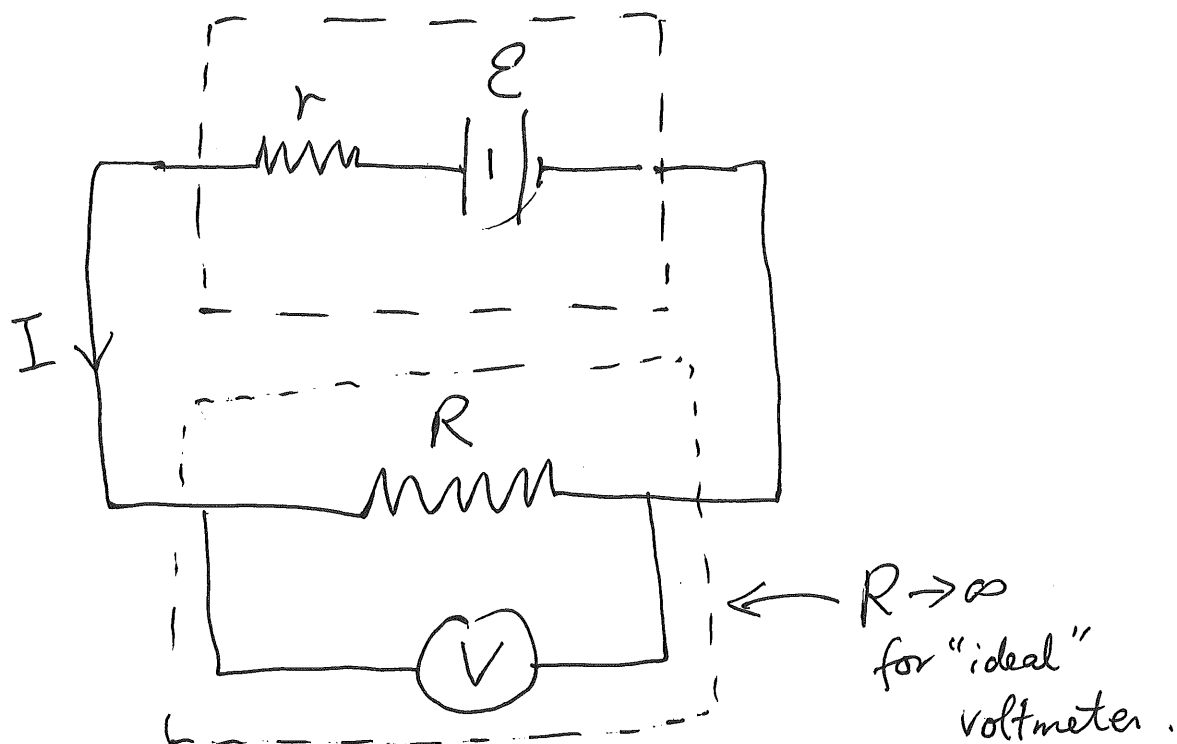ideal because
voltmeter has
" ∞ " resistance



$$I = \frac{\mathcal{E}}{R + r}$$


$$V = IR = \frac{\mathcal{E}R}{R + r}$$

e.g. $r = 1\Omega$, $R = 99\Omega$, $V = 0.99\mathcal{E}$.

~~$r = 1\Omega$~~ $R = 9\Omega$, $V = 0.9\mathcal{E}$.

$R = 1\Omega$, $V = 0.5\mathcal{E}$.

In series.

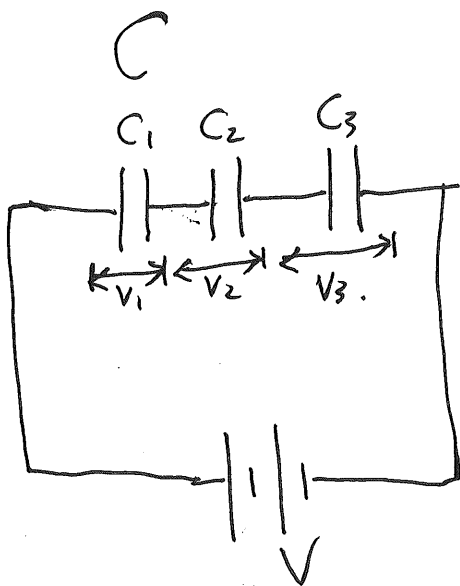


$$V = V_1 + V_2 + V_3$$

$$Q_1 = Q_2 = Q_3$$

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

R.

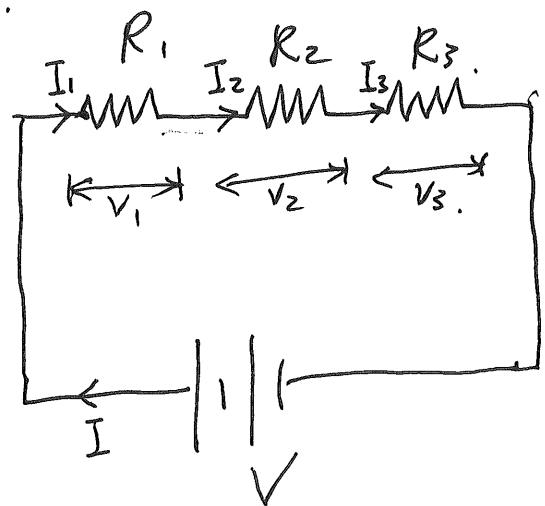

$$V = V_1 + V_2 + V_3$$

$$I_1 = I_2 = I_3$$

$$R_s = R_1 + R_2 + R_3$$


Same result,
Same principle

Similar result
Different principle.

Different
result!

C

In parallel

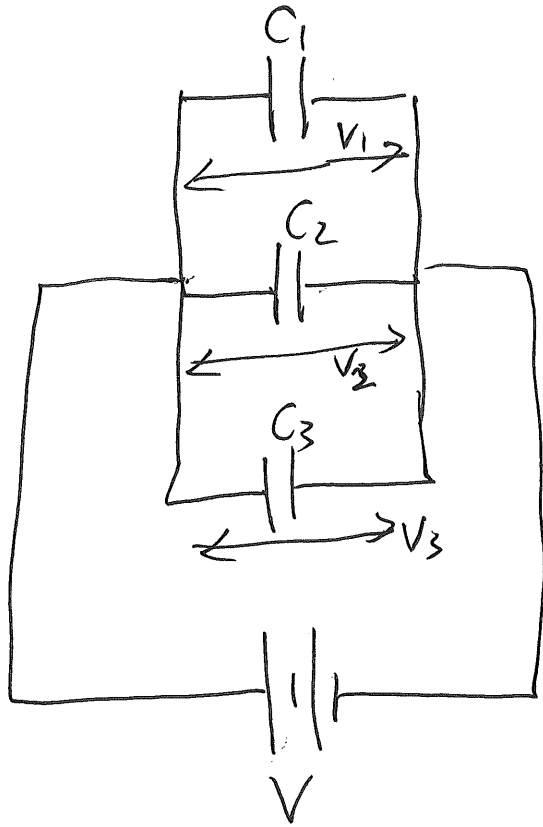


$$V_1 = V_2 = V_3 = V$$

$$Q_1 \neq Q_2 \neq Q_3.$$

$$\text{but } Q = Q_1 + Q_2 + Q_3$$

$$C_p = C_1 + C_2 + C_3.$$

R

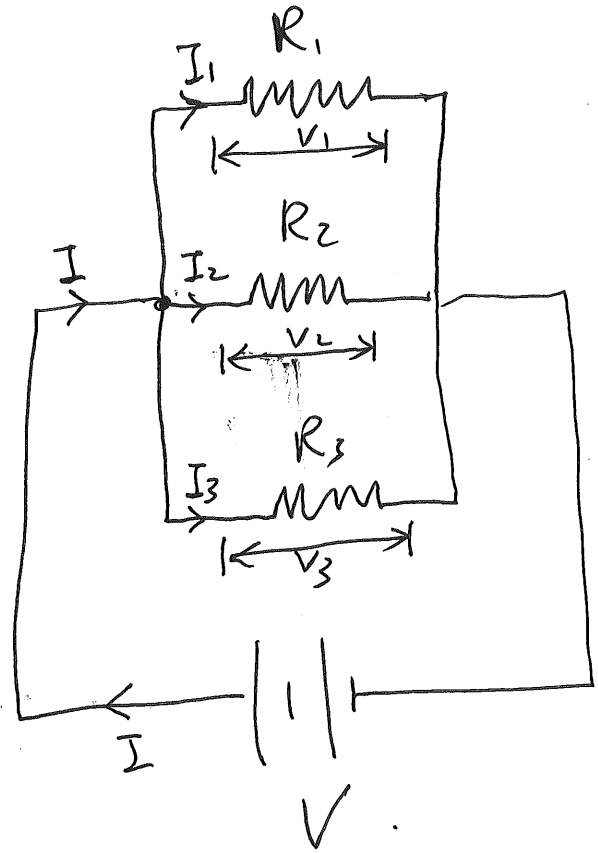

$$V_1 = V_2 = V_3 = V$$

$$I_1 \neq I_2 \neq I_3$$

but

$$I = I_1 + I_2 + I_3.$$

$$\longleftrightarrow \frac{1}{R_s} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}.$$