

$$R = \frac{\rho l}{A}$$

Name: _____

①

PHY 232 Summer 2016 Class Work
Class 18. Current and Resistance

(a) A and B are made of the same kind of material. If A has a resistance R , what is the resistance of B?

$$\frac{\rho L}{\pi (2r)^2} = R \Rightarrow \frac{\rho L}{\pi r^2} = 4R$$

$$\Rightarrow R_B = 4R$$

(b) If A and B are touching each other along its length, what is the resultant resistance across the two ends?


$$\textcircled{1} R_{AB} = \frac{\rho L}{\pi [(2r)^2 + r^2]} = \frac{\rho L}{\pi (5r^2)}$$

$$= \frac{1}{5} \left(\frac{\rho L}{\pi r^2} \right) = \frac{4R}{5}$$


$$\textcircled{2} \frac{1}{R_{AB}} = \frac{1}{R_A} + \frac{1}{R_B}$$

$$= \frac{1}{R} + \frac{1}{4R}$$
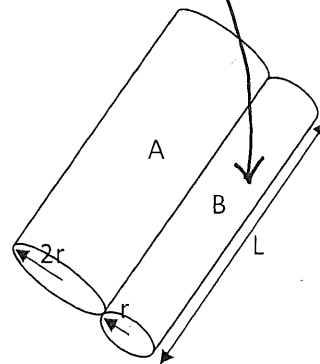
$$= \frac{1}{R} \left(1 + \frac{1}{4} \right) = \frac{5}{4R} \Rightarrow R_{AB} = \frac{4R}{5}$$



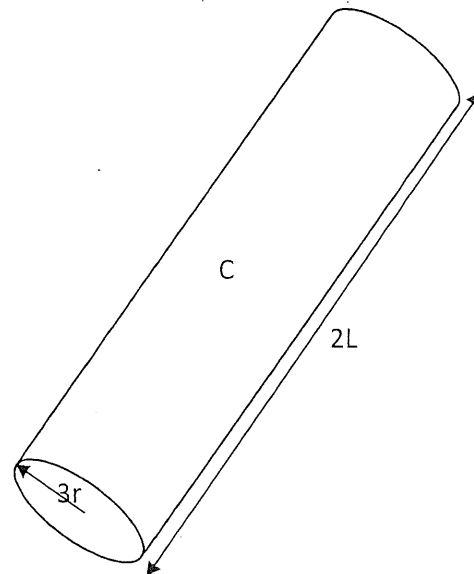(c) C is made of the same kind of material as A and B. If A has a resistance R , what is the resistance of C?





$$\frac{1}{R_p} = \frac{1}{20} + \frac{1}{30}$$


$$= \frac{3+2}{60}$$



$$= \frac{5}{60}$$

$$\Rightarrow R_p = 12\Omega$$

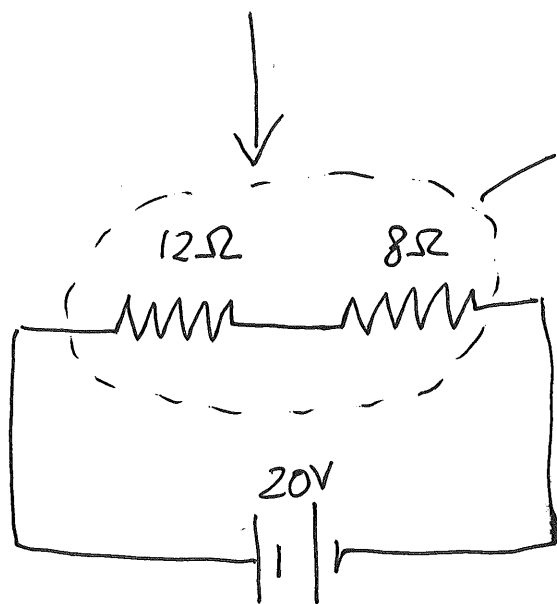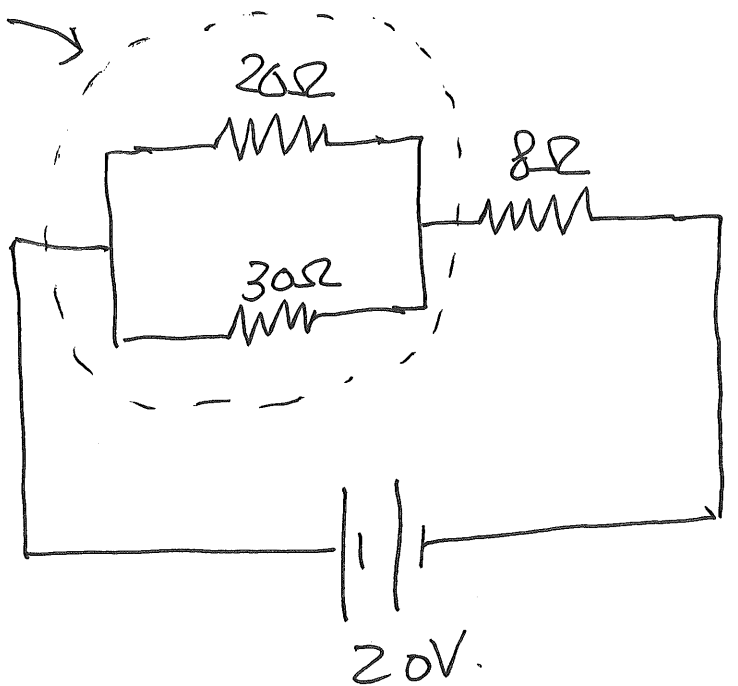


$$R_s = 12\Omega + 8\Omega = 20\Omega$$

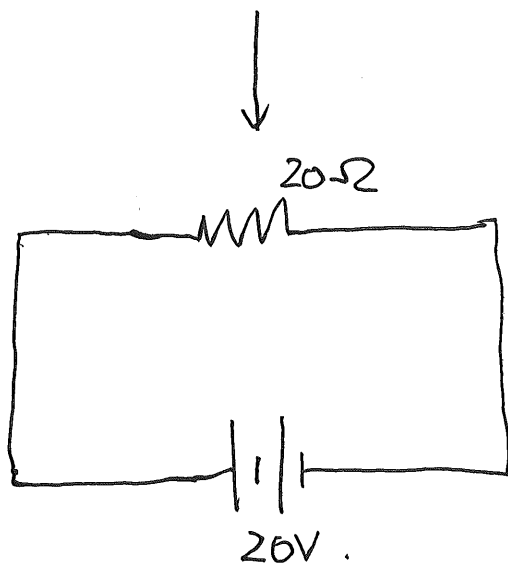

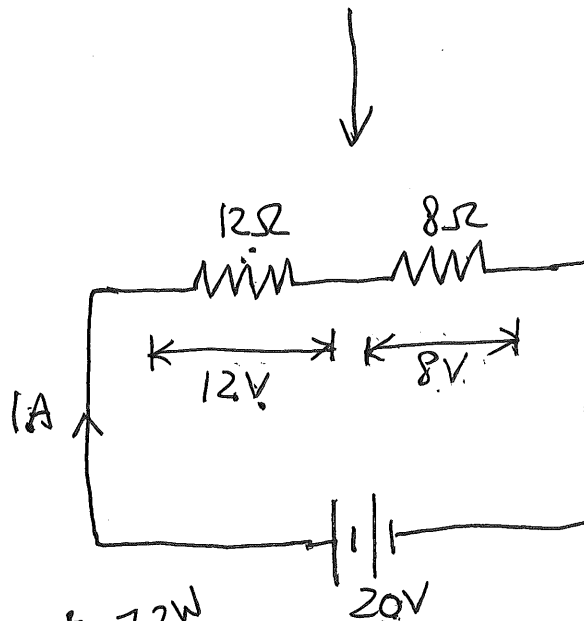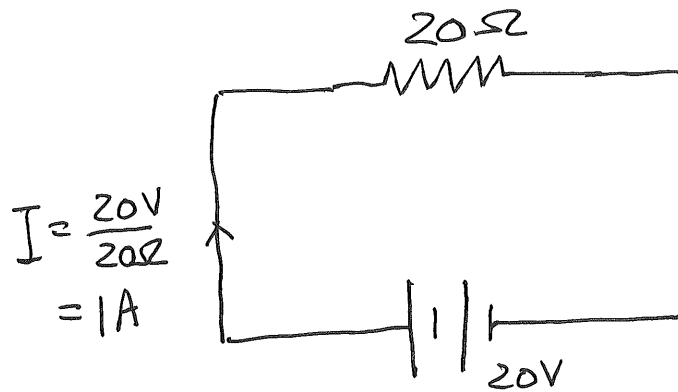


$$P = \frac{(12)^2}{20} = 7.2W$$

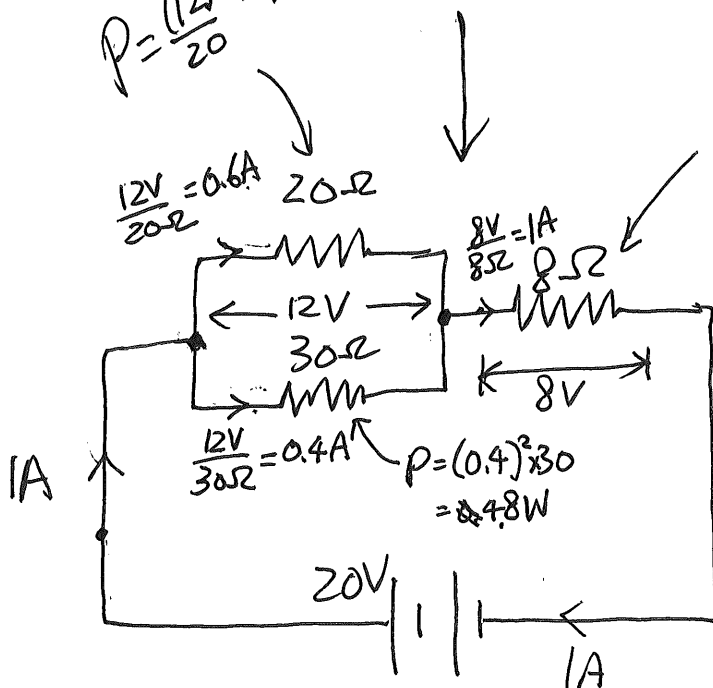

$$P = (8)(1) = 8W$$

Total power dissipation
 by the three resistors
 $= (7.2 + 4.8 + 8)$
 $= 20W$
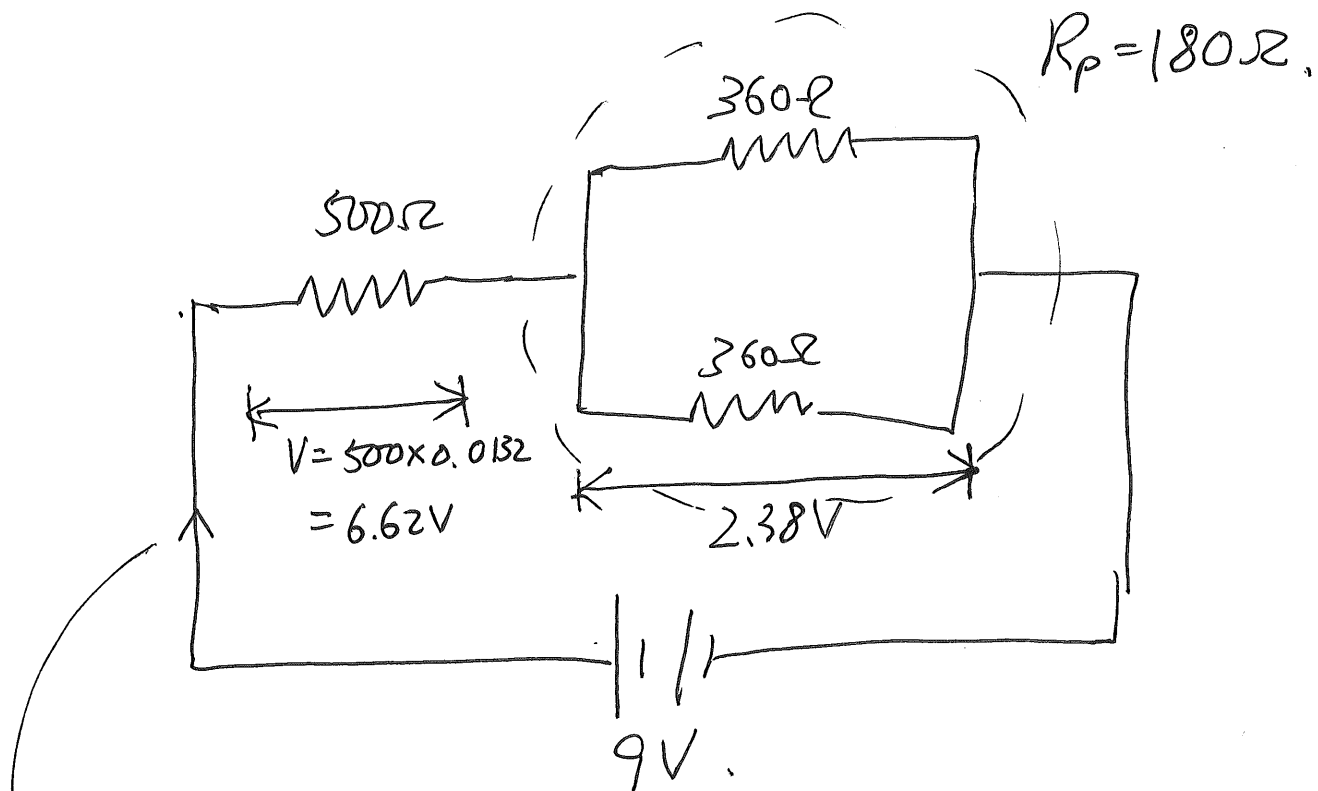
$$\begin{aligned}
 \text{Power delivered by battery} &= IV \\
 &= (1)(20) \\
 &= 20W
 \end{aligned}$$



$$I = \frac{9}{500 + 180} = 0.0132A$$

