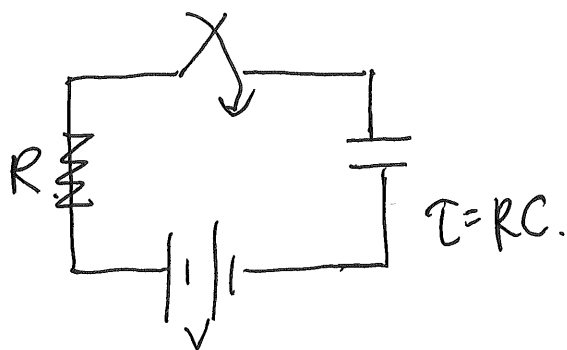



Charging a RC circuit.



At $t=0$. $V_C = 0$
 (Capacitor conducts "perfectly"). $I = \frac{V}{R}$
 $V_R = V$
 $Q = 0$.

At $t=\infty$. $V_C = V$
 (Capacitor does not conduct). $V_R = 0$
 $I = 0$
 $Q = CV$.


Discharging a RC circuit.

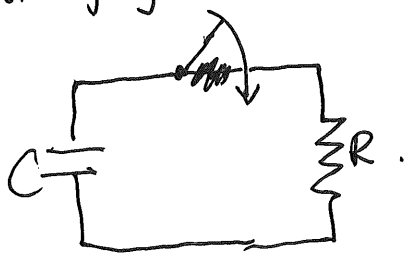

At $t=0$. $I = \frac{V_C}{R}$. $V_R = V_C$
 $V_C = \frac{Q}{C}$.

At $t=\infty$. $I=0$. $V_C=0$. $V_R=0$.


Charging a RL circuit.

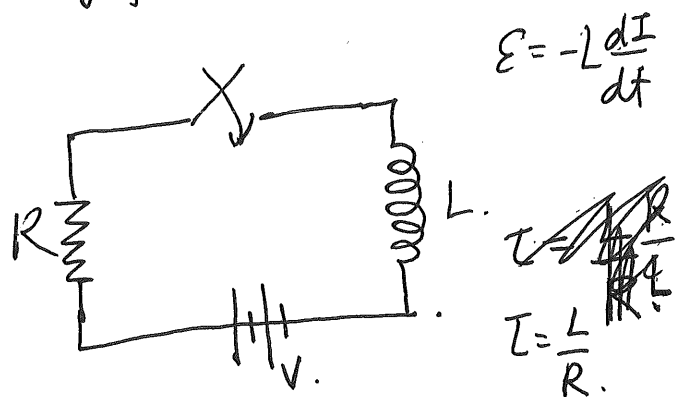

At $t=0$. $V_R = V$
 (Inductor does not conduct). $V_L = V$
 $I = 0$.


At $t=\infty$. $V_R = V$
 (Inductor conducts "perfectly"). $V_L = 0$
 $I = \frac{V}{R}$.

Discharging a RL circuit

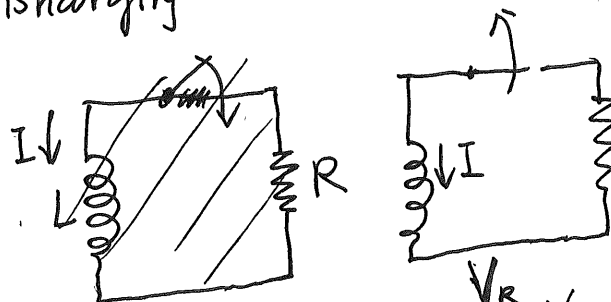


At $t=0$. $I = I_0$. $V_L = V_R = I_0 R$.

At $t=\infty$. $I=0$. $V_L=0$. $V_R=0$.

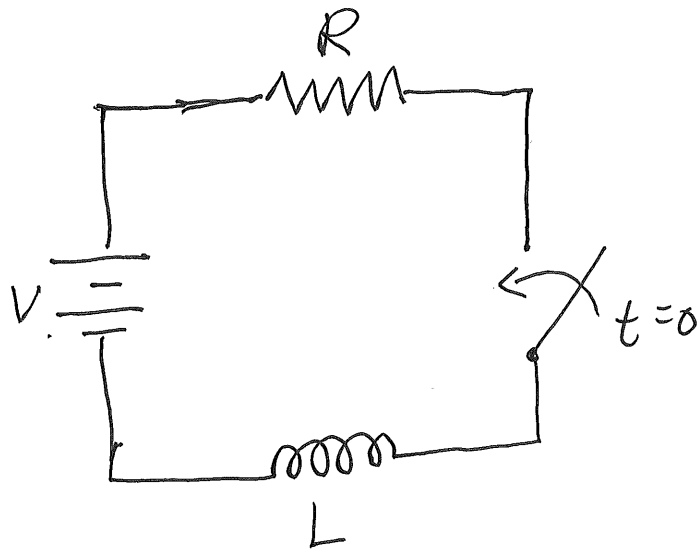

$V_R = 0$ at $t = 0$.

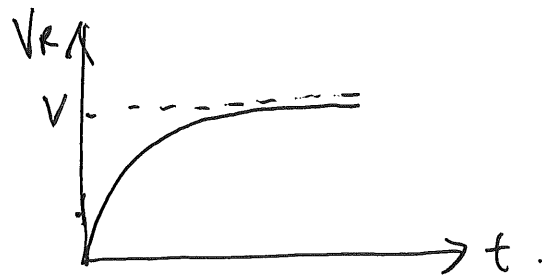

$V_R = V$ at $t = \infty$.

$$I = \frac{V}{R}(1 - e^{-t/\tau}). \quad V_R = V(1 - e^{-t/\tau}). \quad \tau = \frac{L}{R}.$$


$$V_L = V e^{-t/\tau}.$$

$$I = \frac{\mathcal{E}}{R} \left(1 - e^{-\frac{R}{L} t} \right).$$



$$= \frac{\mathcal{E}}{R} \left(1 - e^{-\frac{t}{\left(\frac{L}{R}\right)} \leftarrow \tau} \right).$$

$$\underline{\tau = \frac{L}{R}.$$

"Discharging" a RL circuit.

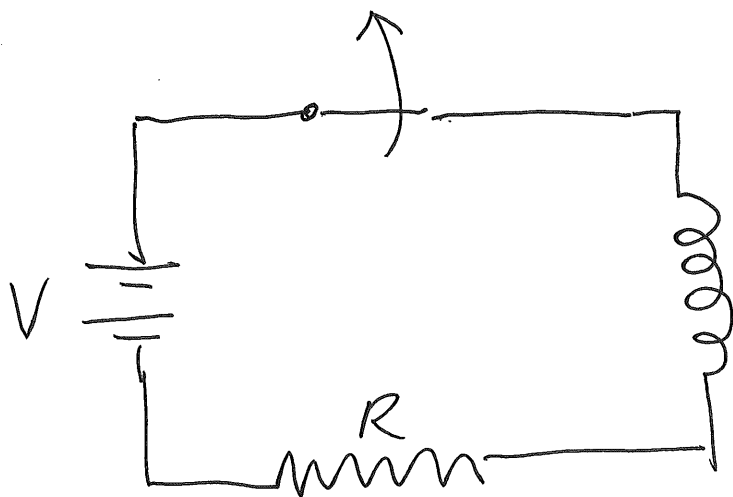

Discharge -

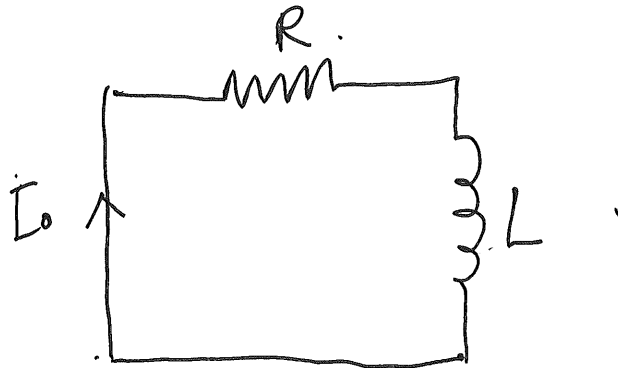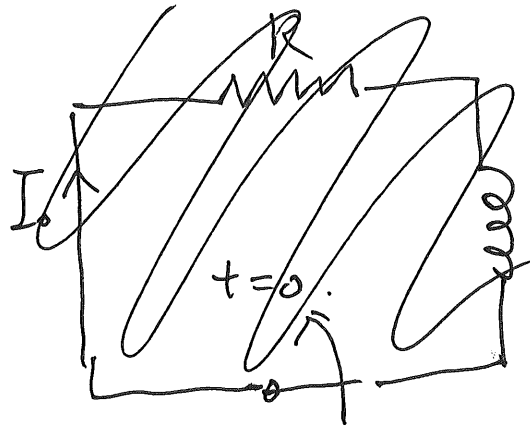

$$V_L = ?$$


$$\text{At } t=0, V_L = V_R.$$

$$t=\infty, V_L = 0.$$

$$\begin{aligned} \therefore V_L &= V_R e^{-t/\tau} \\ &= I_0 R e^{-t/\tau}. \end{aligned}$$

$$\tau = \frac{L}{R}.$$

RC Circuit:

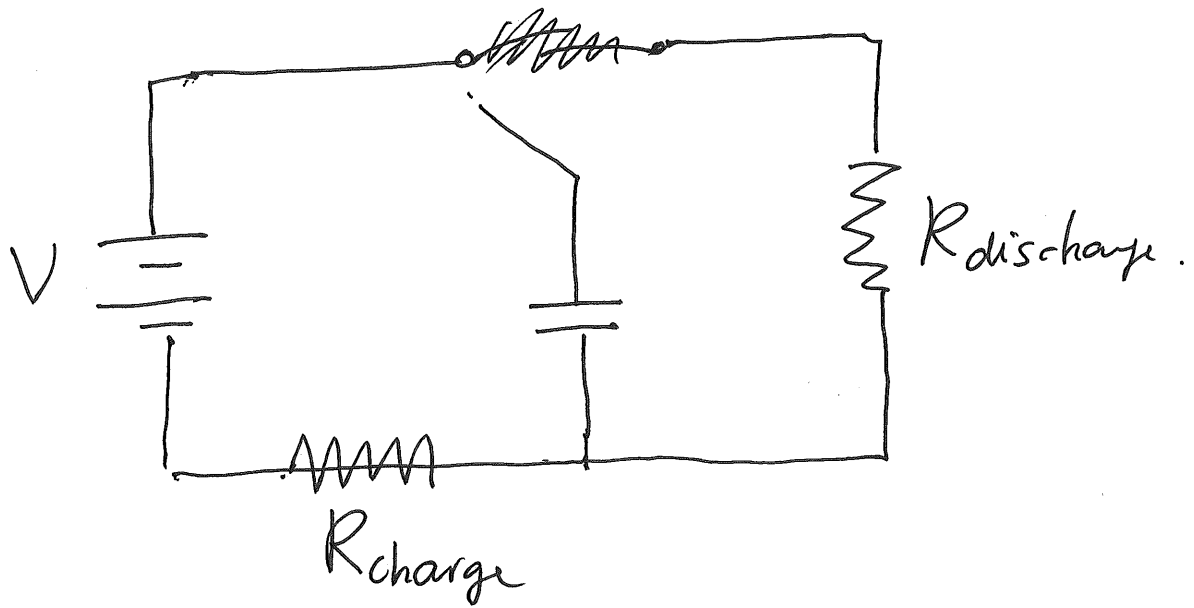

LC Circuit

