

Equation of motion for SHM:

$$\frac{d^2x}{dt^2} = -\omega^2 x.$$

Solution:  $x = A \sin \omega t + B \cos \omega t$

or  $x = A \sin(\omega t + \phi).$

$$m \frac{d^2x}{dt^2} = -kx.$$

$\Downarrow$

$$\omega^2 = \frac{k}{m} \Rightarrow \omega = \sqrt{\frac{k}{m}}$$


—————  $x$  —————

LC oscillation.

Kirchhoff's rule:  $L \frac{d^2Q}{dt^2} = -\frac{1}{C} Q.$

$$\frac{d^2Q}{dt^2} = -\frac{1}{LC} Q. \quad \leftarrow \text{SHM!}$$

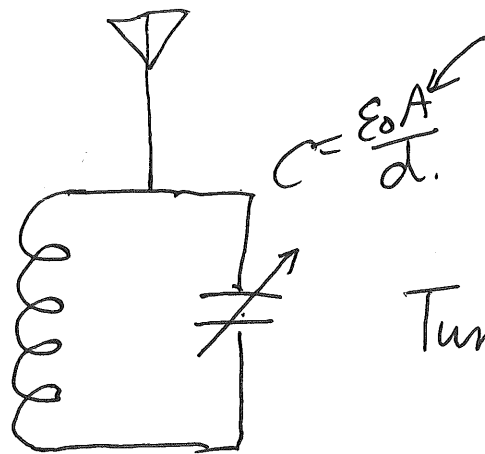
$$\omega^2 = \cancel{\frac{k}{m}} \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}.$$



Tuning circuit.

$\frac{1}{\sqrt{LC}}$  match that  
from radio  
station


AM.

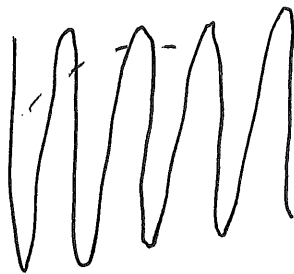

Name: \_\_\_\_\_

PHY 232 Summer 2016 Class Work  
Class 36. LC Circuits Practice

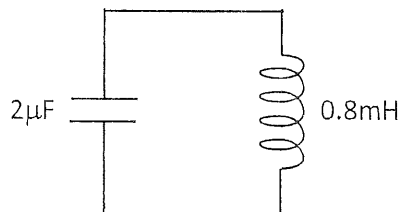Make sure your calculator is set to radian mode. Consider the following circuit



If the charge in the capacitor is given as  $Q = Q_0 \sin(\omega t + \phi)$ .

(a) Calculate the value of  $\omega$  and then the corresponding frequency  $f$  and period  $T$ .

$$\omega = \dots \text{ (known) } .$$

$$\omega = 2\pi f$$

$$f = \frac{1}{T}$$

(b) If the charge and current are  $2\mu\text{C}$  and  $0.05\text{A}$  at  $t=0$ . Determine  $Q_0$  and  $\phi$ .

$$Q = Q_0 \sin(\omega t + \phi) .$$

$\uparrow \quad \quad \quad \uparrow$   
 Unknown

$$2\mu\text{C} = Q_0 \sin \phi .$$

$$I = \frac{dQ}{dt} = Q_0 \omega \cos(\omega t + \phi) .$$

$$0.05 = Q_0 \omega \cos \phi .$$

(c) What are the charge and current at  $t = 10^{-5} \text{ s}$ ?

